

# Circuit Theory 1

## Linear Circuits in Steady State | EE2021E

**Nguyễn Bảo Huy**  
huy.nguyenbao@hust.edu.vn

**Department of Automation Engineering  
School of Electrical and Electronic Engineering  
Hanoi University of Science and Technology**

Hanoi, 2026



# Course Information



- One midterm exam
- One final exam
- Exam structure: 9 points for content and 1 point for presentation
- One A4 sheet of reference material is allowed in the exams
- Bonus points may be added to the coursework grade
  - Solving exercises and class discussions: **0 to 2 bonus points** (no points will be deducted for incorrect solutions or answers)
- Classroom rules
  - No attendance checks or attendance-based grading
  - Students may enter and leave freely and quietly (no permission required)
  - Do not make noise or cause distractions
  - For each reminder to maintain order: **0.25 points will be deducted from the entire class's coursework grade**
- When requested, students are responsible for providing explanations and cooperating to clarify any concerns regarding their examination papers

# How to well study Circuit Theory



1. Do the exercises
2. Do the exercises
3. If you have not done the exercises, review the two points above
  - Sources of exercises
    - In-class examples
    - Homework problems
    - Previous exams
    - Reference materials

1. Charles K. Alexander, Matthew N. O. Sadiku, *Fundamentals of Electric Circuits*, McGraw-Hill, 2021.
2. James Nilsson, Susan Riedel, *Electric Circuits*, 11<sup>th</sup>, Pearson, 2020.
3. William H. Hayt, Jack E. Kemmerly, Steven M. Durbin, *Engineering Circuit Analysis*, 8<sup>th</sup>, McGraw-Hill, 2012.
4. Mahmood Nahvi, Joseph A. Edminister, *Schaum's Outline of Electric Circuits*, 7<sup>th</sup>, McGraw-Hill, 2018.

## **Circuit Theory 1**

1. Linear circuits in steady state

## **Circuit Theory 2**

2. Linear circuits in transient state
3. Nonlinear circuits (steady state and transient state)
4. Transmission lines (steady state and transient state)

# Circuit Theory 1: Linear Circuits in Steady State



- 1 Concepts of Kirchhoff Circuit Model
- 2 Linear Circuits in Steady State with DC Sources
- 3 Methods for Solving Linear Steady-State DC Circuits
- 4 Linear Circuits in Steady State with Sinusoidal Sources
- 5 Methods for Solving Linear Steady-State AC circuits
- 6 Thévenin–Norton Theorem and One-Port Networks
- 7 Mutual Inductance and Solving Magnetically Coupled Circuits
- 8 Two-Port Networks
- 9 Circuits with Multiple Frequencies and Non-Sinusoidal Sources
- 10 Three-Phase Circuits



# Course Outline

- 1 Concepts of Kirchhoff Circuit Model
- 2 Linear Circuits in Steady State with DC Sources
- 3 Methods for Solving Linear Steady-State DC Circuits
- 4 Linear Circuits in Steady State with Sinusoidal Sources
- 5 Methods for Solving Linear Steady-State AC circuits
- 6 Thévenin–Norton Theorem and One-Port Networks
- 7 Mutual Inductance and Solving Magnetically Coupled Circuits
- 8 Two-Port Networks
- 9 Circuits with Multiple Frequencies and Non-Sinusoidal Sources
- 10 Three-Phase Circuits



# Chapter Outline

- 1 Concepts of Kirchhoff Circuit Model
  - Circuit Theory and the Modeling Approach
  - Basic Concepts and Quantities
  - Basic Circuit Elements
  - Circuit Models
  - Basic Problems in Electric Circuits
  - Basic Laws in Electric Circuits
  - Kirchhoff Equations System of a Circuit



# Chapter Outline

- 1 Concepts of Kirchhoff Circuit Model
  - Circuit Theory and the Modeling Approach
  - Basic Concepts and Quantities
  - Basic Circuit Elements
  - Circuit Models
  - Basic Problems in Electric Circuits
  - Basic Laws in Electric Circuits
  - Kirchhoff Equations System of a Circuit



# The Role of Circuit Theory


- General knowledge
  - Linear algebra
  - Single-variable calculus
  - Differential equations
  - Introductory physics (electricity)
- **Circuit Theory**  $\Leftrightarrow$  Signals and systems; automatic control theory
- Specialized knowledge
  - Analog electronics
  - Electrical machines
  - Power electronics
  - Electric drives
  - Power systems
  - etc.



# The Modeling Approach
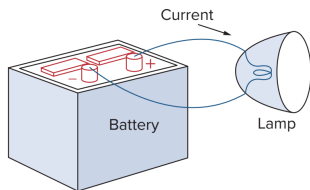
## Problem

- Find the current flowing through the lamp




## Approach \$

- Buy battery, lamp, wires, and multimeter  $\Rightarrow$  build the circuit

## Approach ☹️

- From the physical and chemical properties of the battery  $\Rightarrow$  charges on the two electrodes  $\Rightarrow$  electric field in space  $\Rightarrow$  charges flowing in the wires and lamp  $\Rightarrow$  current

## Approach 😊

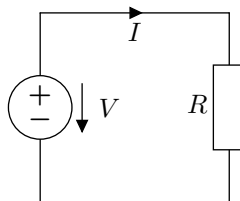

$$I = \frac{V}{R}$$



Note: the *assumptions* for modeling



# Chapter Outline

## 1 Concepts of Kirchhoff Circuit Model

- Circuit Theory and the Modeling Approach
- Basic Concepts and Quantities
- Basic Circuit Elements
- Circuit Models
- Basic Problems in Electric Circuits
- Basic Laws in Electric Circuits
- Kirchhoff Equations System of a Circuit



# Basic Concepts and Quantities: Current

- Current is the rate of change of electric charge with respect to time  
Charge is in coulombs (C); current is in amperes (A)

$$i = \frac{dq}{dt}$$

- Pay attention to the reference direction of current

$$i_{ab}(t) = -i_{ba}(t)$$






# Basic Concepts and Quantities: Voltage

- The voltage (potential difference) between two points is the energy required to move one unit of charge from one point to the other  
Energy is measured in joules (J); voltage is measured in volts (V)


$$u_{ab} = \frac{dw_{ab}}{dq}$$

- Pay attention to the reference direction of the voltage arrow

$$u_{ab}(t) = -u_{ba}(t)$$

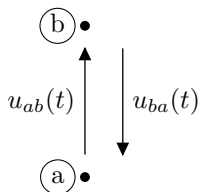

- Voltage “triangle” formula

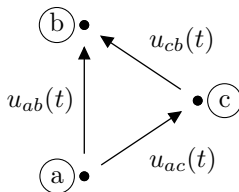

$$u_{ab}(t) = u_{ac}(t) + u_{cb}(t)$$




# Some Basic Concepts and Quantities: Power

- Power is the rate of change of energy with respect to time  
Power is measured in watts (W)

$$p = \frac{dw}{dt} \Leftrightarrow p = \frac{dw}{dq} \cdot \frac{dq}{dt} = u \cdot i$$

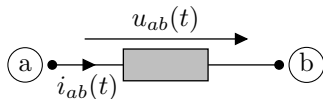$\Rightarrow$  Power = voltage  $\times$  current



- Instantaneous absorbed power:  $p(t) = u_{ab}(t) \cdot i_{ab}(t)$
- Instantaneous supplied power:  $-p(t) = u_{ab}(t) \cdot i_{ba}(t)$

**!** Pay attention to the reference directions of current and voltage arrows and to the sign of power

- Average power over the time interval  $T$ :

$$P_{\text{avg}} = \frac{1}{T} \int_0^T p(t) dt$$



# Chapter Outline

## 1 Concepts of Kirchhoff Circuit Model

- Circuit Theory and the Modeling Approach
- Basic Concepts and Quantities
- **Basic Circuit Elements**
- Circuit Models
- Basic Problems in Electric Circuits
- Basic Laws in Electric Circuits
- Kirchhoff Equations System of a Circuit



# Basic Elements: Characteristic Relations

- Circuit Theory is mainly concerned with two basic quantities: current and voltage; they are called the *state variables*  
(Power is derived from current and voltage)
  - Each element is characterized by the relation between the current and the voltage on that element
- ⇒ This is called the *characteristic relation* of the element
- There are two forms of an element's characteristic relation
    1.  $i(t) = f(u(t))$  or  $u(t) = f(i(t))$
    2.  $i(t) = f_i(t)$   
 $u(t) = f_u(t)$



# Basic Elements: Classification

## Active and passive

- An *active element* can supply energy

Examples: source elements and operational amplifiers (op-amps)

- A *passive element* can only absorb and/or store energy

Examples: resistors, inductors, capacitors

## Linear and nonlinear

- A *linear element* has a characteristic relation that is a linear function (algebraic or differential or integral)

A circuit consisting only of linear elements is a linear circuit

Recall: linearity means satisfying the *superposition principle*

- A *nonlinear element* has a nonlinear characteristic equation

A circuit with at least one nonlinear element is a nonlinear circuit



# Source Elements

A source is an element that supplies electromagnetic energy to a circuit


## Types of electrical sources

- Voltage sources and current sources
- Independent sources and dependent sources
- ⇒ Four main combinations:
  - independent voltage source
  - independent current source
  - dependent voltage source
  - dependent current source
- Dependent sources are also called controlled sources
- Regarding control signal, dependent sources are classified:
  - voltage-controlled voltage source (VCVS)
  - current-controlled voltage source (CCVS)
  - voltage-controlled current source (VCCS)
  - current-controlled current source (CCCS)


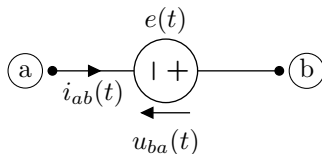
# Independent Voltage Source

- An independent voltage source supplies a voltage that does not depend on the current flowing through it
- Symbol:



- Characteristic relation:  $u_{ba}(t) = e(t), \forall i_{ab}(t), \forall t$

Interpretation: the voltage of a voltage source is equal to the source electromotive force regardless of the current through it




Notes:

- Other materials may use different symbols
- This is an ideal voltage-source model; a practical voltage source can be modeled by an ideal voltage source and other elements
- In practical circuits, never short-circuit a voltage source


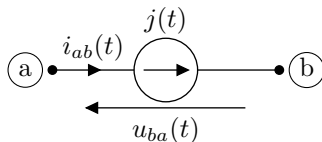
# Independent Current Source

- An independent current source supplies a current that does not depend on the voltage across it
- Symbol:



- Characteristic relation:  $i_{ab}(t) = j(t), \forall u_{ba}(t), \forall t$

Interpretation: the current of a current source is equal to the source current regardless of the voltage applied across it



Notes:

- Other materials may use different symbols
- This is an ideal current-source model; a practical current source can be modeled by an ideal current source and other elements
- In practical circuits, never open-circuit a current source



# Passive Elements

There are three types of passive elements

## 1. Energy-dissipating elements

- Completely dissipate energy at all times
- Do not supply or store energy

## 2. Electric-energy storage elements

- Do not dissipate energy
- Store energy in the form of electric charge

## 3. Magnetic-energy storage elements

- Do not dissipate energy
- Store energy in the form of magnetic flux




# Resistor

- A resistor is an energy-dissipating element; its unit is the ohm ( $\Omega$ )
- $\Rightarrow$  Absorbed power is always nonnegative:  $p(t) = u_{ab}(t) \cdot i_{ab}(t) \geq 0$
- $\Rightarrow$  There is a positive ratio between voltage and current on a resistor:

$$R = \frac{u_{ab}(t)}{i_{ab}(t)} \Leftrightarrow u_{ab}(t) = R \cdot i_{ab}(t), \forall i_{ab}(t), \forall t$$

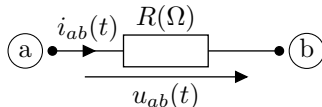- If  $R$  is constant  $\Rightarrow$  linear resistor
- If  $R = R(i)$  or  $R = R(u)$  which is variable  $\Rightarrow$  nonlinear resistor



Notes:


- Directions of current and voltage, and sign of absorbed power
- Conductance is the reciprocal of resistance; its unit is siemens (S)

$$G = \frac{1}{R} \Leftrightarrow i_{ab}(t) = G \cdot u_{ab}(t)$$


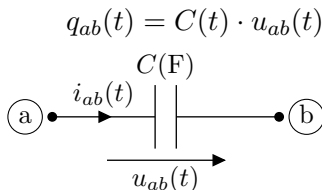
# Capacitance (Capacitor)

- A capacitor stores energy in the form of electric charge  $q_{ab}(t)$  proportional to the voltage  $u_{ab}(t)$  through the coefficient  $C$ , called the capacitor's *capacitance*; its unit is the farad (F)



- From the relation between current and charge, the characteristic relation of a capacitor is:

$$i_{ab}(t) = \frac{dq_{ab}(t)}{dt} \Leftrightarrow i_{ab}(t) = \frac{d(C(t) \cdot u_{ab}(t))}{dt}$$

- If  $C(t) = C$  is constant  $\Rightarrow$  linear capacitor


$$i_{ab}(t) = C \cdot \frac{du_{ab}(t)}{dt}$$



# Inductance (Inductor)

- An inductor stores energy in the form of magnetic flux  $\Psi_{ab}(t)$  proportional to the current  $i_{ab}(t)$  through the inductor's *inductance*  $L$ ; its unit is the henry (H)

$$\Psi_{ab}(t) = L(t) \cdot i_{ab}(t)$$

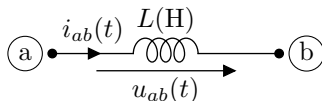

- Variation of magnetic flux induces an electromotive force in the inductor  $\Rightarrow$  the characteristic relation of an inductor is:

$$u_{ab}(t) = \frac{d\Psi_{ab}(t)}{dt} \Leftrightarrow u_{ab}(t) = \frac{d(L(t) \cdot i_{ab}(t))}{dt}$$


- If  $L(t) = L$  is constant  $\Rightarrow$  linear inductor

$$u_{ab}(t) = L \cdot \frac{di_{ab}(t)}{dt}$$


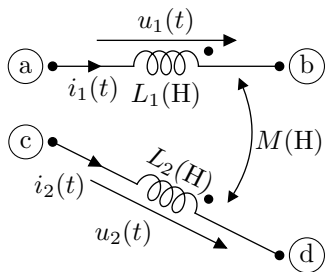
# Mutual Inductance Between Coils

- If there is flux in only one coil, the coefficient  $L$  is the coil's *self-inductance*
- If two or more coils have mutual flux linkages, there is a *mutual inductance*  $M$  between the coils



- Flux linkages:

$$\begin{cases} \Psi_1(t) = L_1 \cdot i_1(t) \pm M \cdot i_2(t) \\ \Psi_2(t) = L_2 \cdot i_2(t) \pm M \cdot i_1(t) \end{cases}$$


- Linear self-inductance and mutual inductance:

$$\begin{cases} u_1(t) = \frac{d\Psi_1(t)}{dt} = L_1 \cdot \frac{di_1(t)}{dt} \pm M \cdot \frac{di_2(t)}{dt} \\ u_2(t) = \frac{d\Psi_2(t)}{dt} = L_2 \cdot \frac{di_2(t)}{dt} \pm M \cdot \frac{di_1(t)}{dt} \end{cases}$$




# Dependent Sources

## Voltage-controlled voltage source

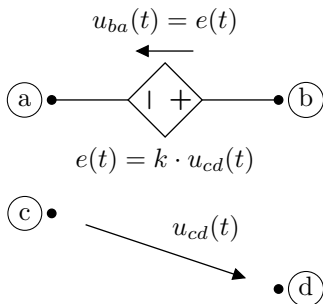


## Current-controlled voltage source

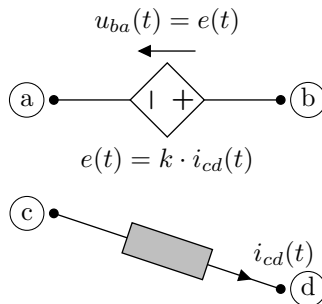




# Dependent Sources

## Voltage-controlled current source

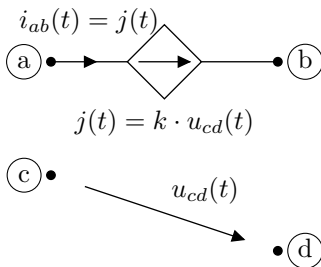

## Current-controlled current source

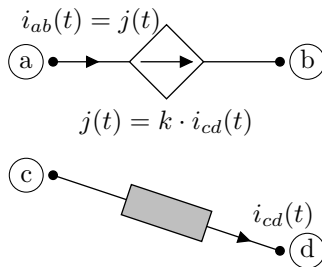




# Operational Amplifier (Op-amp)
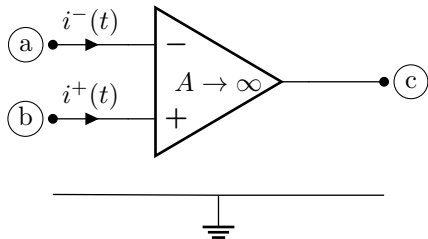
## Operational amplifier

- A signal amplifier with a very large gain  
 $A \sim 10^5 \rightarrow 10^7$
- Commonly used to implement operations such as  $+$   $-$   $\times$   $\div$   $d/dt$   $\int$
- Characteristic relation
 
$$\begin{cases} i^+ \approx 0; i^- \approx 0 \\ v_c(t) = A(v_b(t) - v_a(t)) \end{cases}$$



## Ideal op-amp

- Gain  $A = \infty$ 

$$\begin{cases} i^+ = 0; i^- = 0 \\ v_a(t) = v_b(t) \end{cases}$$




# Chapter Outline

## 1 Concepts of Kirchhoff Circuit Model

- Circuit Theory and the Modeling Approach
- Basic Concepts and Quantities
- Basic Circuit Elements
- **Circuit Models**
- Basic Problems in Electric Circuits
- Basic Laws in Electric Circuits
- Kirchhoff Equations System of a Circuit



# Circuit Models

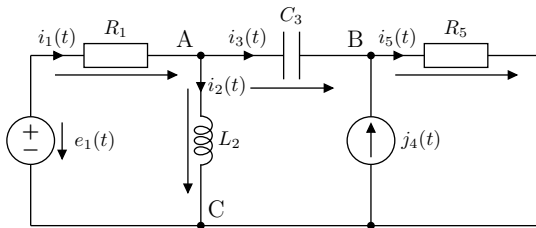


## Topology of a circuit

- A **node** is a connection point of two or more elements. The *degree* of a node is the number of elements connected to it. (If the terminal of an element is not connected to any other element, it is a 1<sup>st</sup>-order node.) In Circuit Theory, we usually focus on nodes of 3<sup>rd</sup> or higher order (called *essential nodes*).
- A **branch** is a path connecting two essential nodes
- A **loop** is a closed path through circuit branches



# Circuit Models

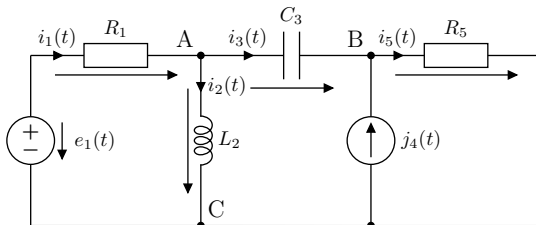


## Topology of a circuit

- A **tree** is a set of branches that connects all nodes of a circuit without forming any closed loop
- A **co-tree** consists of the remaining branches of the circuit that do not belong to the tree being considered
- A **fundamental loop** is the loop formed by one co-tree branch and branches of the tree being considered



# Circuit Models

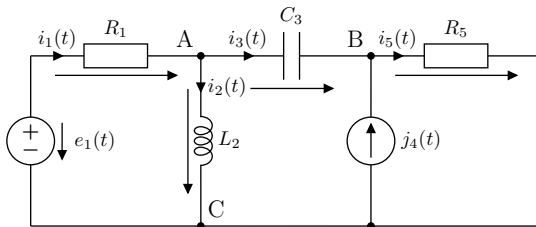

## Some basic concepts

- **Branch current** is the current flowing through the elements of a branch
- **Node potential** is the voltage of that node relative to a node chosen as the reference point (the “ground” node); the ground potential is  $v_{\text{gnd}} = 0$



# Chapter Outline

- 1 Concepts of Kirchhoff Circuit Model
  - Circuit Theory and the Modeling Approach
  - Basic Concepts and Quantities
  - Basic Circuit Elements
  - Circuit Models
  - **Basic Problems in Electric Circuits**
  - Basic Laws in Electric Circuits
  - Kirchhoff Equations System of a Circuit



# Basic Problems in Electric Circuits

## Circuit analysis problem

- Given the circuit structure
- Given the values of the circuit elements
- Find the state-variable pair of current  $i(t)$  and voltage  $u(t)$  on the elements, then determine the power  $p(t)$

## Circuit synthesis (design) problem

- Given requirements for current  $i(t)$ , voltage  $u(t)$ , and power  $p(t)$
- Propose a circuit structure
- Find the values of the circuit elements

Circuit Theory mainly considers circuit analysis problems.



# Chapter Outline

## 1 Concepts of Kirchhoff Circuit Model

- Circuit Theory and the Modeling Approach
- Basic Concepts and Quantities
- Basic Circuit Elements
- Circuit Models
- Basic Problems in Electric Circuits
- **Basic Laws in Electric Circuits**
- Kirchhoff Equations System of a Circuit



# Basic Laws in Electric Circuits


## Kirchhoff's current law (KCL)

- For any node: the algebraic sum of currents at the node is zero

Convention: currents entering the node have sign +, currents leaving the node have sign -

$$\sum a_k \cdot i_k(t) = 0; \text{ entering current: } a_k = 1; \text{ leaving current: } a_k = -1$$

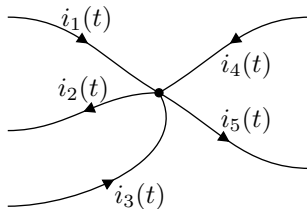- Equivalently: the sum of currents entering a node equals the sum of currents leaving that node:  $\sum i_{\text{in}}(t) = \sum i_{\text{out}}(t)$






# Basic Laws in Electric Circuits
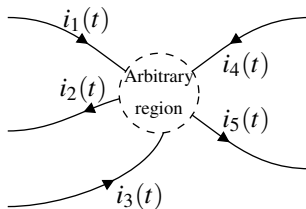
## Extended KCL

- For any closed circuit region: the sum of currents entering the region equals the sum of currents leaving it

$$\sum i_{\text{in}}(t) = \sum i_{\text{out}}(t)$$






# Basic Laws in Electric Circuits

## Kirchhoff's voltage law (KVL)

- For any loop: the algebraic sum of voltages around the loop is zero
- Voltages in the reference direction of the loop have sign +
- Voltages opposite to the reference direction have sign -

$$\sum a_k \cdot u_k(t) = 0$$

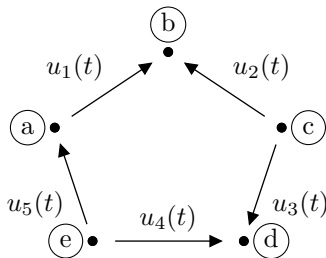same direction:  $a_k = 1$ ; opposite direction:  $a_k = -1$





# Basic Laws in Electric Circuits

## Some consequences of the two Kirchhoff laws

- Elements connected in series have the same current
- Elements connected in parallel have the same voltage
- Two different voltage sources must not be connected in parallel
- Two different current sources must not be connected in series




# Basic Laws in Electric Circuits
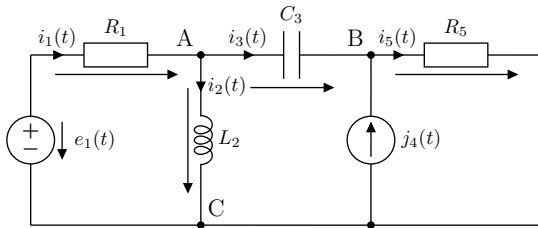
## Power conservation law

- At every instant, the total supplied power equals the total absorbed power
- For the circuit below

$$e_1(t) \cdot i_1(t) + j_4(t) \cdot u_5(t) = u_1(t) \cdot i_1(t) + u_2(t) \cdot i_2(t) + u_3(t) \cdot i_3(t) + u_5(t) \cdot i_5(t)$$





# Basic Laws in Electric Circuits

## Some other laws and properties

- Flux conservation in inductors
- Charge conservation in capacitors
- Superposition property of linear circuits



# Chapter Outline

- 1 Concepts of Kirchhoff Circuit Model
  - Circuit Theory and the Modeling Approach
  - Basic Concepts and Quantities
  - Basic Circuit Elements
  - Circuit Models
  - Basic Problems in Electric Circuits
  - Basic Laws in Electric Circuits
  - Kirchhoff Equations System of a Circuit



# Kirchhoff Equations System of a Circuit

## Variables and equations in a circuit analysis problem


- Unknown variables are currents and voltages on circuit elements
  - For each element, if the current is known then the voltage can be determined, and vice versa (except source elements)
  - On each branch, series-connected elements have the same current
- ⇒ If there are  $b$  unknown branches, set up  $b$  equations to find  $b$  variables

## What type of equations?

- A circuit has  $n$  essential nodes and  $l$  fundamental loops *that do not contain current sources*
- ⇒  $n - 1$  equations from KCL
- ⇒  $l$  equations from KVL
- It is easy to see that  $l = b - (n - 1) = b - n + 1$


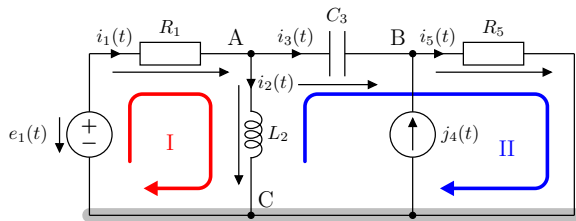
# Kirchhoff Equations System of a Circuit



- Number of equations:  $b = 4$
- Number of KCL equations:  $3 - 1 = 2$
- Number of KVL equations:  $4 - 2 = 2$
- Choose C as ground; write the KCL equations for nodes A and B

$$i_1(t) - i_2(t) - i_3(t) = 0$$

$$i_3(t) + j_4(t) - i_5(t) = 0$$

- Choose loops I and II as shown; write the KVL equations

$$u_1(t) + u_2(t) - e_1(t) = 0$$

$$u_3(t) + u_5(t) - u_2(t) = 0$$



# Course Outline

- 1 Concepts of Kirchhoff Circuit Model
- 2 Linear Circuits in Steady State with DC Sources**
- 3 Methods for Solving Linear Steady-State DC Circuits
- 4 Linear Circuits in Steady State with Sinusoidal Sources
- 5 Methods for Solving Linear Steady-State AC circuits
- 6 Thévenin–Norton Theorem and One-Port Networks
- 7 Mutual Inductance and Solving Magnetically Coupled Circuits
- 8 Two-Port Networks
- 9 Circuits with Multiple Frequencies and Non-Sinusoidal Sources
- 10 Three-Phase Circuits



# Chapter Outline

- 2 Linear Circuits in Steady State with DC Sources
  - Kirchhoff Equation System of a DC Circuit
  - Branch-Current Method
  - Power in DC Circuits



# Chapter Outline

- 2 Linear Circuits in Steady State with DC Sources
  - Kirchhoff Equation System of a DC Circuit
  - Branch-Current Method
  - Power in DC Circuits



# Quantities in DC Circuits

- A DC circuit is a circuit whose sources are *DC sources*
  - A DC source supplies a voltage or current that is *constant*  
(More generally, a DC source is a source whose current or voltage *does not change sign*. In this section, only the special constant case is considered.)
- ⇒ In *steady state* in a DC circuit, all current and voltage quantities are constant

$$u(t) = U = \text{const}$$

$$i(t) = I = \text{const}$$

- ⇒ Power in a DC circuit is also constant

$$p(t) = u(t) \cdot i(t) = U \cdot I = P = \text{const}$$



# Elements in DC Circuits

- In DC circuits, the elements L and C degenerate

- Consider the characteristic relation of an inductor:

$$u_L(t) = L \cdot \frac{di_L(t)}{dt}; \text{ in a DC circuit } i_L(t) = I_L = \text{const}$$

$\Rightarrow u_L(t) = 0 \Leftrightarrow$  *the inductor is short-circuited*

- Consider the characteristic relation of a capacitor:

$$i_C(t) = C \cdot \frac{du_C(t)}{dt}; \text{ in a DC circuit } u_C(t) = U_C = \text{const}$$


$\Rightarrow i_C(t) = 0 \Leftrightarrow$  *the capacitor is open-circuited*

$\Rightarrow$  A DC circuit is equivalent to a **purely resistive** circuit



# Kirchhoff Equation System of a DC Circuit

## Example 2.1

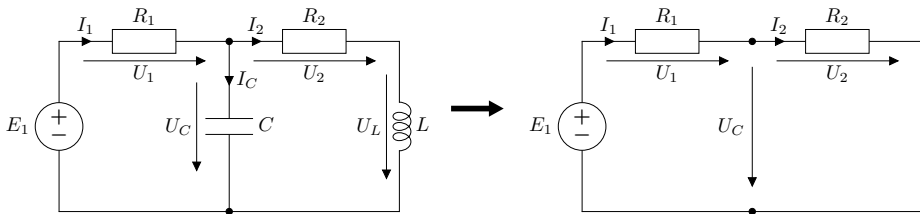

$$i_L(t) = I_L = I_2 = I_1$$

$$u_C(t) = U_C = E_1 - U_1$$



# Chapter Outline

- 2 Linear Circuits in Steady State with DC Sources
  - Kirchhoff Equation System of a DC Circuit
  - Branch-Current Method
  - Power in DC Circuits



# Branch-Current Method

- The KCL and KVL equation systems contain both types of state variables: currents and voltages
  - A circuit with  $b$  branches has  $2b$  unknowns ( $b$  currents and  $b$  voltages)  $\Rightarrow$  direct solution is inconvenient
- $\Rightarrow$  We need to reduce the number of unknowns and equations

## Branch-current method

- The unknown variables are the currents flowing in the branches
- $\Rightarrow$  If the circuit has  $b$  unknown branches, set up  $b$  equations to find  $b$  branch currents
- Then use Ohm's law to determine voltages on branches and elements



# Branch-Current Method

Procedure: Start from the Kirchhoff equation system

- The KCL equations already use branch currents as variables  $\Rightarrow$  keep them unchanged
  - Convert the voltages in the KVL equations into relations of branch currents using Ohm's law
- ⚠ If there are dependent sources  $\Rightarrow$  must continue math operations to have an equation system with only branch-current variables.
- $\Rightarrow$  Solve  $b$  equations in  $b$  branch-current unknowns  $\Rightarrow$  use Ohm's law to determine voltages on branches and elements


## Summary

- Keep KCL in the form  $\sum I$
  - Convert KVL from the form  $\sum U$  to the form  $\sum (R \cdot I)$
- $\Rightarrow$  Solve for  $I \Rightarrow$  determine  $U$



# Branch-Current Method

## Example 2.2

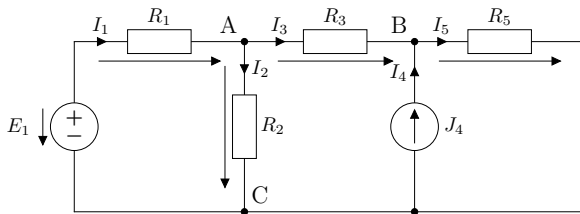


- Number of KCL equations:
- Number of KVL equations:
- Choose nodes and current directions; write KCL equations:
- Choose loops and voltage directions; write KVL equations:



# Branch-Current Method

## Example 2.2

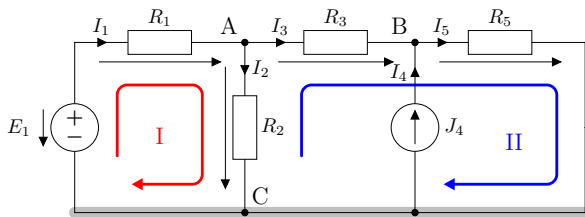

### Kirchhoff equation system

$$I_1 - I_2 - I_3 = 0$$

$$I_3 + J_4 - I_5 = 0$$

$$U_1 + U_2 - E_1 = 0$$

$$-U_2 + U_3 + U_5 = 0$$

### Branch-current equation system

$$I_1 - I_2 - I_3 = 0$$

$$I_3 - I_5 = -J_4$$


$$R_1 \cdot I_1 + R_2 \cdot I_2 = E_1$$

$$-R_2 \cdot I_2 + R_3 \cdot I_3 + R_5 \cdot I_5 = 0$$



# Branch-Current Method

## Example 2.2

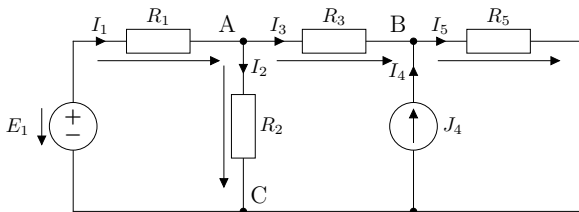

Substitute values:

- $E_1 = 15 \text{ V}; R_1 = 5 \Omega;$
- $R_2 = 8 \Omega; R_3 = 6 \Omega;$
- $J_4 = 1 \text{ A}; R_5 = 10 \Omega.$

### Branch-current equation system

$$I_1 - I_2 - I_3 = 0$$

$$I_3 - I_5 = -1$$

$$5 \cdot I_1 + 8 \cdot I_2 = 15$$

$$-8 \cdot I_2 + 6 \cdot I_3 + 10 \cdot I_5 = 0$$

### Branch-current results

$$I_1 = \quad \text{A}$$

$$I_2 = \quad \text{A}$$

$$I_3 = \quad \text{A}$$

$$I_5 = \quad \text{A}$$



# Solution Method

Write in matrix form

$$\begin{bmatrix} 1 & -1 & -1 & 0 \\ 0 & 0 & 1 & -1 \\ 5 & 8 & 0 & 0 \\ 0 & -8 & 6 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_5 \end{bmatrix} = \begin{bmatrix} 0 \\ -1 \\ 15 \\ 0 \end{bmatrix}$$

Method 1: Use MATLAB (or equivalent tools such as Scilab)

```
>> A = [1 -1 -1 0; 0 0 1 -1; 5 8 0 0; 0 -8 6 10];
>> B = [0; -1; 15; 0];
>> X = inv(A)*B
```

X =

```
1.1290
1.1694
-0.0403
0.9597
```

- Should be used only to verify results
- Should not be overused, because it can weaken calculation skills



# Solution Method

Method 2: Gaussian elimination (transform to upper triangular form)

$$\left| \begin{array}{cccc|c} 1 & -1 & -1 & 0 & 0 \\ 0 & 0 & 1 & -1 & -1 \\ 5 & 8 & 0 & 0 & 15 \\ 0 & -8 & 6 & 10 & 0 \end{array} \right| \Leftrightarrow \left| \begin{array}{cccc|c} 1 & -1 & -1 & 0 & 0 \\ 0 & 13 & 5 & 0 & 15 \\ 0 & 0 & 1 & -1 & -1 \\ 0 & -8 & 6 & 10 & 0 \end{array} \right| \Leftrightarrow$$

$$\left| \begin{array}{cccc|c} 1 & -1 & -1 & 0 & 0 \\ 0 & 13 & 5 & 0 & 15 \\ 0 & 0 & 9,0769 & 10 & 9,230 \\ 0 & 0 & 1 & -1 & -1 \end{array} \right| \Leftrightarrow \left| \begin{array}{cccc|c} 1 & -1 & -1 & 0 & 0 \\ 0 & 13 & 5 & 0 & 15 \\ 0 & 0 & 9,0769 & 10 & 9,230 \\ 0 & 0 & 0 & -2,101 & -2,0168 \end{array} \right|$$

$$\Rightarrow I_5 = -2,0168 \div (-2,101) = 0,9597 \text{ A}$$

$$I_3 = (9,23 - 10 \times 0,9597) \div 9,0769 = -0,0404 \text{ A}$$


$$I_2 = (15 - 5 \times (-0,0404)) \div 13 = 1,1694 \text{ A}$$

$$I_1 = 1,1694 + (-0,0404) = 1,1290 \text{ A}$$



# Branch-Current Method

## Example 2.2

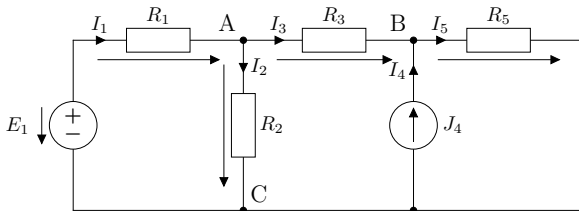

Substitute values:

- $E_1 = 15 \text{ V}; R_1 = 5 \Omega;$
- $R_2 = 8 \Omega; R_3 = 6 \Omega;$
- $J_4 = 1 \text{ A}; R_5 = 10 \Omega.$

### Branch currents

$$I_1 = 1,1290 \text{ A}$$

$$I_2 = 1,1694 \text{ A}$$

$$I_3 = -0,0404 \text{ A}$$

$$I_5 = 0,9597 \text{ A}$$

### Voltages

$$U_1 = R_1 \cdot I_1 = 5 \times 1,1290 = 5,645 \text{ V}$$

$$U_2 = R_2 \cdot I_2 = 8 \times 1,1694 = 9,3552 \text{ V}$$

$$U_3 = R_3 \cdot I_3 = 6 \times -0,0404 = -0,2424 \text{ V}$$

$$U_5 = R_5 \cdot I_5 = 10 \times 0,9597 = 9,597 \text{ V}$$




# Chapter Outline

- 2 Linear Circuits in Steady State with DC Sources
  - Kirchhoff Equation System of a DC Circuit
  - Branch-Current Method
  - Power in DC Circuits



# Power in DC Circuits

## Example 2.2

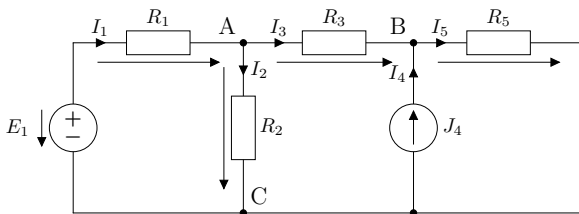

Substitute values:

- $E_1 = 15 \text{ V}; R_1 = 5 \Omega;$
- $R_2 = 8 \Omega; R_3 = 6 \Omega;$
- $J_4 = 1 \text{ A}; R_5 = 10 \Omega.$

Absorbed power on the resistors

- For a purely resistive circuit  $P = U \cdot I = R \cdot I \cdot I = R \cdot I^2$

$$\Rightarrow P_{R_1} = 6,3732 \text{ W}; P_{R_2} = 10,94 \text{ W}; P_{R_3} = 0,00979 \text{ W};$$

$$P_{R_5} = 9,2102 \text{ W} \Rightarrow \sum P(\text{abs}) = 26,5332 \text{ W}$$

Supplied power on the sources


- $P_{E_1}(\text{sup}) = E_1 \cdot I_1 = 16,935 \text{ W}; P_{J_4}(\text{sup}) = J_4 \cdot U_5 = 9,597 \text{ W}$



# Power in DC Circuits

- Dissipative elements (resistors) always absorb energy ( $P_{\text{abs}} > 0$ )
  - Electric-storage elements (capacitors) and magnetic-storage elements (inductors) do not absorb energy; they only exchange energy through charging and discharging
- ⇒ If a circuit has only one source, that source must supply power  
 If there are multiple sources, some may supply power and others may absorb power

## Example 2.3

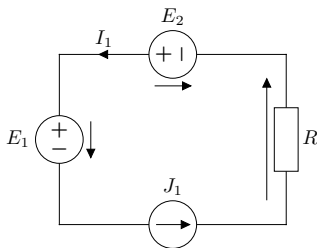

- $E_1 = 15 \text{ V}$ ;  $E_2 = 9 \text{ V}$ ;  
 $R = 5 \Omega$ ;  $J_1 = 1 \text{ A}$
- ⇒ determine the power on the elements



# Course Outline

- 1 Concepts of Kirchhoff Circuit Model
- 2 Linear Circuits in Steady State with DC Sources
- 3 Methods for Solving Linear Steady-State DC Circuits**
- 4 Linear Circuits in Steady State with Sinusoidal Sources
- 5 Methods for Solving Linear Steady-State AC circuits
- 6 Thévenin–Norton Theorem and One-Port Networks
- 7 Mutual Inductance and Solving Magnetically Coupled Circuits
- 8 Two-Port Networks
- 9 Circuits with Multiple Frequencies and Non-Sinusoidal Sources
- 10 Three-Phase Circuits



# Chapter Outline

- 3 Methods for Solving Linear Steady-State DC Circuits
  - Loop Analysis
  - Nodal Analysis
  - Equivalent-Resistance Method
  - Superposition Method



# Methods for Solving Linear Steady-State Circuits

## Branch-current method

- 😊 Easy to understand and easy to set up equations
- 😞 Many unknowns and many equations  $\Rightarrow$  difficult to solve
- $\Rightarrow$  Need to reduce the number of variables to simplify the problem

## Approaches for simplifying the problem

- Introduce intermediate variables to simplify the equation system
  1. Loop Analysis
  2. Nodal Analysis
- Transform the circuit to simplify its structure
  3. Equivalent-resistance method
  4. Superposition method



# Chapter Outline

- 3 Methods for Solving Linear Steady-State DC Circuits
  - Loop Analysis
  - Nodal Analysis
  - Equivalent-Resistance Method
  - Superposition Method



# Loop Analysis

## Variables and equations

- Instead of solving directly for branch currents, introduce “substituted unknowns” as dummy currents flowing in the *fundamental loops*
- ⇒ If the circuit has  $l = b - n + 1$  fundamental loops *that do not contain current sources*, set up  $l$  equations to find  $l$  loop currents
- For each *current source*, a “discharging” loop is needed whose loop current equals the source current ⚠ Don’t “discharge” through another current source
- ⇒ *Independent current source* doesn’t increase the no. of equations
- Then determine each branch current as a combination of loop currents

## Procedure


- Set up  $l$  equations from KVL
- Assign a reference loop current to each fundamental loop
- Determine the “discharging” loop for current sources (if any)



# Loop Analysis
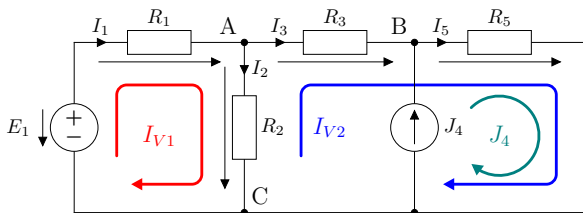
## Example 3.1

- The circuit has 4 branches and 3 nodes  
→ it has  $4 - 3 + 1 = 2$  fundamental loops
- Define 2 loop currents and 1 current-source discharging loop



## Branch-current equations on loops from KVL

### Loop 1

$$R_1 \cdot I_1 + R_2 \cdot I_2 - E_1 = 0$$

### Loop 2

$$-R_2 \cdot I_2 + R_3 \cdot I_3 + R_5 \cdot I_5 = 0$$

## Relation between branch currents and loop currents

- $I_1 = I_{V1}$
- $I_2 = I_{V1} - I_{V2}$
- $I_3 = I_{V2}$
- $I_5 = I_{V2} + J_4$




# Loop Analysis
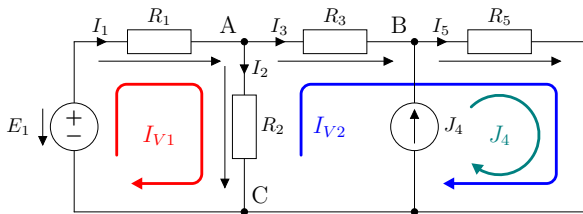
## Example 3.1

Substitute values

- $E_1 = 15 \text{ V}$ ;  $R_1 = 5 \Omega$ ;
- $R_2 = 8 \Omega$ ;  $R_3 = 6 \Omega$ ;
- $J_4 = 1 \text{ A}$ ;  $R_5 = 10 \Omega$ .



⇒ Loop-current equation system

$$\begin{aligned} (R_1 + R_2) \cdot I_{V1} - R_2 \cdot I_{V2} &= E_1 \\ -R_2 \cdot I_{V1} + (R_2 + R_3 + R_5) \cdot I_{V2} &= -R_5 \cdot J_4 \end{aligned}$$

Substitute values → solve equations → loop currents → branch currents

$$\begin{aligned} 13 \cdot I_{V1} - 8 \cdot I_{V2} &= 15 \\ -8 \cdot I_{V1} + 24 \cdot I_{V2} &= -10 \end{aligned} \quad \Rightarrow \quad \begin{aligned} I_{V1} &= \text{A} \\ I_{V2} &= \text{A} \end{aligned} \quad \Rightarrow \quad \begin{aligned} I_1 &= \text{A}; I_2 = \text{A}; \\ I_3 &= \text{A}; I_5 = \text{A}. \end{aligned}$$



# Solution Method

## Matrix form of the equation system

$$\begin{bmatrix} 13 & -8 \\ -8 & 24 \end{bmatrix} \begin{bmatrix} I_{V1} \\ I_{V2} \end{bmatrix} = \begin{bmatrix} 15 \\ -10 \end{bmatrix}$$

- Method 1: Use MATLAB or Scilab (for cross-checking)
- Method 2: Elementary transformations or Gaussian elimination

## Method 3: Use Cramer's rule

Equation system  $A \cdot x = b$

Solution:

$$\begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \begin{bmatrix} b_1 \\ b_2 \end{bmatrix} \quad x_j = \frac{\det A_j}{\det A}; \quad A_j: \text{replace } j^{\text{th}} \text{ column of matrix } A \text{ by vector } b$$

With  $\det A = a_{11} \cdot a_{22} - a_{12} \cdot a_{21}$



# Solution Method

Matrix form of the equation system

$$\begin{bmatrix} 13 & -8 \\ -8 & 24 \end{bmatrix} \begin{bmatrix} I_{V1} \\ I_{V2} \end{bmatrix} = \begin{bmatrix} 15 \\ -10 \end{bmatrix}$$

Apply Cramer's rule


$$I_{V1} = \frac{\begin{vmatrix} 15 & -8 \\ -10 & 24 \end{vmatrix}}{\begin{vmatrix} 13 & -8 \\ -8 & 24 \end{vmatrix}} = \frac{15 \cdot 24 - ((-8) \cdot (-10))}{13 \cdot 24 - ((-8) \cdot (-8))} = 1,129 \text{ A}$$

$$I_{V2} = \frac{\begin{vmatrix} 13 & 15 \\ -8 & -10 \end{vmatrix}}{\begin{vmatrix} 13 & -8 \\ -8 & 24 \end{vmatrix}} = \frac{13 \cdot (-10) - (15 \cdot (-8))}{13 \cdot 24 - ((-8) \cdot (-8))} = -0.0403 \text{ A}$$



# Loop Analysis

## Example 3.2

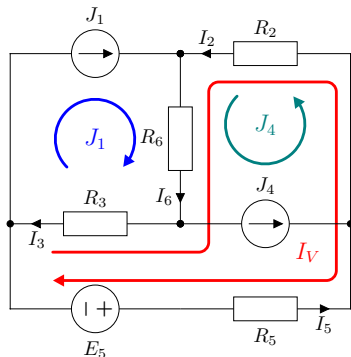

$J_1 = 1 \text{ A}$ ;  $R_2 = 5 \Omega$ ;  $R_3 = 6 \Omega$ ;  $J_4 = 1,5 \text{ A}$ ;  
 $R_5 = 4 \Omega$ ;  $E_5 = 12 \text{ V}$ ;  $R_6 = 8 \Omega$ .

- Number of unknown branches: 4
- Number of nodes: 4
- $\Rightarrow$  Number of fundamental loops:  
 $4 - 4 + 1 = 1$
- Number of independent current sources: 2
- $\Rightarrow$  Number of discharging loops: 2

- Branch-current equation on the fundamental loop:

$$-R_2 \cdot I_2 - R_3 \cdot I_3 - R_5 \cdot I_5 - R_6 \cdot I_6 + E_5 = 0$$


- Replace branch-current variables by loop-current variables:

$$R_2 \cdot (-I_V + J_4) + R_3 \cdot (-I_V + J_1) - R_5 \cdot I_V + R_6 \cdot (-I_V + J_1 + J_4) = E_5$$



# Loop Analysis

## Example 3.2

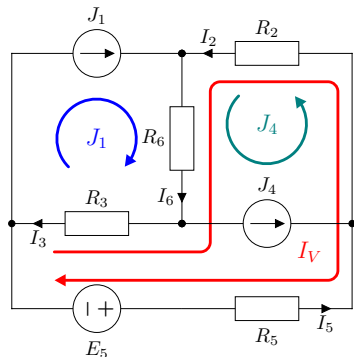

$$J_1 = 1 \text{ A}; R_2 = 5 \Omega; R_3 = 6 \Omega; J_4 = 1,5 \text{ A}; \\ R_5 = 4 \Omega; E_5 = 12 \text{ V}; R_6 = 8 \Omega$$

- Simplify the loop-current equation  

$$(R_2 + R_3 + R_5 + R_6) \cdot I_V = \\ (R_3 + R_6) \cdot J_1 + (R_2 + R_6) \cdot J_4 - E_5$$
- Substitute values to solve for the loop-current unknown  

$$23 \cdot I_V = 21,5 \Rightarrow I_V = 0,9348 \text{ A}$$
- From there, determine the branch currents, voltages, and power

- ⚠ Some “quick calculation” shortcuts can be found in the references
- ⚠ However, such shortcuts are easy to confuse in unusual cases  
 $\Rightarrow$  regular method starting from Kirchhoff equations is safer.



# Chapter Outline

## 3 Methods for Solving Linear Steady-State DC Circuits

- Loop Analysis
- Nodal Analysis
- Equivalent-Resistance Method
- Superposition Method



# Nodal Analysis

## Variables and equations

- The substituted variables are the node potentials of the circuit
- ⇒ If the circuit has  $n$  *essential* nodes, set up  $n - 1$  equations to find  $n - 1$  node potentials
- Then determine branch currents from the node potentials


## Procedure

- Choose any node as the *ground* point with zero potential
  - Set up  $n - 1$  equations from KCL
- 
- This is the fundamental method for solving circuits containing op-amps

# Nodal Analysis
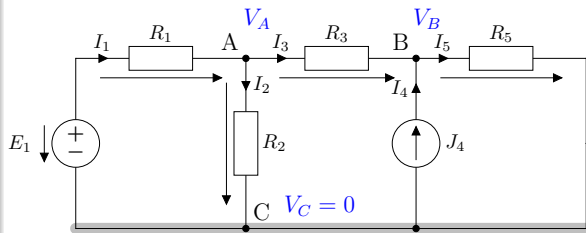
## Example 3.3

- The circuit has 3 nodes  $\rightarrow$  it has  $3 - 1 = 2$  KCL equations
- Choose point C as *ground*
- The unknowns are the potentials  $V_A$  and  $V_B$



## KCL equation system

- Node A:  $I_1 - I_2 - I_3 = 0$
- Node B:  $I_3 + J_4 - I_5 = 0$

$\Rightarrow$  Node-potential equation system

- $$\frac{-V_A + E_1}{R_1} - \frac{V_A}{R_2} - \frac{V_A - V_B}{R_3} = 0$$
- $$\frac{V_A - V_B}{R_3} - \frac{V_B}{R_5} = -J_4$$




# Nodal Analysis
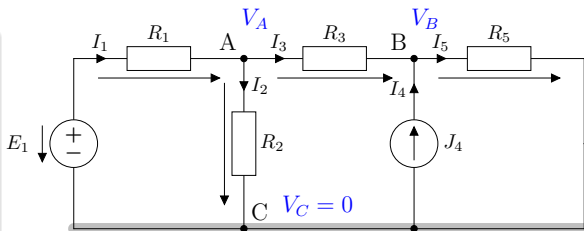
## Example 3.3

Substitute values

- $E_1 = 15 \text{ V}$ ;  $R_1 = 5 \Omega$ ;
- $R_2 = 8 \Omega$ ;  $R_3 = 6 \Omega$ ;
- $J_4 = 1 \text{ A}$ ;  $R_5 = 10 \Omega$ .



Simplified node-potential equation system

$$\left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) \cdot V_A - \frac{1}{R_3} \cdot V_B = \frac{E_1}{R_1}$$

$$\frac{1}{R_3} \cdot V_A - \left( \frac{1}{R_3} + \frac{1}{R_5} \right) \cdot V_B = -J_4$$

Substitute values


$$\begin{aligned} 0,4917 \cdot V_A - 0,1667 \cdot V_B &= 3 \\ 0,1667 \cdot V_A - 0,2667 \cdot V_B &= -1 \\ \Rightarrow V_A &= 9,3548 \text{ V} \\ V_B &= 9,5967 \text{ V} \end{aligned}$$



# Nodal Analysis
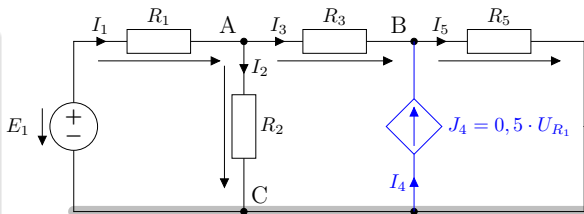
## Example 3.4: Case with a dependent source

- $E_1 = 15 \text{ V}; R_1 = 5 \Omega;$
- $R_2 = 8 \Omega; R_3 = 6 \Omega;$
- $R_5 = 10 \Omega.$



⇒ Continue converting the dependent-source value into independent branch currents

## KCL equation system

- Node A:  $I_1 - I_2 - I_3 = 0$
- Node B:  $I_3 + J_4 - I_5 = 0$   
 $\Leftrightarrow I_3 + 2,5 \cdot I_1 - I_5 = 0$

## ⇒ Node-potential equation system


- $\frac{-V_A + E_1}{R_1} - \frac{V_A}{R_2} - \frac{V_A - V_B}{R_3} = 0$
- $\frac{V_A - V_B}{R_3} + 2,5 \cdot \frac{-V_A + E_1}{R_1} - \frac{V_B}{R_5} = 0$



# Nodal Analysis
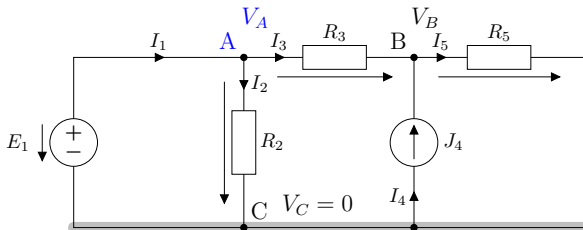
## Example 3.5: Supernode case

This is the case where circuit nodes are connected by a voltage source, with no “buffer” resistor




- ✗ Solve as in Example 3.3 and then set  $R_1 = 0$   
 → indeterminate equation system → cannot be solved
- ✓ Potential  $V_A = E_1$  → only one equation is needed to find potential  $V_B$   
 → A supernode reduces the number of unknowns



# Nodal Analysis
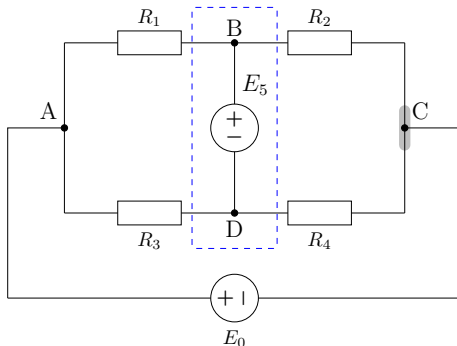
## Example 3.6: Circuit with multiple supernodes




- Choose one node as the reference, e.g., node C  $\Rightarrow V_A = E_0$
- Potential difference BD:  $V_B - V_D = E_5$
- Apply the *extended KCL* to the closed region BD



# Nodal Analysis

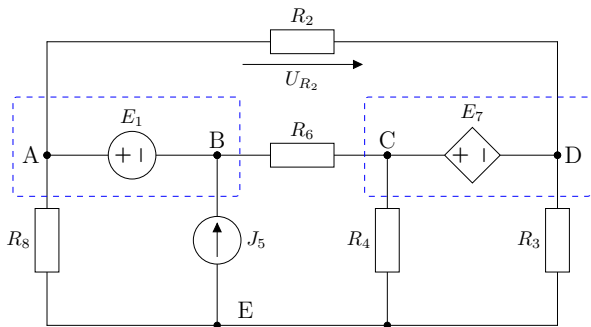Example 3.7: Circuit with multiple supernodes and a dependent source



$$\begin{aligned}
 E_1 &= 20 \text{ V}; R_2 = 3 \Omega; \\
 R_3 &= 1 \Omega; R_4 = 4 \Omega; \\
 J_5 &= 10 \text{ A}; R_6 = 6 \Omega; \\
 E_7 &= 3 \cdot U_{R_2}; R_8 = 2 \Omega.
 \end{aligned}$$




# Chapter Outline

- 3 Methods for Solving Linear Steady-State DC Circuits
  - Loop Analysis
  - Nodal Analysis
  - Equivalent-Resistance Method
  - Superposition Method



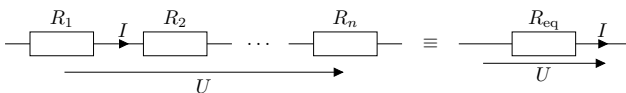
# Equivalent-Resistance Method

Series circuit: equivalent resistance equals total resistance



$$R_{\text{eq}} = R_1 + R_2 + \dots + R_n$$

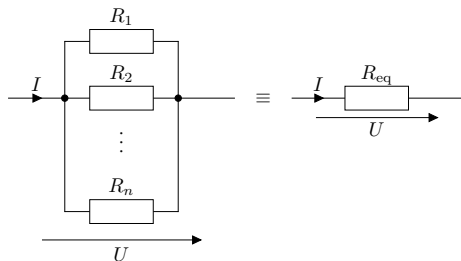Parallel circuit: equivalent conductance equals total conductance




$$G_{\text{eq}} = G_1 + G_2 + \dots + G_n$$

$$\Leftrightarrow \frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$



# Equivalent-Resistance Method


## Voltage-division formula

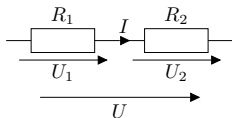

- General formula:  $U_k = \frac{R_k}{\sum_{i=1}^n R_i} \cdot U$
- Two-element case (common)  

$$U_1 = \frac{R_1}{R_1 + R_2} \cdot U; \quad U_2 = \frac{R_2}{R_1 + R_2} \cdot U$$

## Current-division formula

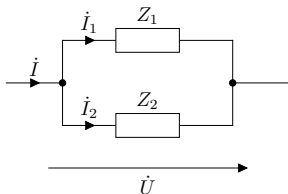


- General formula:  $I_k = \frac{G_k}{\sum_{i=1}^n G_i} \cdot I$
- Two-element case (common)  

$$I_1 = \frac{R_2}{R_1 + R_2} \cdot I; \quad I_2 = \frac{R_1}{R_1 + R_2} \cdot I$$



# Equivalent-Resistance Method


## Wye–delta transformation

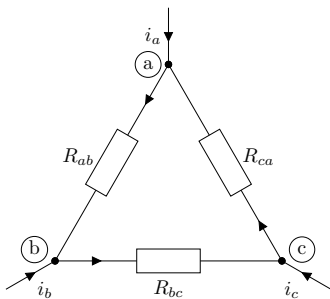

$$R_{ab} = R_a + R_b + \frac{R_a \cdot R_b}{R_c}$$

$$Y \rightarrow \Delta : R_{bc} = R_b + R_c + \frac{R_b \cdot R_c}{R_a}$$
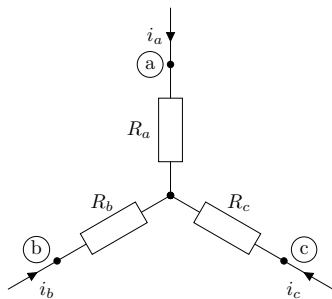
$$R_{ca} = R_c + R_a + \frac{R_c \cdot R_a}{R_b}$$



$$R_a = \frac{R_{ca} \cdot R_{ab}}{R_{ab} + R_{bc} + R_{ca}}$$

$$\Delta \rightarrow Y : R_b = \frac{R_{ab} \cdot R_{bc}}{R_{ab} + R_{bc} + R_{ca}}$$

$$R_c = \frac{R_{bc} \cdot R_{ca}}{R_{ab} + R_{bc} + R_{ca}}$$



# Chapter Outline

- 3 Methods for Solving Linear Steady-State DC Circuits
  - Loop Analysis
  - Nodal Analysis
  - Equivalent-Resistance Method
  - Superposition Method



# Superposition Method

- A linear system satisfies the *superposition principle*
- ⇒ The superposition principle can be used to simplify the analysis of linear circuits

## Superposition in linear circuits with multiple sources

- Currents and voltages in the circuit are the *algebraic sum* of the currents and voltages produced by each *independent source* while the other *independent sources* are “turned off”


## How to “turn off” (or “suppress”) a source

- Independent voltage source → Short circuit
- Independent current source → Open circuit
- Do NOT turn off dependent sources



# Superposition Method

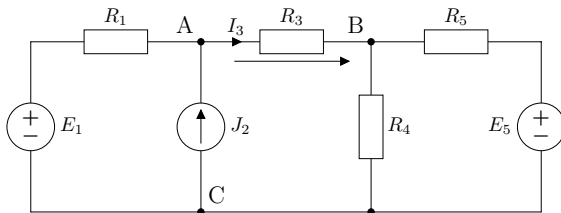Example 3.8: Determine current  $I_3$  using superposition





Solution

- $I_3 = I_{31} + I_{32} + I_{35}$
- $I_{31}$  is the current through  $R_3$  when only  $E_1$  acts, with  $J_2$  and  $E_5$  off
- $I_{32}$  is the current through  $R_3$  when only  $J_2$  acts, with  $E_1$  and  $E_5$  off
- $I_{35}$  is the current through  $R_3$  when only  $E_5$  acts, with  $J_2$  and  $E_1$  off



# Superposition Method

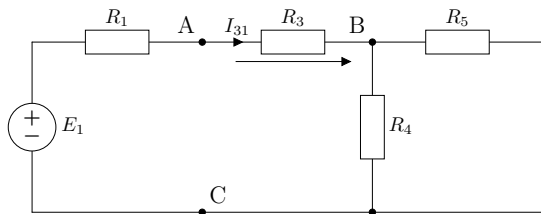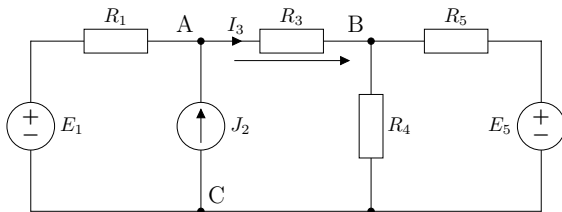Example 3.8: Determine current  $I_3$  using superposition



Component  $I_{31}$



$$R_{eq} = R_1 + R_3 + \frac{R_4 \cdot R_5}{R_4 + R_5}$$

$$I_{31} = \frac{E_1}{R_{eq}}$$



# Superposition Method

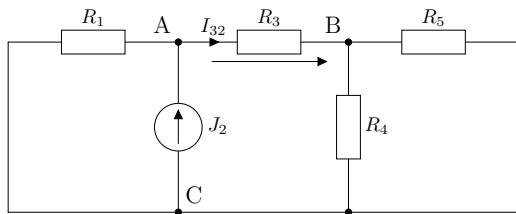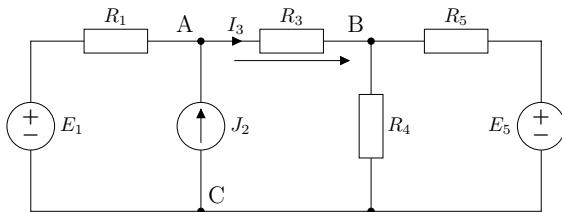Example 3.8: Determine current  $I_3$  using superposition



Component  $I_{32}$



$$R_{345} = R_3 + \frac{R_4 \cdot R_5}{R_4 + R_5}$$

$$I_{32} = \frac{R_1}{R_1 + R_{345}} \cdot J_2$$



# Superposition Method

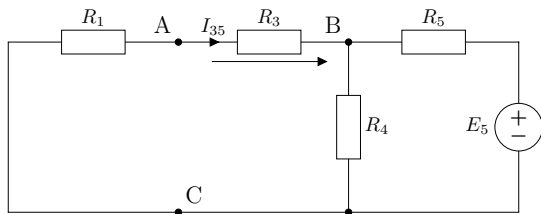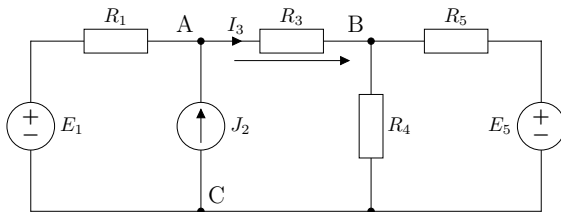Example 3.8: Determine current  $I_3$  using superposition



Component  $I_{35}$


$$R_{eq} = R_5 + \frac{R_4 \cdot (R_1 + R_3)}{R_1 + R_3 + R_4}$$

$$I_{32} = -\frac{E_5}{R_{eq}} \cdot \frac{R_4}{R_1 + R_3 + R_4}$$



# Superposition Method
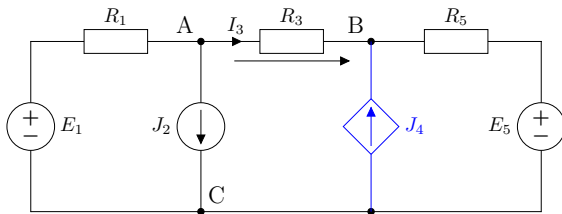
## Example 3.9: Superposition in a circuit with a dependent source



## Solution



- $I_3 = I_{31} + I_{32}$
- $I_{31}$  is the current through  $R_3$  when only  $E_1$  acts and  $J_2$  off
- $I_{32}$  is the current through  $R_3$  when only  $J_2$  acts and  $E_1$  off

⚠ Do not turn off the dependent source  $J_4$



# Superposition Method
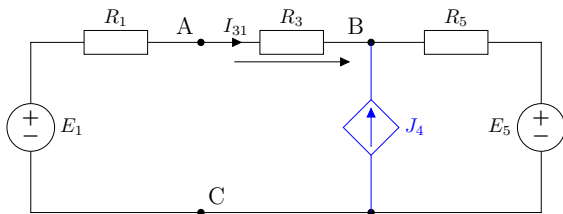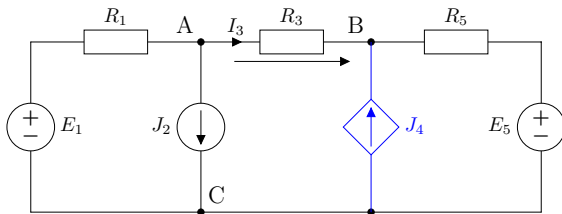
## Example 3.9: Superposition in a circuit with a dependent source





### Component $I_{31}$

- Open-circuit source  $J_2$
- Find  $I_{31}$  using a circuit-solving method (for example, nodal analysis)



# Superposition Method
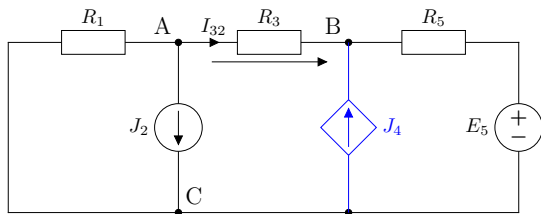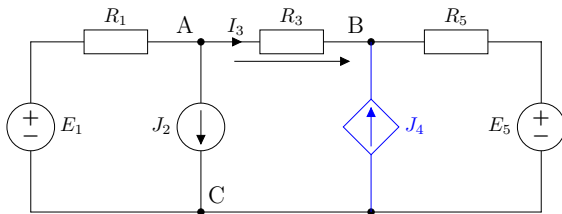
## Example 3.9: Superposition in a circuit with a dependent source



### Component $I_{32}$

- Short-circuit source  $E_1$
- Find  $I_{32}$  using a circuit-solving method (for example, loop analysis)



# Course Outline

- 1 Concepts of Kirchhoff Circuit Model
- 2 Linear Circuits in Steady State with DC Sources
- 3 Methods for Solving Linear Steady-State DC Circuits
- 4 Linear Circuits in Steady State with Sinusoidal Sources**
- 5 Methods for Solving Linear Steady-State AC circuits
- 6 Thévenin–Norton Theorem and One-Port Networks
- 7 Mutual Inductance and Solving Magnetically Coupled Circuits
- 8 Two-Port Networks
- 9 Circuits with Multiple Frequencies and Non-Sinusoidal Sources
- 10 Three-Phase Circuits



# Chapter Outline

- ④ Linear Circuits in Steady State with Sinusoidal Sources
  - Sinusoidal AC Quantities
  - Characteristic Equations of AC Circuit Elements
  - Kirchhoff Equations in AC Circuits
  - Using Complex Numbers to determine Sinusoidal Quantities
  - Phasor Representations of Circuit Elements
  - Phasor Representation of a Circuit and Kirchhoff Equation System



# Chapter Outline

- ④ Linear Circuits in Steady State with Sinusoidal Sources
  - Sinusoidal AC Quantities
  - Characteristic Equations of AC Circuit Elements
  - Kirchhoff Equations in AC Circuits
  - Using Complex Numbers to determine Sinusoidal Quantities
  - Phasor Representations of Circuit Elements
  - Phasor Representation of a Circuit and Kirchhoff Equation System



# Sinusoidal AC Quantities

- AC quantity has instantaneous value whose sign changes over time
- If the change repeats with *period*  $T$  (*frequency*  $f = 1/T$ ), it is called a *periodic* quantity
- If the periodic function is **sin** or **cos**, it is a *sinusoidal* function


$$u(t) = U_0 \sin(\omega t + \varphi) \text{ V}$$

$$i(t) = I_0 \sin(\omega t + \theta) \text{ A}$$

$U_0, I_0$ : amplitude;  $\varphi, \theta$ : phase angle;

$\omega$ : angular frequency;

$$\omega = 2\pi f = 2\pi/T$$

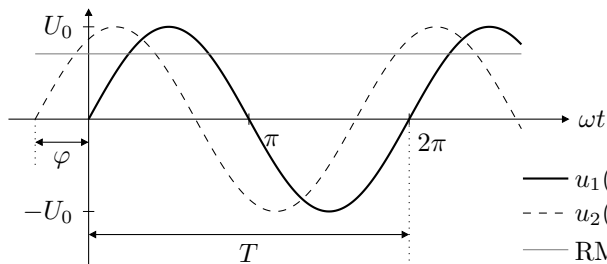

—  $u_1(t) = U_0 \sin(\omega t)$

- - -  $u_2(t) = U_0 \sin(\omega t + \varphi)$

— RMS value  $U_0/\sqrt{2}$




# Chapter Outline

- 4 Linear Circuits in Steady State with Sinusoidal Sources
  - Sinusoidal AC Quantities
  - Characteristic Equations of AC Circuit Elements
  - Kirchhoff Equations in AC Circuits
  - Using Complex Numbers to determine Sinusoidal Quantities
  - Phasor Representations of Circuit Elements
  - Phasor Representation of a Circuit and Kirchhoff Equation System




# Characteristic Equation of AC circuit Element

## Voltage source

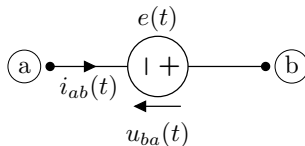

- $u_{ba}(t) = e(t) = E_0 \sin(\omega t + \varphi), \forall i_{ab}(t), \forall t$

## Current source

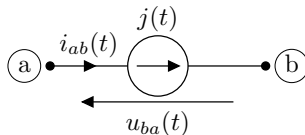


- $i_{ab}(t) = j(t) = J_0 \sin(\omega t + \theta), \forall u_{ba}(t), \forall t$



# Characteristic Equation of AC circuit Element

## Resistor

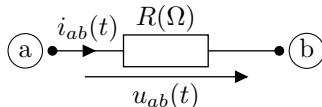

- $i_{ab}(t) = I_0 \sin(\omega t + \theta)$

$$\Rightarrow u_{ab}(t) = R \cdot i_{ab}(t) = R \cdot I_0 \sin(\omega t + \theta)$$

## Conductance

- $u_{ab}(t) = U_0 \sin(\omega t + \varphi)$


$$\Rightarrow i_{ab}(t) = G \cdot u_{ab}(t) = G \cdot U_0 \sin(\omega t + \varphi)$$

$\Rightarrow$  Current and voltage on a resistor (and conductance) have the *same frequency* and are *in phase*



# Characteristic Equation of AC circuit Element

## Capacitance (capacitor)

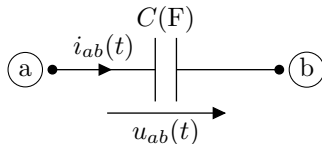

- $u_{ab}(t) = U_0 \sin(\omega t + \varphi)$

$$\Rightarrow i_{ab}(t) = C \cdot \frac{du_{ab}(t)}{dt} = C \cdot \frac{d}{dt} (U_0 \sin(\omega t + \varphi))$$

$$= C \cdot U_0 \cdot \cos(\omega t + \varphi) \cdot \omega = \omega C \cdot U_0 \sin(\omega t + \varphi + 90^\circ)$$


$\Rightarrow$  Current and voltage on a capacitor have the *same frequency* and are *in quadrature*

- Capacitor current *leads* capacitor voltage by  $90^\circ$
- Capacitor voltage *lags* capacitor current by  $90^\circ$



# Characteristic Equation of AC circuit Element

## Inductance (inductor)

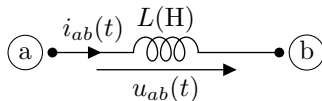

- $i_{ab}(t) = I_0 \sin(\omega t + \theta)$

$$\Rightarrow u_{ab}(t) = L \cdot \frac{di_{ab}(t)}{dt} = L \cdot \frac{d}{dt} (I_0 \sin(\omega t + \theta))$$

$$= L \cdot I_0 \cdot \cos(\omega t + \theta) \cdot \omega = \omega L \cdot I_0 \sin(\omega t + \theta + 90^\circ)$$


$\Rightarrow$  Current and voltage on an inductor have the *same frequency* and are *in quadrature*

- Inductor voltage *leads* current by  $90^\circ$
- Inductor current *lags* voltage by  $90^\circ$



# Characteristic Equation of AC circuit Element

## Mutual inductance between coils

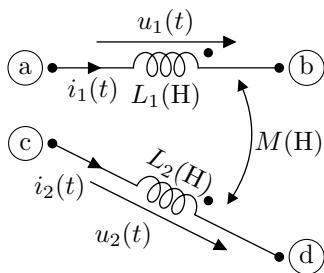

$$\bullet i_1(t) = I_1 \sin(\omega t + \theta_1)$$

$$\bullet i_2(t) = I_2 \sin(\omega t + \theta_2)$$

$$\Rightarrow u_1(t) = L_1 \cdot \frac{di_1(t)}{dt} \pm M \cdot \frac{di_2(t)}{dt}$$

$$u_2(t) = L_2 \cdot \frac{di_2(t)}{dt} \pm M \cdot \frac{di_1(t)}{dt}$$

$$\Rightarrow u_1(t) = \omega L_1 \cdot I_1 \sin(\omega t + \theta_1 + 90^\circ) \pm \omega M \cdot I_2 \sin(\omega t + \theta_2 + 90^\circ)$$

$$u_2(t) = \omega L_2 \cdot I_2 \sin(\omega t + \theta_2 + 90^\circ) \pm \omega M \cdot I_1 \sin(\omega t + \theta_1 + 90^\circ)$$


$\Rightarrow$  Currents and voltages on magnetically coupled coils have the *same frequency* and are *phase shifted* relative to one another

- The phase shift depends on the coupling sign and on  $\theta_1$  and  $\theta_2$




# Characteristic Equation of AC circuit Element

## Voltage-controlled voltage source

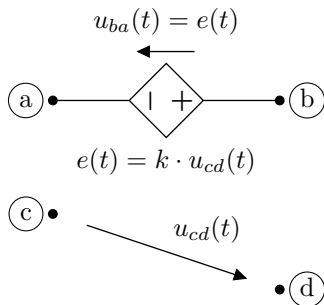

$\Rightarrow e(t)$  is a sinusoidal function with the *same frequency* and *same phase* as  $u_{cd}(t)$

## Current-controlled voltage source

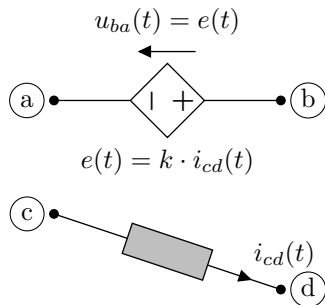


$\Rightarrow e(t)$  is a sinusoidal function with the *same frequency* and *same phase* as  $i_{cd}(t)$




# Characteristic Equation of AC circuit Element

## Voltage-controlled current source

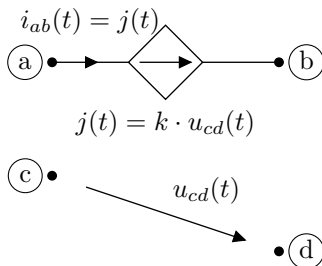

$\Rightarrow j(t)$  is a sinusoidal function  
 with the *same frequency*  
 and *same phase* as  $u_{cd}(t)$

## Current-controlled current source

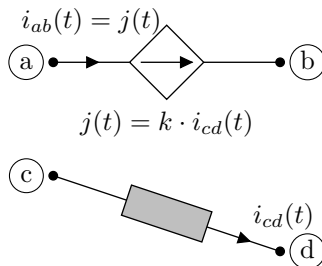

$\Rightarrow j(t)$  is a sinusoidal function  
 with the *same frequency*  
 and *same phase* as  $i_{cd}(t)$




# Characteristic Equation of AC circuit Element
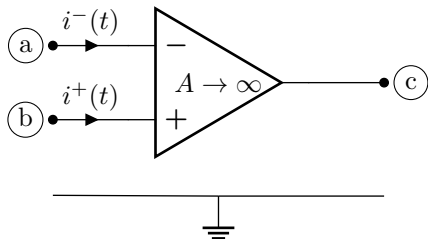
## Operational amplifier (op-amp)

- All quantities in the circuit are sinusoidal functions with the *same frequency*
- The *phase angles* between quantities depend on the circuit structure and element values
- The characteristic relation keeps its general form

$$\begin{cases} i^+ \approx 0; i^- \approx 0 \\ v_c(t) = A(v_b(t) - v_a(t)) \end{cases}$$



## Ideal op-amp

- Gain  $A = \infty$ 

$$\begin{cases} i^+ = 0; i^- = 0 \\ v_a(t) = v_b(t) \end{cases}$$



# Chapter Outline


- 4 Linear Circuits in Steady State with Sinusoidal Sources
  - Sinusoidal AC Quantities
  - Characteristic Equations of AC Circuit Elements
  - **Kirchhoff Equations in AC Circuits**
  - Using Complex Numbers to determine Sinusoidal Quantities
  - Phasor Representations of Circuit Elements
  - Phasor Representation of a Circuit and Kirchhoff Equation System



# Kirchhoff Equations in AC circuits

- KCL and KVL are stated generally for all forms of current and voltage
- ⇒ KCL and KVL keep the forms  $\sum i(t) = 0$  at a node and  $\sum u(t) = 0$  around a loop, with  $u(t)$  and  $i(t)$  as sinusoidal functions
- ⚠ However, direct calculations with sinusoidal functions are not simple

Example 4.1: Determine voltage  $u(t)$

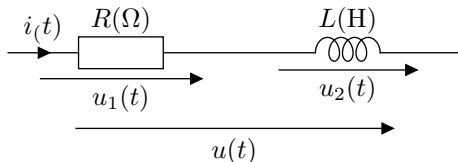


$$i(t) = 2 \sin(5t + 20^\circ)$$

$$R = 6 \Omega; L = 0,5 \text{ H}$$



# Kirchhoff Equations in AC circuits

Example 4.1: Determine voltage  $u(t)$

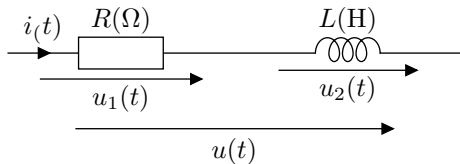

$$i(t) = 2 \sin(5t + 20^\circ)$$

$$R = 6 \Omega; L = 0,5 \text{ H}$$

- KVL equation:  $u(t) = u_1(t) + u_2(t)$
- $u_1(t) = R \cdot i(t) = 12 \sin(5t + 20^\circ)$
- $u_2(t) = \omega L \cdot I_m \sin(\omega t + \varphi + 90^\circ) = 5 \cdot 0,5 \cdot 2 \sin(5t + 110^\circ)$

$$\begin{aligned} \Rightarrow u(t) &= 12 \sin(5t + 20^\circ) + 5 \sin(5t + 110^\circ) \\ &= \sqrt{12^2 + 5^2} \left( \frac{12}{\sqrt{12^2 + 5^2}} \sin(5t + 20^\circ) + \frac{5}{\sqrt{12^2 + 5^2}} \cos(5t + 20^\circ) \right) \\ &= \sqrt{12^2 + 5^2} \sin(5t + 20^\circ + 22,62^\circ) = 13 \sin(5t + 42,62^\circ) \text{ V} \end{aligned}$$



# Chapter Outline



- 4 Linear Circuits in Steady State with Sinusoidal Sources
  - Sinusoidal AC Quantities
  - Characteristic Equations of AC Circuit Elements
  - Kirchhoff Equations in AC Circuits
  - Using Complex Numbers to determine Sinusoidal Quantities
  - Phasor Representations of Circuit Elements
  - Phasor Representation of a Circuit and Kirchhoff Equation System



# Idea

- Calculations with trigonometric functions are difficult  $\rightarrow$  convert to a form that is easier to determine
  - Consider the AC quantity  $f(t) = F_0 \sin(\omega t + \varphi)$
  - If all current and voltage quantities are *sinusoidal functions*
- $\Rightarrow$  Only 3 parameters,  $F_0$ ,  $\omega$ , and  $\varphi$ , are **sufficient to represent**  $f(t)$
- If all sources in a linear circuit have the *same frequency* and considering that electrical engineering emphasizes the *RMS value*
- $\Rightarrow$  Only 2 parameters,  $F_0/\sqrt{2}$  and  $\varphi$ , are **sufficient to represent**  $f(t)$
- $\Rightarrow$  We need **a vector** with magnitude  $F_0/\sqrt{2}$  and angle  $\varphi$

---

In the language of linear algebra, the *space* of same-frequency sinusoidal quantities in a circuit and the *space* of vectors of RMS values and phase angles are two *isomorphic* spaces.





# Phasor Concept

- Revisit Example 4.1

$$i(t) = 2 \sin(5t + 20^\circ)$$

$$R = 6 \Omega; L = 0,5 \text{ H}$$

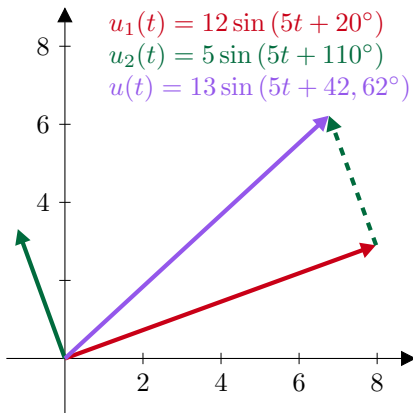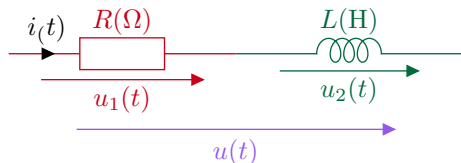

- Geometric vector operations are still inconvenient for complex circuits

$\Rightarrow$  use *complex numbers* (Steinmetz, 1893)




# Review of Complex Numbers

- Complex numbers extend the set of real numbers by adding an *imaginary component*

$$x = a + j \cdot b$$

where  $(a,b)$  is a pair of real numbers and the imaginary operator is  $j = \sqrt{-1}$

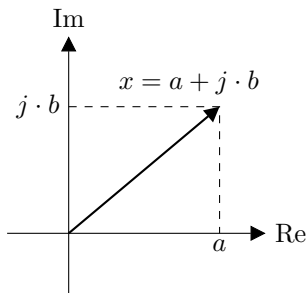- A complex number has 2 components  $\rightarrow$  it can be represented on the *complex plane* with the *real axis* Re and *imaginary axis* Im



$$a = \text{Re}(x)$$

$$b = \text{Im}(x)$$




# Review of Complex Numbers

- As a vector on the complex plane  $\rightarrow$  it can be written in terms of *modulus* and *angle*

$$x = r \cdot e^{j\varphi}$$

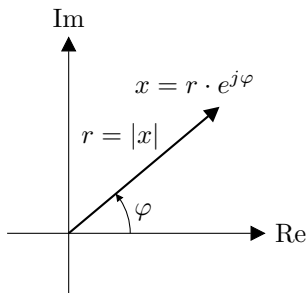- Modulus  $r \geq 0$
- By convention, the positive direction and the value of  $\varphi$  are counterclockwise from the Re axis
- Conventional range of  $\varphi$ :  $[-180^\circ, 180^\circ]$



$$r = |x| = \sqrt{a^2 + b^2}$$

$$\varphi = \arctan\left(\frac{b}{a}\right)$$

- Euler's formula

$$e^{j\varphi} = \cos \varphi + j \cdot \sin \varphi$$



# Phasor Representation of a Sinusoidal Quantity

## Phasor concept

- Let  $\mathcal{P}$  be the **mapping** from the space of *same-frequency* sinusoidal functions in the **time domain** to the phasor space in the **complex domain**

$\Rightarrow$  The **phasor** of the quantity  $f(t) = F_0 \sin(\omega t + \varphi)$  is

$$\dot{F} = \mathcal{P}(f(t)) = \frac{F_0}{\sqrt{2}} e^{j\varphi} = \frac{F_0}{\sqrt{2}} \angle \varphi$$

$\triangle$  Some phasor definitions use **amplitude** and/or the **cosine function**

## Linearity of the phasor mapping

- Given a function  $f(t) = a_1 \cdot f_1(t) + a_2 \cdot f_2(t) + \dots + a_N \cdot f_N(t)$

$$\begin{aligned} \Rightarrow \dot{F} &= \mathcal{P}(f(t)) = a_1 \cdot \mathcal{P}(f_1(t)) + a_2 \cdot \mathcal{P}(f_2(t)) + \dots + a_N \cdot \mathcal{P}(f_N(t)) \\ &= a_1 \cdot \dot{F}_1 + a_2 \cdot \dot{F}_2 + \dots + a_N \cdot \dot{F}_N \end{aligned}$$



# Phasor Representation of a Sinusoidal Quantity

## Phasor of differentiation

- Given  $f(t) = F_0 \sin(\omega t + \varphi)$

$$\Rightarrow \frac{d}{dt} f(t) = \omega \cdot F_0 \sin(\omega t + \varphi + 90^\circ)$$

$\Rightarrow$  Phasor of the derivative

$$\begin{aligned} \mathcal{P} \left( \frac{d}{dt} f(t) \right) &= \mathcal{P} (\omega \cdot F_0 \sin(\omega t + \varphi + 90^\circ)) = \frac{\omega \cdot F_0}{\sqrt{2}} \angle \varphi + 90^\circ \\ &= \frac{\omega \cdot F_0}{\sqrt{2}} e^{j(\varphi + 90^\circ)} = j\omega \frac{F_0}{\sqrt{2}} e^{j\varphi} = j\omega \frac{F_0}{\sqrt{2}} \angle \varphi \\ &= j\omega \cdot \mathcal{P}(f(t)) \end{aligned}$$

$\Rightarrow$  The *phasor of the derivative* equals the phasor of the function multiplied by  $j\omega$



# Phasor Representation of a Sinusoidal Quantity

## Phasor of integration

- Given  $f(t) = F_0 \sin(\omega t + \varphi)$

$$\Rightarrow \int f(t) dt = \frac{-1}{\omega} F_0 \sin(\omega t + \varphi + 90^\circ)$$

$\Rightarrow$  Phasor of the integral

$$\begin{aligned} \mathcal{P} \left( \int f(t) dt \right) &= \mathcal{P} \left( \frac{-1}{\omega} F_0 \sin(\omega t + \varphi + 90^\circ) \right) = \frac{-F_0}{\omega \sqrt{2}} \angle \varphi + 90^\circ \\ &= \frac{-F_0}{\omega \sqrt{2}} e^{j(\varphi + 90^\circ)} = \frac{-j}{\omega} \cdot \frac{F_0}{\sqrt{2}} e^{j\varphi} = \frac{-j}{\omega} \cdot \frac{F_0}{\sqrt{2}} \angle \varphi \\ &= \frac{1}{j\omega} \cdot \mathcal{P}(f(t)) \end{aligned}$$

$\Rightarrow$  The *phasor of the integral* equals the phasor of the function divided by  $j\omega$



# Using Phasors to determine Sinusoidal Quantities

## Example 4.2

- Given the currents  $i_1(t) = 2 \sin(5t + 20^\circ) \text{ A}$ ;  
 $i_2(t) = 3 \sin(5t + 60^\circ) \text{ A}$ ;  $i_3(t) = 5 \sin(5t - 15^\circ) \text{ A}$   
determine  $i_4(t) = i_1(t) + i_2(t) + i_3(t)$

- Phasor method

$$\begin{aligned}\dot{I}_4 &= \dot{I}_1 + \dot{I}_2 + \dot{I}_3 \\ &= \frac{2}{\sqrt{2}} \angle 20^\circ + \frac{3}{\sqrt{2}} \angle 60^\circ + \frac{5}{\sqrt{2}} \angle -15^\circ \\ &= 5,972 \angle 13,61^\circ \text{ A}\end{aligned}$$

$$\Rightarrow i_4(t) = 5,972\sqrt{2} \sin(5t + 13,61^\circ) \text{ A}$$




# Chapter Outline

- 4 Linear Circuits in Steady State with Sinusoidal Sources
  - Sinusoidal AC Quantities
  - Characteristic Equations of AC Circuit Elements
  - Kirchhoff Equations in AC Circuits
  - Using Complex Numbers to determine Sinusoidal Quantities
  - **Phasor Representations of Circuit Elements**
  - Phasor Representation of a Circuit and Kirchhoff Equation System




# Independent Voltage Source
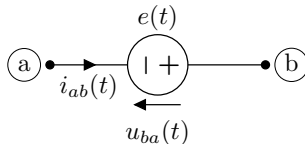
## Independent voltage source in the time domain



$$u_{ba}(t) = e(t) = E_0 \sin(\omega t + \varphi), \forall i_{ab}(t), \forall t$$
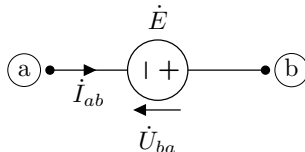
## Phasor of an independent voltage source




$$\dot{U}_{ba} = \dot{E}, \forall \dot{I}_{ab}$$




# Independent Current Source
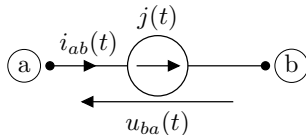
## Independent current source in the time domain



$$i_{ab}(t) = j(t) = J_0 \sin(\omega t + \theta), \forall u_{ba}(t), \forall t$$
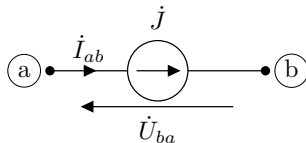
## Phasor of an independent current source




$$I_{ab} = J, \forall U_{ba}$$




# Resistor
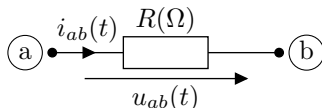
## Resistor (and conductance) in the time domain



$$u_{ab}(t) = R \cdot i_{ab}(t); \quad i_{ab}(t) = G \cdot u_{ab}(t)$$
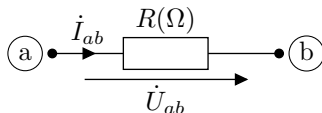
## Phasor representation of a resistor (and conductance)




$$\dot{U}_{ab} = R \cdot \dot{I}_{ab}; \quad \dot{I}_{ab} = G \cdot \dot{U}_{ab};$$




# Capacitance (Capacitor)

## Capacitor in the time domain

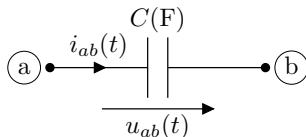

$$i_{ab}(t) = C \cdot \frac{du_{ab}(t)}{dt} = \omega C \cdot U_0 \sin(\omega t + \varphi + 90^\circ)$$

## Phasor representation of a capacitor

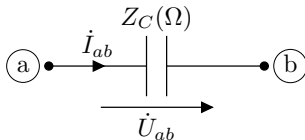


$$\begin{aligned} \dot{I}_{ab} &= j\omega C \cdot \dot{U}_{ab} \\ \Leftrightarrow \dot{U}_{ab} &= \frac{1}{j\omega C} \cdot \dot{I}_{ab} = Z_C \cdot \dot{I}_{ab} \end{aligned}$$




# Inductance (Inductor)

## Inductor in the time domain

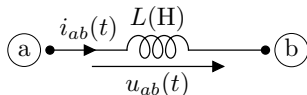

$$u_{ab}(t) = L \cdot \frac{di_{ab}(t)}{dt} = \omega L \cdot I_0 \sin(\omega t + \theta + 90^\circ)$$

## Phasor representation of an inductor

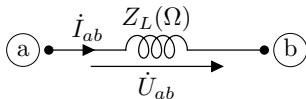


$$\begin{aligned} \dot{U}_{ab} &= j\omega L \cdot \dot{I}_{ab} \\ &= Z_L \cdot \dot{I}_{ab} \end{aligned}$$

⇒ The concept of **complex impedance**  $Z_C$  and  $Z_L$



# Mutual Inductance Between Two Coils


Mutual inductance in the time domain

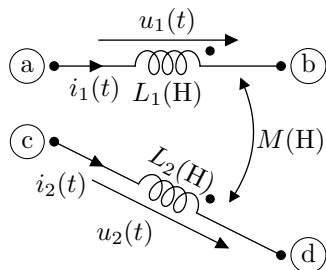

$$u_1(t) = L_1 \cdot \frac{di_1(t)}{dt} \pm M \cdot \frac{di_2(t)}{dt}$$

$$u_2(t) = L_2 \cdot \frac{di_2(t)}{dt} \pm M \cdot \frac{di_1(t)}{dt}$$

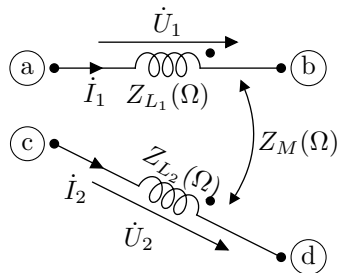Phasor representation of mutual inductance




$$\begin{aligned} \dot{U}_1 &= j\omega L_1 \cdot \dot{I}_1 \pm j\omega M \cdot \dot{I}_2 \\ &= Z_{L_1} \cdot \dot{I}_1 \pm Z_M \cdot \dot{I}_2 \\ \dot{U}_2 &= j\omega L_2 \cdot \dot{I}_2 \pm j\omega M \cdot \dot{I}_1 \\ &= Z_{L_2} \cdot \dot{I}_2 \pm Z_M \cdot \dot{I}_1 \end{aligned}$$




# Phasor Representations of Dependent Sources

## Voltage-controlled voltage source

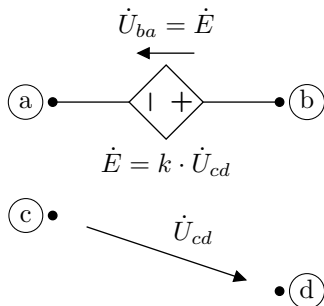


## Current-controlled voltage source

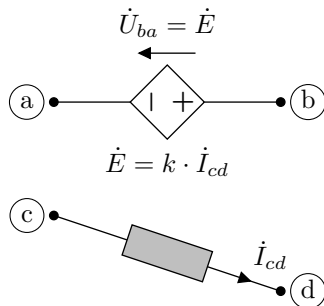




# Phasor Representations of Dependent Sources

## Voltage-controlled current source

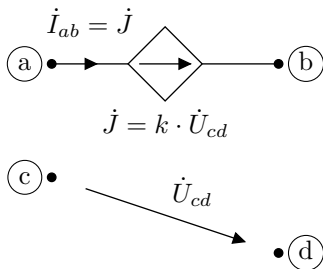

## Current-controlled current source

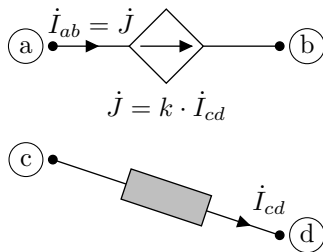




# Phasor Representation of the Operational Amplifier
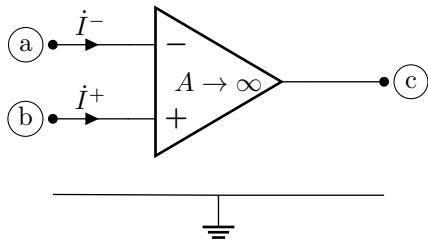
## Practical op-amp

- The characteristic relation keeps its general form

$$\begin{cases} \dot{I}^+ \approx 0; \dot{I}^- \approx 0 \\ \dot{V}_c = A (\dot{V}_b - \dot{V}_a) \end{cases}$$



## Ideal op-amp

- Gain  $A = \infty$
- $$\begin{cases} \dot{I}^+ = 0; \dot{I}^- = 0 \\ \dot{V}_a = \dot{V}_b \end{cases}$$




# Chapter Outline

- ④ Linear Circuits in Steady State with Sinusoidal Sources
  - Sinusoidal AC Quantities
  - Characteristic Equations of AC Circuit Elements
  - Kirchhoff Equations in AC Circuits
  - Using Complex Numbers to determine Sinusoidal Quantities
  - Phasor Representations of Circuit Elements
  - Phasor Representation of a Circuit and Kirchhoff Equation System




# Phasor Representation of a Circuit

## Circuit in the time domain

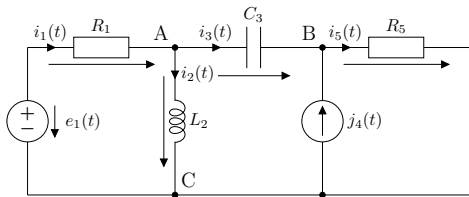


## Phasor representation of the circuit

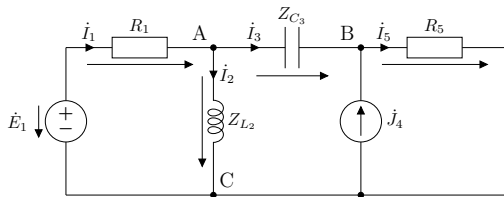



# Phasor Representation of the Kirchhoff Equations

## Circuit in the time domain

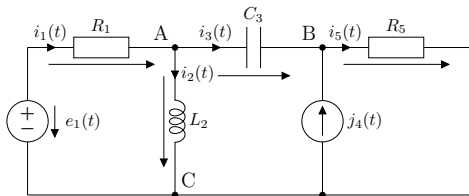


$$i_1(t) - i_2(t) - i_3(t) = 0$$

$$i_3(t) + j_4(t) - i_5(t) = 0$$

$$u_{R_1}(t) + u_{L_2}(t) - e_1(t) = 0$$

$$u_{C_3}(t) + u_{R_5}(t) - u_{L_2}(t) = 0$$

## Phasor representation of the circuit

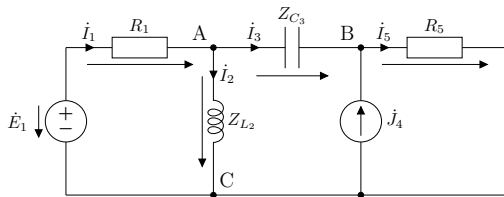

$$\dot{I}_1 - \dot{I}_2 - \dot{I}_3 = 0$$

$$\dot{I}_3 + \dot{J}_4 - \dot{I}_5 = 0$$


$$\dot{U}_{R_1} + \dot{U}_{L_2} - \dot{E}_1 = 0$$

$$\dot{U}_{C_3} + \dot{U}_{R_5} - \dot{U}_{L_2} = 0$$



# DC Circuits and Phasor Circuits

## DC circuit

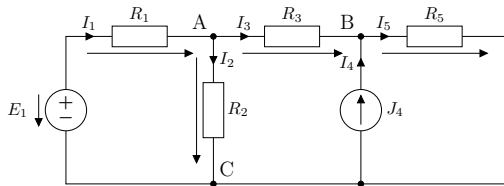


$$I_1 - I_2 - I_3 = 0$$

$$I_3 + J_4 - I_5 = 0$$

$$U_{R_1} + U_{R_2} - E_1 = 0$$

$$U_{R_3} + U_{R_5} - U_{R_2} = 0$$

## Phasor representation of a AC circuit

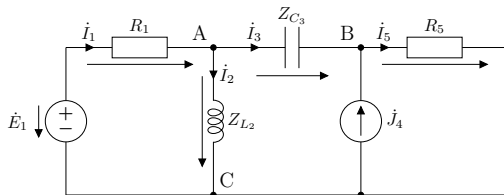

$$\dot{I}_1 - \dot{I}_2 - \dot{I}_3 = 0$$


$$\dot{I}_3 + \dot{J}_4 - \dot{I}_5 = 0$$

$$\dot{U}_{R_1} + \dot{U}_{L_2} - \dot{E}_1 = 0$$

$$\dot{U}_{C_3} + \dot{U}_{R_5} - \dot{U}_{L_2} = 0$$



# Exercises

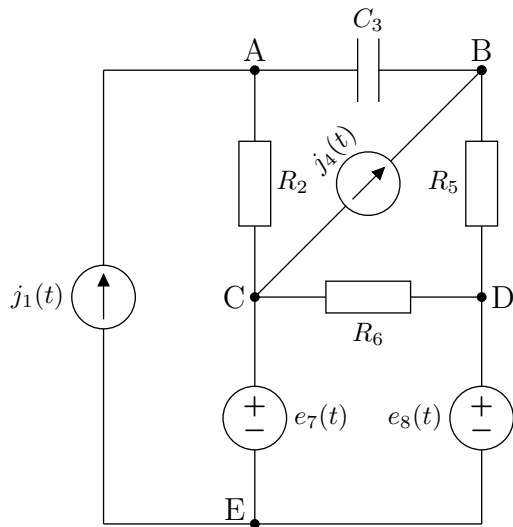

$$j_1(t) = 2 \sin 50t \text{ A}$$

$$j_4(t) = 3 \sin (50t + 30^\circ) \text{ A}$$

$$e_7(t) = 80 \sin (50t - 45^\circ) \text{ V}$$

$$e_8(t) = 45 \sin (50t + 90^\circ) \text{ V}$$

$$R_2 = 20 \Omega; R_5 = 16 \Omega$$

$$R_6 = 24 \Omega; C_3 = 0,4 \text{ mF}$$

determine the impedances

Write the Kirchhoff equation systems



# Course Outline

- 1 Concepts of Kirchhoff Circuit Model
- 2 Linear Circuits in Steady State with DC Sources
- 3 Methods for Solving Linear Steady-State DC Circuits
- 4 Linear Circuits in Steady State with Sinusoidal Sources
- 5 Methods for Solving Linear Steady-State AC circuits**
- 6 Thévenin–Norton Theorem and One-Port Networks
- 7 Mutual Inductance and Solving Magnetically Coupled Circuits
- 8 Two-Port Networks
- 9 Circuits with Multiple Frequencies and Non-Sinusoidal Sources
- 10 Three-Phase Circuits



# Chapter Outline

- 5 Methods for Solving Linear Steady-State AC circuits
  - Branch-Current Method
  - Loop Analysis
  - Nodal Analysis
  - Equivalent-Impedance Method
  - Superposition Method
  - Power in Sinusoidal AC Circuits



# Solving Circuits in the Complex Domain


Characteristic equations  
in the time domain

$$u(t) = U_0 \sin(\omega t + \phi)$$

$$i(t) = I_0 \sin(\omega t + \theta)$$

$$u_L(t) = L \frac{di_L(t)}{dt}$$

$$i_C(t) = C \frac{du_C(t)}{dt}$$

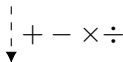

Solution in the time  
domain

$$u(t) ; i(t)$$

Phasor  
→


Linear algebraic equations  
in the complex domain

$$\dot{U} = \frac{U_0}{\sqrt{2}} \angle \phi$$

$$\dot{I} = \frac{I_0}{\sqrt{2}} \angle \theta$$

$$\dot{U}_L = j\omega L \dot{I}_L = Z_L \dot{I}_L$$
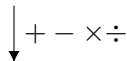
$$\dot{U}_C = \frac{1}{j\omega C} \dot{I}_C = Z_C \dot{I}_C$$



Solution in the complex  
domain

$$\dot{U} ; \dot{I}$$

Inverse phasor  
←



# Chapter Outline

## 5 Methods for Solving Linear Steady-State AC circuits

- Branch-Current Method
- Loop Analysis
- Nodal Analysis
- Equivalent-Impedance Method
- Superposition Method
- Power in Sinusoidal AC Circuits




# Branch-Current Method

## Example 5.1

- 5 branches  $\rightarrow$  5 equations in 5 unknowns
- 3 nodes  $\rightarrow$  set up  $3 - 1 = 2$  KCL equations and  $5 - 2 = 3$  KVL equations
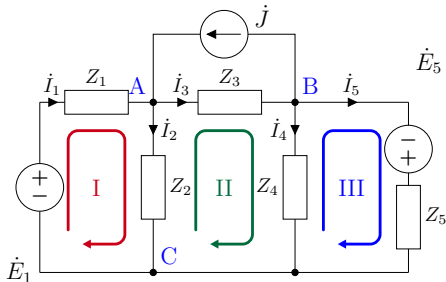
## Kirchhoff equation system

- Node A:  $\dot{I}_1 - \dot{I}_2 - \dot{I}_3 + \dot{J} = 0$
- Node B:  $\dot{I}_3 - \dot{I}_4 - \dot{I}_5 - \dot{J} = 0$
- Loop I:  $\dot{U}_{Z_1} + \dot{U}_{Z_2} - \dot{E}_1 = 0$
- Loop II:  $-\dot{U}_{Z_2} + \dot{U}_{Z_3} + \dot{U}_{Z_4} = 0$
- Loop III:  $-\dot{U}_{Z_4} + \dot{U}_{Z_5} - \dot{E}_5 = 0$



## Branch-current equation system

- A:  $\dot{I}_1 - \dot{I}_2 - \dot{I}_3 + \dot{J} = 0$
- B:  $\dot{I}_3 - \dot{I}_4 - \dot{I}_5 - \dot{J} = 0$
- I:  $\dot{I}_1 Z_1 + \dot{I}_2 Z_2 - \dot{E}_1 = 0$
- II:  $-\dot{I}_2 Z_2 + \dot{I}_3 Z_3 + \dot{I}_4 Z_4 = 0$
- III:  $-\dot{I}_4 Z_4 - \dot{E}_5 + \dot{I}_5 Z_5 = 0$



# Branch-Current Method

## Example 5.2


Determine the currents using the branch-current method

$$e_1(t) = 12\sqrt{2} \sin(10t + 20^\circ) \text{ V};$$

$$R_1 = 5 \Omega; L_2 = 0,3 \text{ H};$$

$$C_3 = 0,02 \text{ F}; R_5 = 8 \Omega;$$
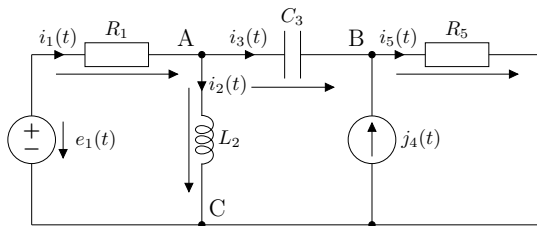
$$j_4(t) = \sqrt{2} \sin(10t - 15^\circ) \text{ A}.$$





# Branch-Current Method


Example 5.2: convert to the complex domain

$$\dot{E}_1 = 12/20^\circ \text{ V};$$

$$R_1 = 5 \Omega; Z_{L_2} = j3 \Omega;$$

$$Z_{C_3} = -j5 \Omega; R_5 = 8 \Omega;$$

$$\dot{J}_4 = 1/-15^\circ \text{ A}.$$

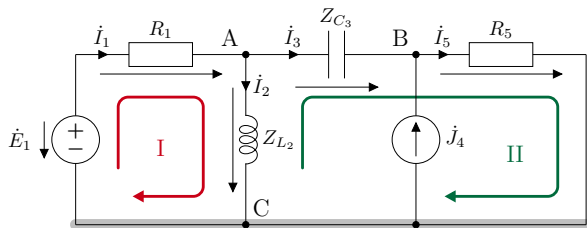

Kirchhoff equation system

- $\dot{I}_1 - \dot{I}_2 - \dot{I}_3 = 0$
- $\dot{I}_3 - \dot{I}_5 + \dot{J} = 0$
- $\dot{U}_{R_1} + \dot{U}_{L_2} - \dot{E}_1 = 0$
- $\dot{U}_{C_3} + \dot{U}_{R_5} - \dot{U}_{L_2} = 0$

Branch-current equation system

- $\dot{I}_1 - \dot{I}_2 - \dot{I}_3 = 0$
- $\dot{I}_3 - \dot{I}_5 + \dot{J} = 0$
- $R_1 \dot{I}_1 + Z_{L_2} \dot{I}_2 - \dot{E}_1 = 0$
- $Z_{C_3} \dot{I}_3 + R_5 \dot{I}_5 - Z_{L_2} \dot{I}_2 = 0$



# Branch-Current Method

## Matrix form of the equation system

- Substitute  $\dot{I}_1 = \dot{I}_2 + \dot{I}_3$  and  $\dot{I}_5 = \dot{I}_3 + \dot{J}$  into loops I and II

$$\begin{bmatrix} R_1 + Z_{L_2} & R_1 \\ -Z_{L_2} & R_5 + Z_{C_3} \end{bmatrix} \begin{bmatrix} \dot{I}_2 \\ \dot{I}_3 \end{bmatrix} = \begin{bmatrix} \dot{E}_1 \\ -R_5 \dot{J} \end{bmatrix}$$

$$\Leftrightarrow \begin{bmatrix} 5 + j3 & 5 \\ -j3 & 8 - j5 \end{bmatrix} \begin{bmatrix} \dot{I}_2 \\ \dot{I}_3 \end{bmatrix} = \begin{bmatrix} 12\angle 20^\circ \\ -8\angle -15^\circ \end{bmatrix}$$

- Solve using Gaussian elimination or Cramer's rule

$$\dot{I}_1 = 1,6405\angle -22,25^\circ \Rightarrow i_1(t) = 1,6405\sqrt{2}\sin(10t - 22,25^\circ) \text{ A}$$

$$\dot{I}_2 = 2,6988\angle -27,07^\circ \Rightarrow i_2(t) = 2,6988\sqrt{2}\sin(10t - 27,07^\circ) \text{ A}$$

$$\dot{I}_3 = 1,0730\angle 145,55^\circ \Rightarrow i_3(t) = 1,0730\sqrt{2}\sin(10t + 145,55^\circ) \text{ A}$$

$$\dot{I}_5 = 0,3575\angle 76,88^\circ \Rightarrow i_5(t) = 0,3575\sqrt{2}\sin(10t + 76,88^\circ) \text{ A}$$



# Chapter Outline

## 5 Methods for Solving Linear Steady-State AC circuits


- Branch-Current Method
- **Loop Analysis**
- Nodal Analysis
- Equivalent-Impedance Method
- Superposition Method
- Power in Sinusoidal AC Circuits



# Loop Analysis
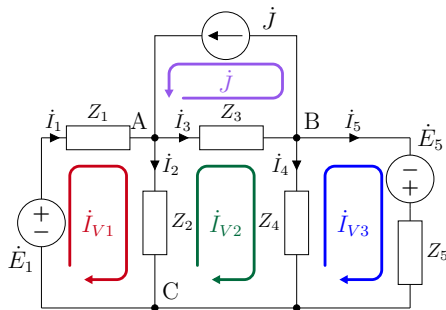
## Example 5.3

- The circuit has 5 branches and 3 nodes  $\rightarrow$  it has  $5 - 3 + 1 = 3$  fundamental loops
- Define 3 loop currents and a current-source discharging loop



## Branch-current equations on loops from KVL

- Loop 1:  $\dot{I}_1 Z_1 + \dot{I}_2 Z_2 - \dot{E}_1 = 0$
- Loop 2:  $-\dot{I}_2 Z_2 + \dot{I}_3 Z_3 + \dot{I}_4 Z_4 = 0$
- Loop 3:  $-\dot{I}_4 Z_4 + \dot{I}_5 Z_5 - \dot{E}_5 = 0$

## Relation between branch currents and loop currents

- $\dot{I}_1 = \dot{I}_{V1}$ ;  $\dot{I}_2 = \dot{I}_{V1} - \dot{I}_{V2}$
- $\dot{I}_3 = \dot{I}_{V2} + J$ ;  $\dot{I}_4 = \dot{I}_{V2} - \dot{I}_{V3}$
- $\dot{I}_5 = \dot{I}_{V3}$



# Loop Analysis

⇒ Matrix form of the loop-current equation system

$$\begin{bmatrix} Z_1 + Z_2 & -Z_2 & 0 \\ -Z_2 & Z_2 + Z_3 + Z_4 & -Z_4 \\ 0 & -Z_4 & Z_4 + Z_5 \end{bmatrix} \begin{bmatrix} \dot{I}_{V1} \\ \dot{I}_{V2} \\ \dot{I}_{V3} \end{bmatrix} = \begin{bmatrix} \dot{E}_1 \\ -Z_3 \dot{J} \\ \dot{E}_5 \end{bmatrix}$$

Supplement: Sarrus' rule for computing a  $3 \times 3$  determinant

• For matrix  $A^{3 \times 3}$

$$\begin{vmatrix} a_{11} & a_{12} & a_{13} \\ a_{21} & a_{22} & a_{23} \\ a_{31} & a_{32} & a_{33} \end{vmatrix} \begin{matrix} a_{11} & a_{12} & - \\ a_{21} & a_{22} & \\ a_{31} & a_{32} & + \end{matrix}$$

⇒ The determinant of the matrix

$$\begin{aligned} \det A = & a_{11}a_{22}a_{33} + a_{12}a_{23}a_{31} \\ & + a_{13}a_{21}a_{32} - a_{31}a_{22}a_{13} \\ & - a_{32}a_{23}a_{11} - a_{33}a_{21}a_{12} \end{aligned}$$


⚠ This rule is NOT valid for determinants of order  $\geq 4$



# Loop Analysis
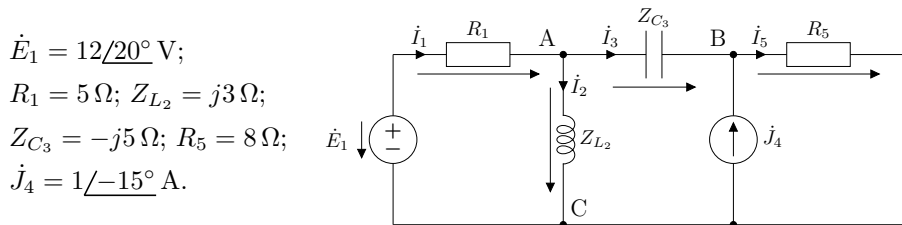
## Example 5.4

Solve the circuit using the loop analysis



Branch-current equations on loops from KVL

- $R_1 \dot{I}_1 + Z_{L_2} \dot{I}_2 - \dot{E}_1 = 0$
- $Z_{C_3} \dot{I}_3 + R_5 \dot{I}_5 - Z_{L_2} \dot{I}_2 = 0$

Relation between branch currents and loop currents

- $\dot{I}_1 = \dot{I}_{V1}; \dot{I}_2 = \dot{I}_{V1} - \dot{I}_{V2}$
- $\dot{I}_3 = \dot{I}_{V2}; \dot{I}_5 = \dot{I}_{V2} + \dot{J}$



# Loop Analysis

Matrix form of the loop-current equation system

$$\begin{bmatrix} R_1 + Z_{L_2} & -Z_{L_2} \\ -Z_{L_2} & Z_{L_2} + Z_{C_3} + R_5 \end{bmatrix} \begin{bmatrix} \dot{I}_{V1} \\ \dot{I}_{V2} \end{bmatrix} = \begin{bmatrix} \dot{E}_1 \\ -R_5 j \end{bmatrix}$$

$$\Leftrightarrow \begin{bmatrix} 5 + j3 & -j3 \\ -j3 & 8 - j2 \end{bmatrix} \begin{bmatrix} \dot{I}_{V1} \\ \dot{I}_{V2} \end{bmatrix} = \begin{bmatrix} 12/\underline{20^\circ} \\ -8/\underline{-15^\circ} \end{bmatrix}$$

- Solve the system using algebraic methods

$$\dot{I}_{V1} = 1,6403/\underline{-22,25^\circ} \text{ A}$$

$$\dot{I}_{V2} = 1,0730/\underline{145,55^\circ} \text{ A}$$

$\Rightarrow$  determine the branch currents and other quantities



# Chapter Outline

## 5 Methods for Solving Linear Steady-State AC circuits


- Branch-Current Method
- Loop Analysis
- **Nodal Analysis**
- Equivalent-Impedance Method
- Superposition Method
- Power in Sinusoidal AC Circuits



# Nodal Analysis
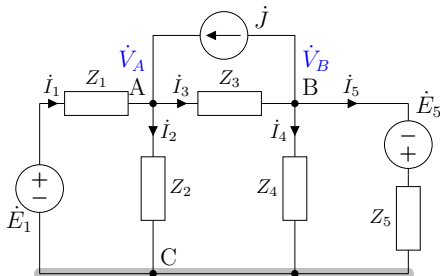
## Example 5.5

- The circuit has 3 nodes  $\rightarrow 3 - 1 = 2$  KCL equations
- Choose point C as *ground*
- The unknowns are the potentials  $\dot{V}_A$  and  $\dot{V}_B$



## KCL equation system

- Node A:  $\dot{I}_1 - \dot{I}_2 - \dot{I}_3 + \dot{J} = 0$
- $\Leftrightarrow \frac{\dot{U}_{Z1}}{Z_1} - \frac{\dot{U}_{Z2}}{Z_2} - \frac{\dot{U}_{Z3}}{Z_3} = -\dot{J}$
- Node B:  $\dot{I}_3 - \dot{I}_4 - \dot{I}_5 - \dot{J} = 0$
- $\Leftrightarrow \frac{\dot{U}_{Z3}}{Z_3} - \frac{\dot{U}_{Z4}}{Z_4} - \frac{\dot{U}_{Z5}}{Z_5} = \dot{J}$

## Node-potential equation system

- $\frac{-\dot{V}_A + \dot{E}_1}{Z_1} - \frac{\dot{V}_A}{Z_2} - \frac{\dot{V}_A - \dot{V}_B}{Z_3} = -\dot{J}$
- $\frac{\dot{V}_A - \dot{V}_B}{Z_3} - \frac{\dot{V}_B}{Z_4} - \frac{\dot{V}_B + \dot{E}_5}{Z_5} = \dot{J}$



# Nodal Analysis

## Example 5.6


Solve the circuit below using the nodal analysis

$$\dot{E}_1 = 12/\underline{20^\circ} \text{ V};$$

$$R_1 = 5 \Omega; Z_{L_2} = j3 \Omega;$$

$$Z_{C_3} = -j5 \Omega; R_5 = 8 \Omega;$$
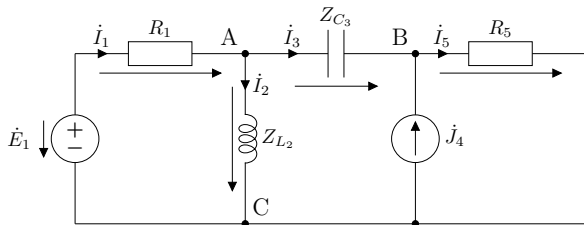
$$\dot{J}_4 = 1/\underline{-15^\circ} \text{ A}.$$



### KCL equation system

$$\bullet \dot{I}_1 - \dot{I}_2 - \dot{I}_3 = 0$$

$$\bullet \dot{I}_3 - \dot{I}_5 + \dot{J}_4 = 0$$

### Node-potential equation system

$$\bullet \frac{-\dot{V}_A + \dot{E}_1}{R_1} - \frac{\dot{V}_A}{Z_{L_2}} - \frac{\dot{V}_A - \dot{V}_B}{Z_{C_3}} = 0$$

$$\bullet \frac{\dot{V}_A - \dot{V}_B}{Z_{C_3}} - \frac{\dot{V}_B}{R_5} + \dot{J}_4 = 0$$



# Nodal Analysis

Matrix form of the node-potential equation system

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{Z_{L_2}} + \frac{1}{Z_{C_3}} & -\frac{1}{Z_{C_3}} \\ -\frac{1}{Z_{C_3}} & \frac{1}{R_5} + \frac{1}{Z_{C_3}} \end{bmatrix} \begin{bmatrix} \dot{V}_A \\ \dot{V}_B \end{bmatrix} = \begin{bmatrix} \frac{\dot{E}_1}{R_1} \\ j_4 \end{bmatrix}$$

$$\Leftrightarrow \begin{bmatrix} \frac{1}{5} + \frac{1}{j3} + \frac{1}{-j5} & -\frac{1}{-j5} \\ -\frac{1}{-j5} & \frac{1}{8} + \frac{1}{-j5} \end{bmatrix} \begin{bmatrix} \dot{V}_A \\ \dot{V}_B \end{bmatrix} = \begin{bmatrix} 2,4 \angle 20^\circ \\ 1 \angle -15^\circ \end{bmatrix}$$

- Solve the system using algebraic methods


$$\dot{V}_A = 8,0964 \angle 62,93^\circ \text{ V}$$

$$\dot{V}_B = 2,8603 \angle 76,88^\circ \text{ V}$$



# Nodal Analysis

Consider an op-amp circuit

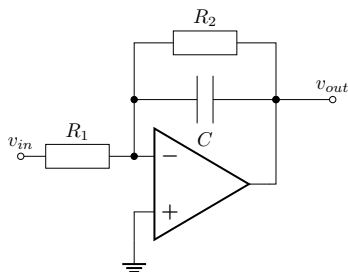

Exercise:

Inspect the solution and comment on the circuit property.

Ideal op-amp

- Ideal input currents are zero

$$\Rightarrow \dot{I}^+ = 0; \dot{I}^- = 0$$

- Ideal gain is  $\infty$

$$\Rightarrow \dot{V}^+ = \dot{V}^-$$

$$\dot{I}_{R1} - \dot{I}_{R2} - \dot{I}_C = 0$$

$$\Leftrightarrow \frac{\dot{V}_{in}}{R_1} + \frac{\dot{V}_{out}}{R_2} + \frac{\dot{V}_{out}}{Z_C} = 0$$

$$\Leftrightarrow \dot{V}_{out} = -\frac{\frac{1}{R_1}}{\frac{1}{R_2} + j\omega C} \dot{V}_{in}$$



# Chapter Outline


## 5 Methods for Solving Linear Steady-State AC circuits

- Branch-Current Method
- Loop Analysis
- Nodal Analysis
- Equivalent-Impedance Method
- Superposition Method
- Power in Sinusoidal AC Circuits



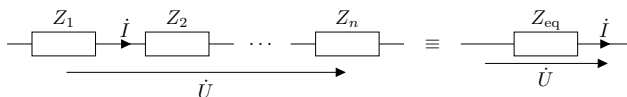
# Equivalent-Impedance Method

Series circuit: equivalent impedance equals total impedance



$$Z_{eq} = Z_1 + Z_2 + \dots + Z_n$$

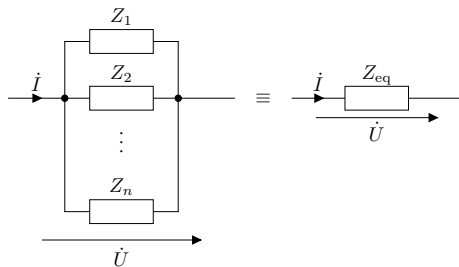Parallel circuit: equivalent admittance equals total admittance




$$Y_{eq} = Y_1 + Y_2 + \dots + Y_n$$

$$\Leftrightarrow \frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n}$$



# Equivalent-Impedance Method


## Voltage-division formula

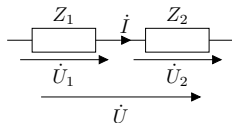

- General formula:  $\dot{U}_k = \frac{Z_k}{\sum_{i=1}^n Z_i} \cdot \dot{U}$
- Two-element case (common)

$$\dot{U}_1 = \frac{Z_1}{Z_1 + Z_2} \cdot \dot{U}; \quad \dot{U}_2 = \frac{Z_2}{Z_1 + Z_2} \cdot \dot{U}$$

## Current-division formula

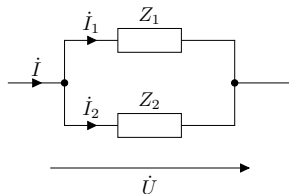



- General formula:  $\dot{I}_k = \frac{Y_k}{\sum_{i=1}^n Y_i} \cdot \dot{I}$
- Two-element case (common)

$$\dot{I}_1 = \frac{Z_2}{Z_1 + Z_2} \cdot \dot{I}; \quad \dot{I}_2 = \frac{Z_1}{Z_1 + Z_2} \cdot \dot{I}$$



# Equivalent-Impedance Method

## Wye–delta transformation

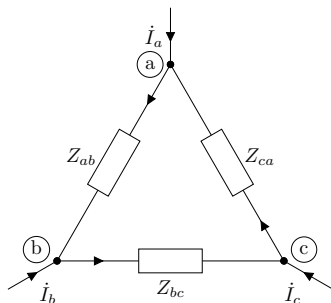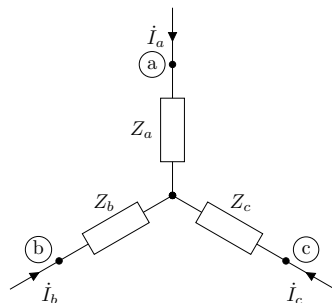
 $\equiv$ 


$$\begin{aligned}
 Z_{ab} &= Z_a + Z_b + \frac{Z_a \cdot Z_b}{Z_c} \\
 Y \rightarrow \Delta : Z_{bc} &= Z_b + Z_c + \frac{Z_b \cdot Z_c}{Z_a} \\
 Z_{ca} &= Z_c + Z_a + \frac{Z_c \cdot Z_a}{Z_b}
 \end{aligned}$$

$$\begin{aligned}
 Z_a &= \frac{Z_{ca} \cdot Z_{ab}}{Z_{ab} + Z_{bc} + Z_{ca}} \\
 \Delta \rightarrow Y : Z_b &= \frac{Z_{ab} \cdot Z_{bc}}{Z_{ab} + Z_{bc} + Z_{ca}} \\
 Z_c &= \frac{Z_{bc} \cdot Z_{ca}}{Z_{ab} + Z_{bc} + Z_{ca}}
 \end{aligned}$$



# Chapter Outline


## 5 Methods for Solving Linear Steady-State AC circuits

- Branch-Current Method
- Loop Analysis
- Nodal Analysis
- Equivalent-Impedance Method
- **Superposition Method**
- Power in Sinusoidal AC Circuits



# Superposition Method

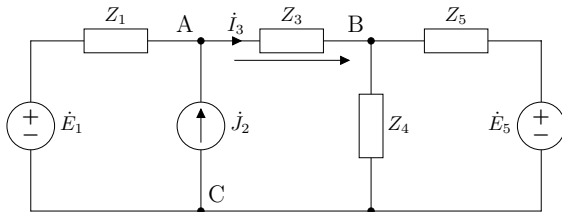Example 5.7: Determine current  $\dot{I}_3$  using superposition





Solution

- $\dot{I}_3 = \dot{I}_{31} + \dot{I}_{32} + \dot{I}_{35}$
- $\dot{I}_{31}$  is the current through  $Z_3$  when only  $\dot{E}_1$  acts, with  $\dot{J}_2$  and  $\dot{E}_5$  off
- $\dot{I}_{32}$  is the current through  $Z_3$  when only  $\dot{J}_2$  acts, with  $\dot{E}_1$  and  $\dot{E}_5$  off
- $\dot{I}_{35}$  is the current through  $Z_3$  when only  $\dot{E}_5$  acts, with  $\dot{J}_2$  and  $\dot{E}_1$  off



# Superposition Method

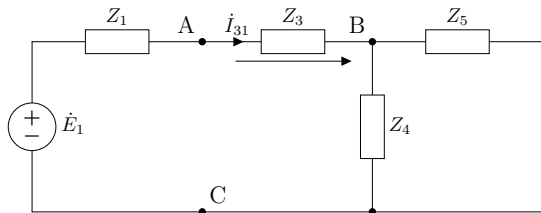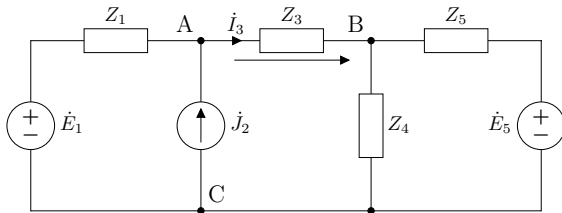Example 5.7: Determine current  $\dot{I}_3$  using superposition



Component  $\dot{I}_{31}$



$$Z_{\text{eq}} = Z_1 + Z_3 + \frac{Z_4 \cdot Z_5}{Z_4 + Z_5}$$

$$\dot{I}_{31} = \frac{\dot{E}_1}{Z_{\text{eq}}}$$



# Superposition Method

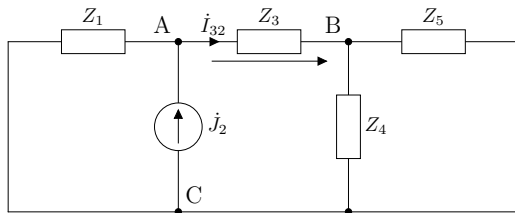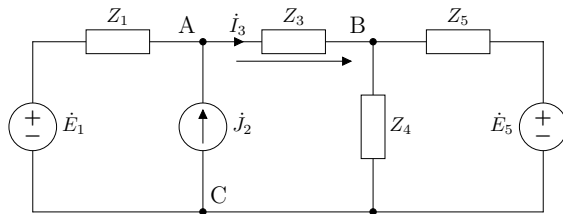Example 5.7: Determine current  $\dot{I}_3$  using superposition



Component  $\dot{I}_{32}$



$$Z_{345} = Z_3 + \frac{Z_4 \cdot Z_5}{Z_4 + Z_5}$$

$$\dot{I}_{32} = \frac{Z_1}{Z_1 + Z_{345}} \cdot \dot{j}_2$$



# Superposition Method

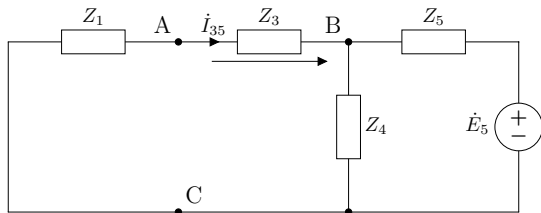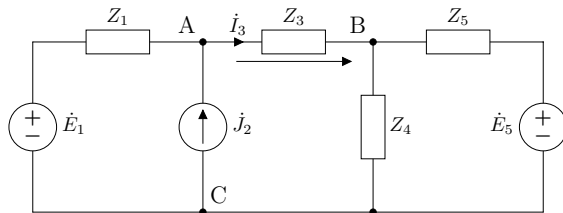Example 5.7: Determine current  $\dot{I}_3$  using superposition



Component  $\dot{I}_{35}$

$$Z_{\text{eq}} = Z_5 + \frac{Z_4 \cdot (Z_1 + Z_3)}{Z_1 + Z_3 + Z_4}$$

$$\dot{I}_{35} = -\frac{\dot{E}_5}{Z_{\text{eq}}} \cdot \frac{Z_4}{Z_1 + Z_3 + Z_4}$$




# Chapter Outline

- 5 Methods for Solving Linear Steady-State AC circuits
  - Branch-Current Method
  - Loop Analysis
  - Nodal Analysis
  - Equivalent-Impedance Method
  - Superposition Method
  - Power in Sinusoidal AC Circuits



# Instantaneous Power Concept

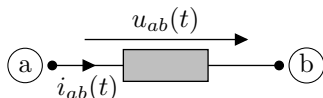

- Instantaneous absorbed power:  $p(t) = u_{ab}(t) \cdot i_{ab}(t)$
- When current and voltage are sinusoidal functions

$$u_{ab}(t) = U_0 \sin(\omega t + \varphi)$$

$$i_{ab}(t) = I_0 \sin(\omega t + \theta)$$

$$\Rightarrow p(t) = U_0 I_0 \sin(\omega t + \varphi) \sin(\omega t + \theta)$$

$$= \frac{U_0 I_0}{2} [\cos(\varphi - \theta) - \cos(2\omega t + \varphi + \theta)]$$

$$= \underbrace{\frac{U_0 I_0}{2} \cos(\varphi - \theta)}_{\text{Constant component}} - \underbrace{\frac{U_0 I_0}{2} \cos(2\omega t + \varphi + \theta)}_{\text{Time-varying component}}$$

Constant component

Time-varying component



# Average Power Concept

- Average power  $P$  is the average value of instantaneous power  $p(t)$

$$\begin{aligned}
 P &= \frac{1}{T} \int_0^T p(t) \cdot dt \\
 &= \frac{1}{T} \int_0^T \left[ \underbrace{\frac{U_0 I_0}{2} \cos(\varphi - \theta)}_{\text{Constant component}} - \underbrace{\frac{U_0 I_0}{2} \cos(2\omega t + \varphi + \theta)}_{\text{Time-varying component}} \right] dt \\
 &= \frac{U_0 I_0}{2} \cos(\varphi - \theta) \\
 &= \frac{U_0}{\sqrt{2}} \cdot \frac{I_0}{\sqrt{2}} \cdot \cos(\varphi - \theta)
 \end{aligned}$$

- $\Rightarrow$  Average power on a resistor equals the product of the RMS current and voltage (always  $\geq 0$ )
- $\Rightarrow$  Average power on an inductor and a capacitor is 0



# Average Power Concept

Computing average power from current and voltage phasors

$$\bullet u_{ab}(t) = U_0 \sin(\omega t + \varphi) \rightarrow \dot{U} = \frac{U_0}{\sqrt{2}} \angle \varphi$$

$$\bullet i_{ab}(t) = I_0 \sin(\omega t + \theta) \rightarrow \dot{I} = \frac{I_0}{\sqrt{2}} \angle \theta \rightarrow \dot{I}^* = \frac{I_0}{\sqrt{2}} \angle -\theta$$

$$\begin{aligned} \Rightarrow \dot{U} \cdot \dot{I}^* &= \frac{U_0 I_0}{2} \angle \varphi - \theta \\ &= \frac{U_0 I_0}{2} (\cos(\varphi - \theta) - j \sin(\varphi - \theta)) \\ &= \frac{U_0}{\sqrt{2}} \cdot \frac{I_0}{\sqrt{2}} \cos(\varphi - \theta) - j \cdot \frac{U_0}{\sqrt{2}} \cdot \frac{I_0}{\sqrt{2}} \sin(\varphi - \theta) \end{aligned}$$

$$\Rightarrow P = \operatorname{Re}(\dot{U} \cdot \dot{I}^*) \text{ (W)} \rightarrow \text{also called real power (or active power)}$$

---

$x^*$ : complex conjugate of  $x$



# Extending the Power Concept

- The phasor-domain viewpoint allows us to extend the concept of power

## Apparent power $S$

- The “visible” power obtained by multiplying the RMS current and voltage

$$S = \frac{U_0}{\sqrt{2}} \cdot \frac{I_0}{\sqrt{2}} \text{ (VA)}$$

⇒  $S$  is the modulus of  $(\dot{U} \cdot \dot{I}^*)$ ; its unit is **volt-ampere** (NOT watt)

## Reactive power $Q$

- Real power  $P$  is always less than apparent power  $S$

⇒ There is another component: the imaginary part of the product  $(\dot{U} \cdot \dot{I}^*)$

⇒  $Q = \text{Im}(\dot{U} \cdot \dot{I}^*) \text{ (VAR)}$  (**volt-ampere-reactive**)



# Extending the Power Concept

## Complex power

$$\dot{S} = (\dot{U} \cdot \dot{I}^*)$$

⇒ It contains active power in the real part and reactive power in the imaginary part:  $\dot{S} = P + j \cdot Q$ ; its unit is **VA**

⇒ Apparent power is the modulus of complex power:  
 $S = |\dot{S}| = \sqrt{P^2 + Q^2}$

## Power factor

- The ratio between real power and apparent power:

$$\text{pf} = \frac{P}{S} = \cos(\varphi - \theta)$$


- Often called the  **$\cos \varphi$  coefficient**


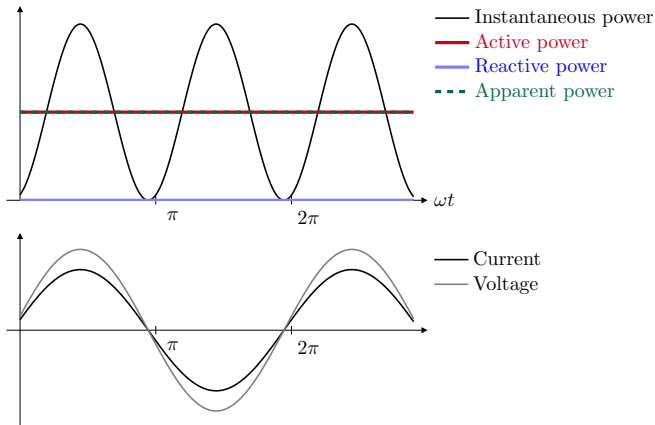
# Summary of Power Concepts

Purely resistive load: current and voltage are in phase

•  $\varphi = \theta \rightarrow$  power factor  $\cos(\varphi - \theta) = 1$





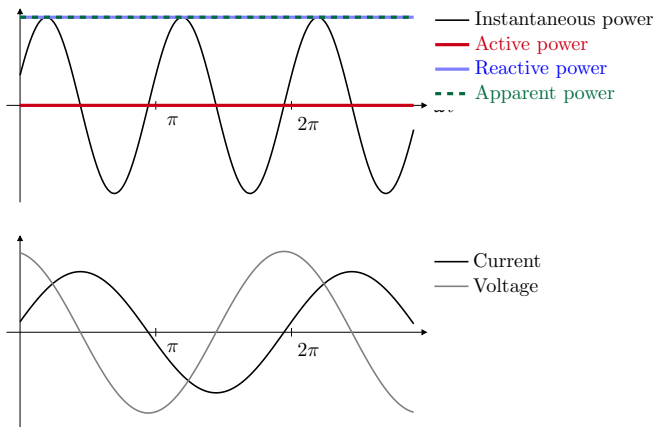
# Summary of Power Concepts

Purely inductive load: current lags voltage by  $90^\circ$

•  $\varphi - \theta = 90^\circ \rightarrow \text{power factor } \cos(\varphi - \theta) = 0$






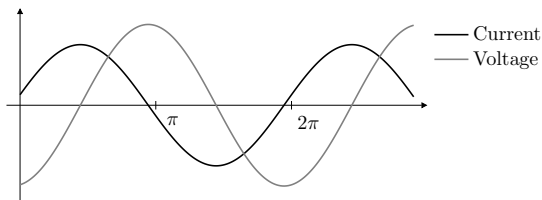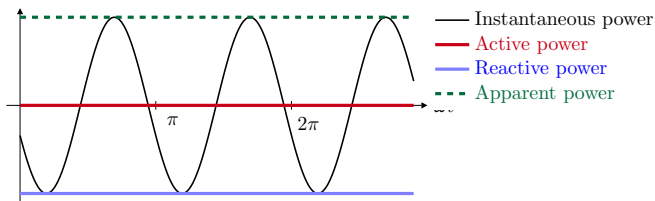
# Summary of Power Concepts

Purely capacitive load: voltage lags current by  $90^\circ$

•  $\varphi - \theta = -90^\circ \rightarrow \text{power factor } \cos(\varphi - \theta) = 0$





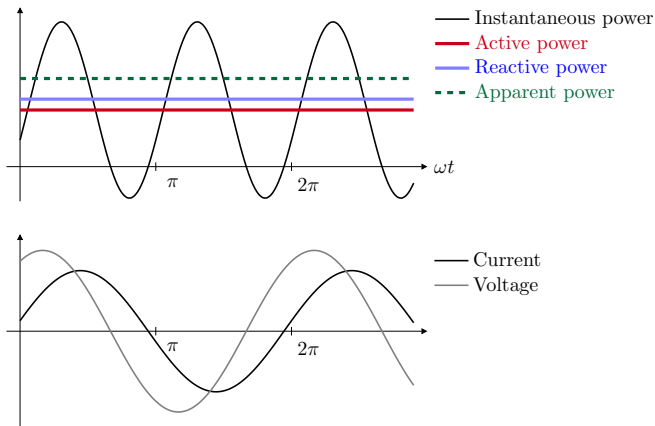
# Summary of Power Concepts

Inductive load: current lags voltage

- $\varphi > \theta \rightarrow$  power factor  $\cos(\varphi - \theta) < 1$






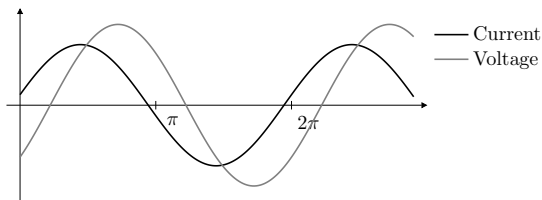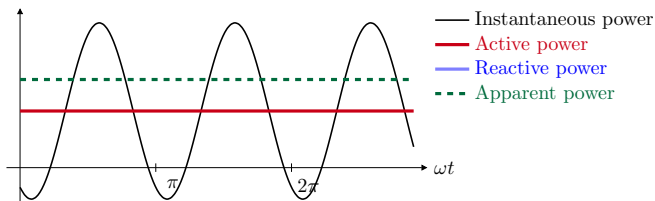
# Summary of Power Concepts

Capacitive load: voltage lags current

- $\varphi < \theta \rightarrow$  power factor  $\cos(\varphi - \theta) < 1$





# Course Outline

- 1 Concepts of Kirchhoff Circuit Model
- 2 Linear Circuits in Steady State with DC Sources
- 3 Methods for Solving Linear Steady-State DC Circuits
- 4 Linear Circuits in Steady State with Sinusoidal Sources
- 5 Methods for Solving Linear Steady-State AC circuits
- 6 Thévenin–Norton Theorem and One-Port Networks**
- 7 Mutual Inductance and Solving Magnetically Coupled Circuits
- 8 Two-Port Networks
- 9 Circuits with Multiple Frequencies and Non-Sinusoidal Sources
- 10 Three-Phase Circuits



# Chapter Outline

- 6 Thévenin–Norton Theorem and One-Port Networks
  - Source Transformation Method
  - Thévenin–Norton Theorem for One-Port Network Models
  - Impedance Matching Problem




# Chapter Outline

- 6 Thévenin–Norton Theorem and One-Port Networks
  - Source Transformation Method
  - Thévenin–Norton Theorem for One-Port Network Models
  - Impedance Matching Problem




# Practical Voltage-Source and Current-Source Models

## Ideal DC voltage source

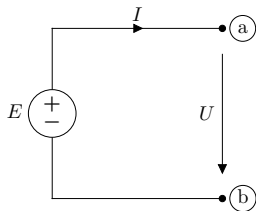

$$U = E$$

## Practical DC voltage source

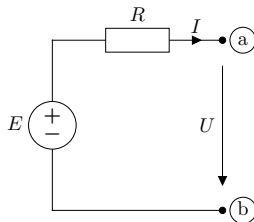


$$U = E - R \cdot I$$




# Practical Voltage-Source and Current-Source Models

## Ideal AC voltage source

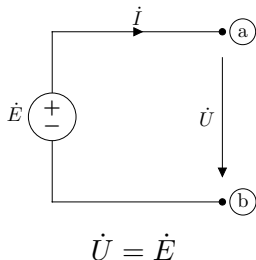


## Practical AC voltage source

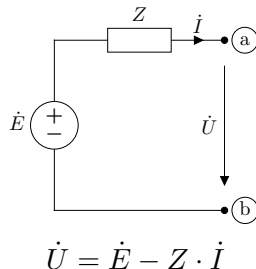




# Practical Voltage-Source and Current-Source Models

## Ideal DC current source

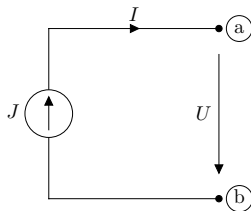

$$I = J$$

## Practical DC current source

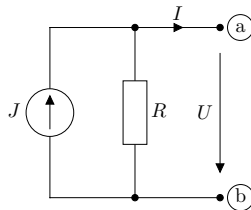


$$I = J - \frac{U}{R} \Leftrightarrow U = R \cdot J - R \cdot I$$




# Practical Voltage-Source and Current-Source Models

## Ideal AC current source

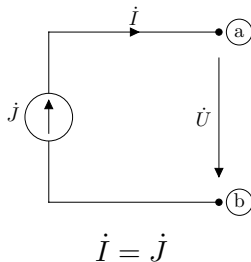


## Practical AC current source

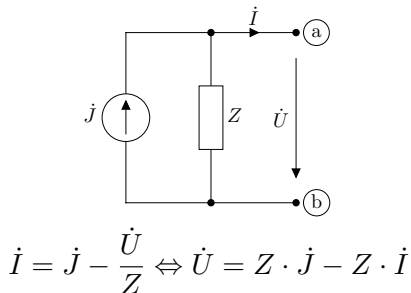




# Source Transformation

## Practical DC voltage source

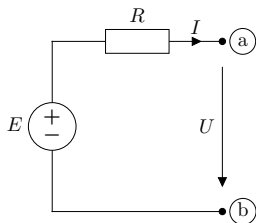

$$U = E - R \cdot I$$

## Practical DC current source

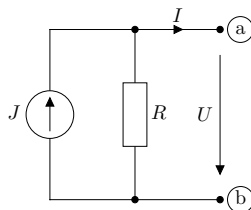


$$U = R \cdot J - R \cdot I$$

$\Rightarrow$  If  $E = R \cdot J \Leftrightarrow J = \frac{E}{R}$ , then the two models are equivalent




# Source Transformation

## Practical AC voltage source

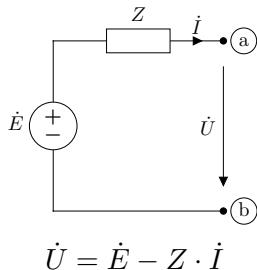

## Practical AC current source

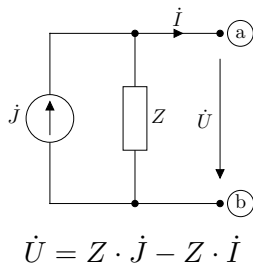

$\Rightarrow$  If  $\dot{E} = Z \cdot \dot{J} \Leftrightarrow \dot{J} = \frac{\dot{E}}{Z}$ , then **the two models are equivalent**

$\Rightarrow$  Source transformation method


If a circuit contains a practical voltage-source and/or current-source model, source transformation can be used to simplify the circuit structure.



# Source Transformation
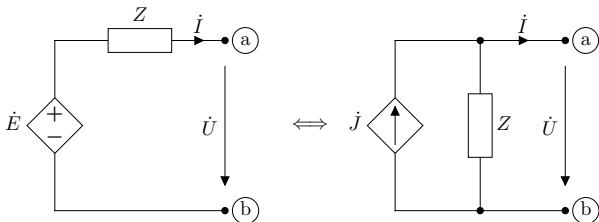
## Some notes

- The source-transformation formulas for DC circuits and AC circuits in the complex domain have equivalent forms  $\Rightarrow$  the lecture may discuss only one form
- Source transformation can be applied to dependent sources, provided that  $E = R \cdot J \Leftrightarrow J = \frac{E}{R}$  or  $\dot{E} = Z \cdot \dot{J} \Leftrightarrow \dot{J} = \frac{\dot{E}}{Z}$  is satisfied






# Source Transformation

## Some notes

- Source transformation changes the circuit structure  
 $\Rightarrow$  do not transform the element containing the current or voltage to be found
- Directions of current sources, voltage sources, and equivalent currents and voltages
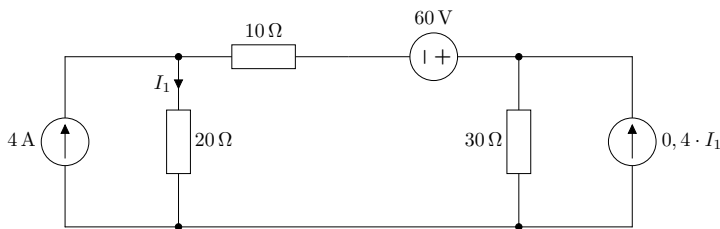
## Example 6.1: Determine $I_1$ using source transformation







# Chapter Outline

- 6 Thévenin–Norton Theorem and One-Port Networks
  - Source Transformation Method
  - Thévenin–Norton Theorem for One-Port Network Models
  - Impedance Matching Problem
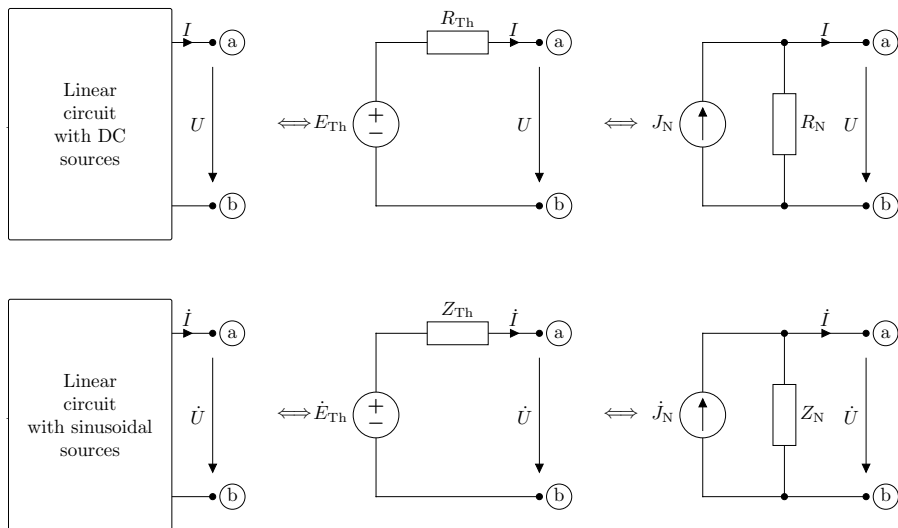
# Thévenin–Norton Theorem for One-Port Network



# Determining Thévenin–Norton Parameters

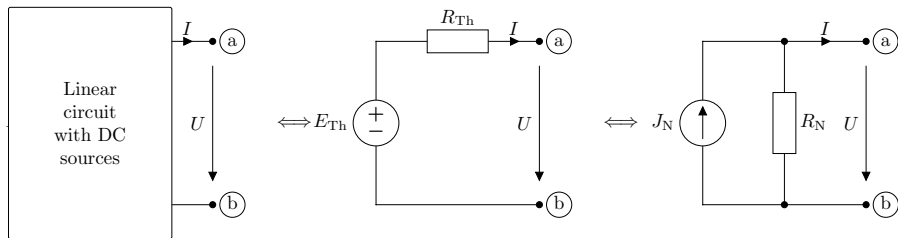


- The equivalent voltage source equals the open-circuit voltage:  $E_{Th} = U_{oc}$
- The equivalent current source equals the short-circuit current:  $J_N = I_{sc}$
- The resistance  $R_{Th} = R_N$  can be determined in 2 ways:
  1.  $R_{Th} = R_N = \frac{E_{Th}}{I_N} = \frac{E_{oc}}{I_{sc}}$
  2.  $R_{Th} = R_N = R_{eq}$  when the independent sources are suppressed
- The same applies to AC circuits



# Determining Thévenin–Norton Parameters
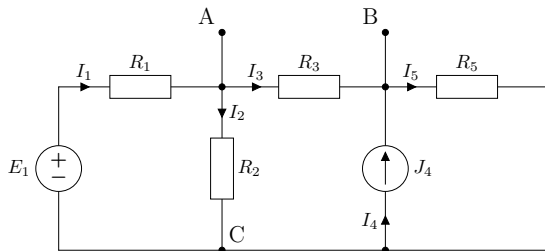
## Example 6.2

- Determine the Thévenin one-port model at nodes A and B
- Determine the Norton equivalent one-port model at nodes A and B
- Use the Thévenin–Norton theorem to determine  $I_3$



- $E_1 = 15 \text{ V}; R_1 = 5 \Omega;$
- $R_2 = 8 \Omega; R_3 = 6 \Omega;$
- $J_4 = 1 \text{ A}; R_5 = 10 \Omega.$



# Chapter Outline



- 6 Thévenin–Norton Theorem and One-Port Networks
  - Source Transformation Method
  - Thévenin–Norton Theorem for One-Port Network Models
  - Impedance Matching Problem



# Impedance Matching Problem
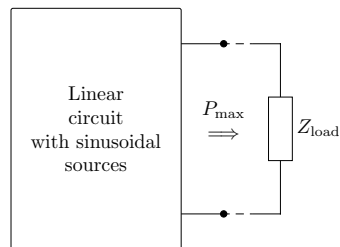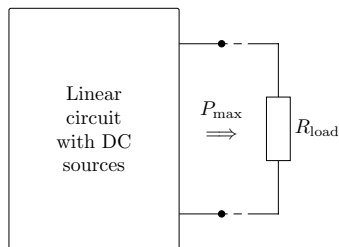
## Problem statement


- Determine the load value that maximizes the power received from the source circuit




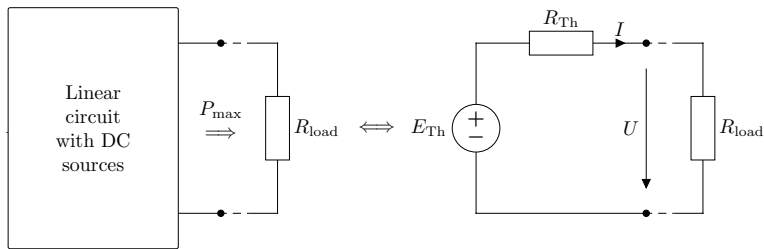
# Impedance Matching Problem

Solution: Use the Thévenin–Norton theorem




- $I = \frac{E_{Th}}{R_{Th} + R_l} \Leftrightarrow P = R_l \cdot I^2 = \frac{R_l \cdot E_{Th}^2}{(R_{Th} + R_l)^2} \leq \frac{E_{Th}^2}{4R_{Th}}$
- $P$  is maximized when the equality sign “=” occurs, with  $R_l = R_{Th}$
- Prove this with the Norton one-port model?


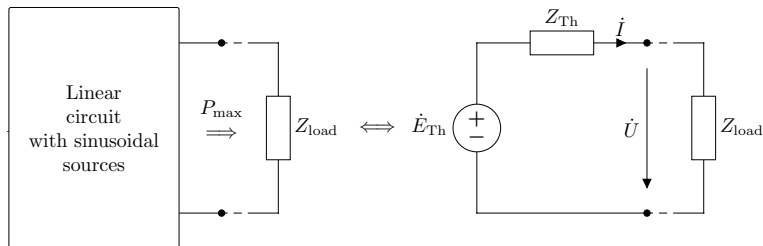
# Impedance Matching Problem

Solution: Use the Thévenin–Norton theorem



- $$\dot{I} = \frac{\dot{E}_{Th}}{Z_{Th} + Z_l} \Leftrightarrow P = \operatorname{Re}(Z_l) \cdot |\dot{I}|^2$$

$$= \frac{\operatorname{Re}(Z_l) \cdot |\dot{E}_{Th}|^2}{(\operatorname{Re}(Z_{Th}) + \operatorname{Re}(Z_l))^2 + (\operatorname{Im}(Z_{Th}) + \operatorname{Im}(Z_l))^2} \leq \frac{|\dot{E}_{Th}|^2}{4 \operatorname{Re}(Z_{Th})}$$
- $P$  is maximized when the equality sign “=” occurs, with  $Z_l = Z_{Th}^*$



# Impedance Matching Problem

## Example 6.3


- Determine the matched load to connect between nodes A and B for maximum power transfer

$$\dot{E}_1 = 12\angle 20^\circ \text{ V};$$

$$R_1 = 5 \Omega; Z_{L_2} = j3 \Omega;$$

$$Z_{C_3} = -j5 \Omega; R_5 = 8 \Omega;$$
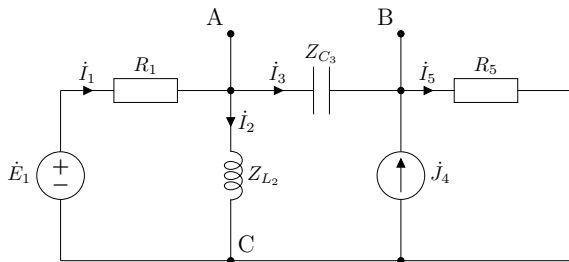
$$\dot{J}_4 = 1\angle -15^\circ \text{ A}.$$





# Course Outline

- 1 Concepts of Kirchhoff Circuit Model
- 2 Linear Circuits in Steady State with DC Sources
- 3 Methods for Solving Linear Steady-State DC Circuits
- 4 Linear Circuits in Steady State with Sinusoidal Sources
- 5 Methods for Solving Linear Steady-State AC circuits
- 6 Thévenin–Norton Theorem and One-Port Networks
- 7 Mutual Inductance and Solving Magnetically Coupled Circuits**
- 8 Two-Port Networks
- 9 Circuits with Multiple Frequencies and Non-Sinusoidal Sources
- 10 Three-Phase Circuits



# Chapter Outline

- 7 Mutual Inductance and Solving Magnetically Coupled Circuits
  - Mutual-Inductance Phenomenon
  - Methods for Solving Magnetically Coupled Circuits
  - Mutual-Inductance Power
  - One-Port Networks Containing Mutual Inductance




# Chapter Outline

- 7 Mutual Inductance and Solving Magnetically Coupled Circuits
  - Mutual-Inductance Phenomenon
  - Methods for Solving Magnetically Coupled Circuits
  - Mutual-Inductance Power
  - One-Port Networks Containing Mutual Inductance



# Mutual Inductance Between Two Coils


Mutual inductance in the time domain

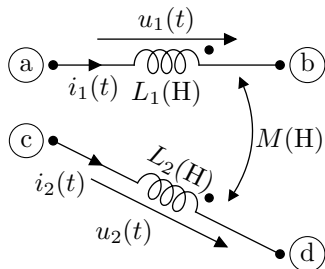

$$u_1(t) = L_1 \cdot \frac{di_1(t)}{dt} \pm M \cdot \frac{di_2(t)}{dt}$$

$$u_2(t) = L_2 \cdot \frac{di_2(t)}{dt} \pm M \cdot \frac{di_1(t)}{dt}$$

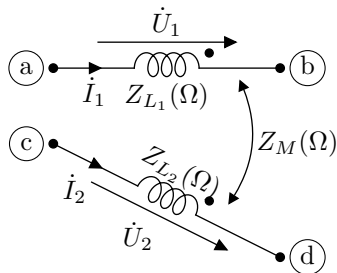Phasor representation of mutual inductance



$$\begin{aligned} \dot{U}_1 &= j\omega L_1 \cdot \dot{I}_1 \pm j\omega M \cdot \dot{I}_2 \\ &= Z_{L_1} \cdot \dot{I}_1 \pm Z_M \cdot \dot{I}_2 \\ \dot{U}_2 &= j\omega L_2 \cdot \dot{I}_2 \pm j\omega M \cdot \dot{I}_1 \\ &= Z_{L_2} \cdot \dot{I}_2 \pm Z_M \cdot \dot{I}_1 \end{aligned}$$




# Sign of the Mutual-Inductance Electromotive Force


## Rule for determining the sign of the mutual-inductance component

- If the directions of **both currents both enter or both leave** the polarity dots, the mutual-inductance component  $M$  has the **same sign** as the self-inductance component  $L$  of the coil being considered
- If **one current enters and one current leaves** the polarity dots, the mutual-inductance component  $M$  has the **opposite sign** to the self-inductance component  $L$  of the coil being considered

• Same sign

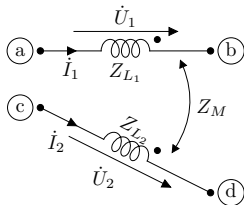

• Opposite sign

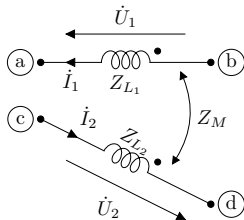




# Mutual-Inductance Model Using Dependent Source


- Same-sign mutual inductance: Example 1

## Mutual inductance

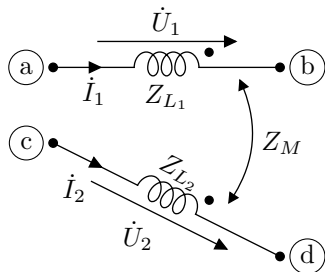

$$\begin{aligned}\dot{U}_1 &= Z_{L_1} \cdot \dot{I}_1 + Z_M \cdot \dot{I}_2 \\ \dot{U}_2 &= Z_{L_2} \cdot \dot{I}_2 + Z_M \cdot \dot{I}_1\end{aligned}$$

## Equivalent model

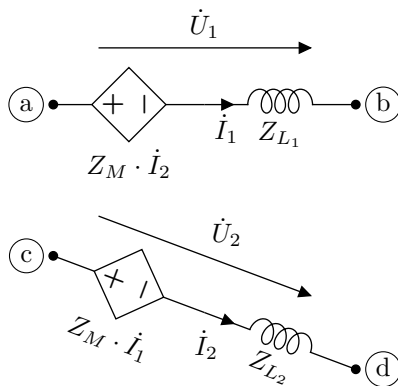




# Mutual-Inductance Model Using Dependent Source

- Same-sign mutual inductance: Example 2


## Mutual inductance

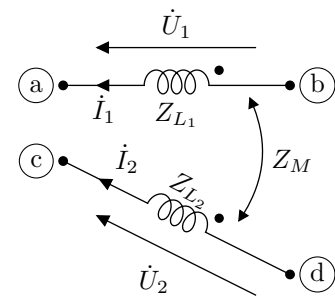

$$\dot{U}_1 = Z_{L1} \cdot \dot{I}_1 + Z_M \cdot \dot{I}_2$$

$$\dot{U}_2 = Z_{L2} \cdot \dot{I}_2 + Z_M \cdot \dot{I}_1$$

## Equivalent model

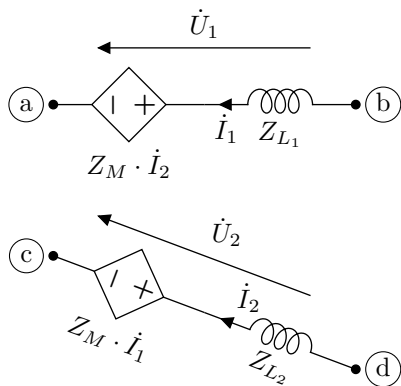




# Mutual-Inductance Model Using Dependent Source

- Opposite-sign mutual inductance: Example 1


## Mutual inductance

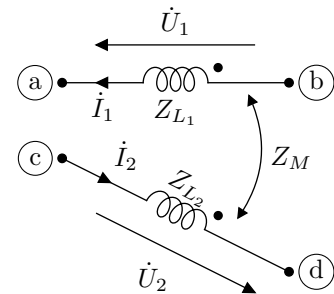

$$\dot{U}_1 = Z_{L1} \cdot \dot{I}_1 - Z_M \cdot \dot{I}_2$$

$$\dot{U}_2 = Z_{L2} \cdot \dot{I}_2 - Z_M \cdot \dot{I}_1$$

## Equivalent model

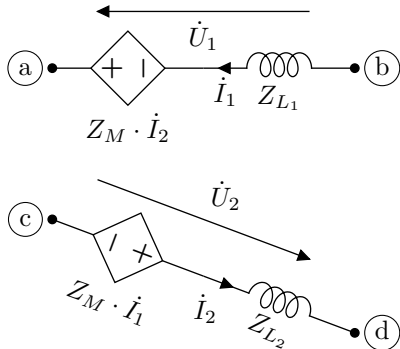




# Mutual-Inductance Model Using Dependent Source


- Opposite-sign mutual inductance: Example 2

## Mutual inductance

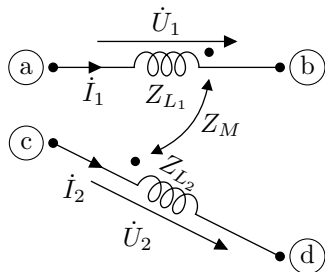

$$\begin{aligned}\dot{U}_1 &= Z_{L1} \cdot \dot{I}_1 - Z_M \cdot \dot{I}_2 \\ \dot{U}_2 &= Z_{L2} \cdot \dot{I}_2 - Z_M \cdot \dot{I}_1\end{aligned}$$

## Equivalent model

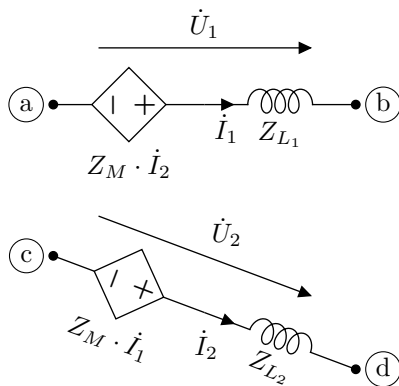



# Chapter Outline

- 7 Mutual Inductance and Solving Magnetically Coupled Circuits
  - Mutual-Inductance Phenomenon
  - Methods for Solving Magnetically Coupled Circuits
  - Mutual-Inductance Power
  - One-Port Networks Containing Mutual Inductance



# Methods for Solving Magnetically Coupled Circuits

## Steps for solving circuits with mutual inductance

1. Determine the sign of the mutual inductance
2. Convert the circuit with mutual inductance into equivalent model
3. Solve the circuit using studied methods

## Some notes


- ⚠ Because a magnetically coupled circuit is equivalent to current-controlled voltage sources, some methods are affected
  - Equivalent impedance: cannot be determined directly
  - Voltage-division and current-division: cannot be used directly
  - The nodal analysis is inconvenient
- Branch-current and loop analysis can be used normally



# Methods for Solving Magnetically Coupled Circuits
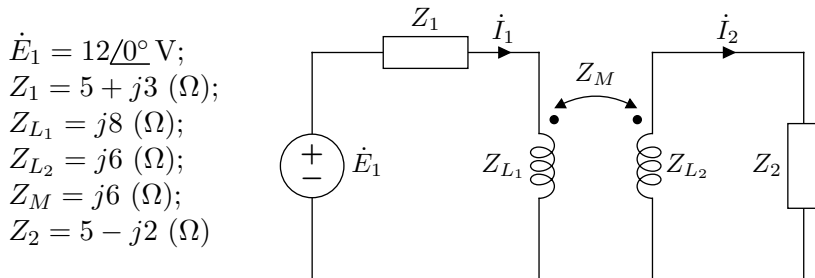
## Example 7.1

Given a transformer circuit. Determine currents and voltages on the coils.



- Determine the sign of the mutual inductance: the mutual-inductance EMF (the  $M$  component) has the opposite sign to the self-inductance EMF (the  $L$  component)




# Methods for Solving Magnetically Coupled Circuits
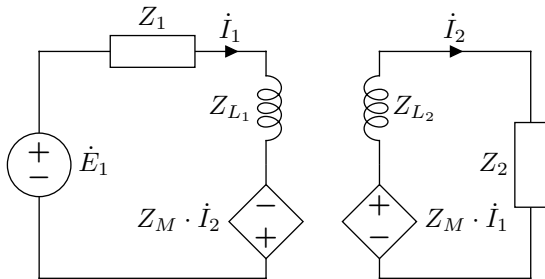
## Example 7.1

Convert to an equivalent CCVS model

$$\begin{aligned}\dot{E}_1 &= 12/\underline{0^\circ} \text{ V}; \\ Z_1 &= 5 + j3 \text{ } (\Omega); \\ Z_{L_1} &= j8 \text{ } (\Omega); \\ Z_{L_2} &= j6 \text{ } (\Omega); \\ Z_M &= j6 \text{ } (\Omega); \\ Z_2 &= 5 - j2 \text{ } (\Omega)\end{aligned}$$



- Number of branches: 2
- Number of essential nodes: 0

⇒ Number of loops: 2


☺ This circuit has the same number of branches and loops



# Methods for Solving Magnetically Coupled Circuits
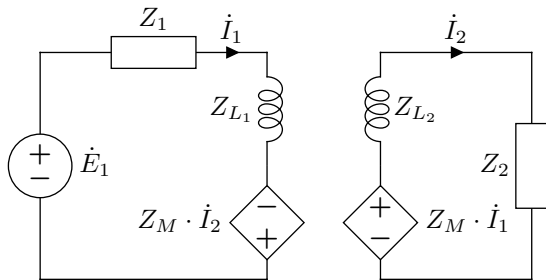
## Example 7.1

$$\begin{aligned}\dot{E}_1 &= 12/\underline{0^\circ} \text{ V}; \\ Z_1 &= 5 + j3 \text{ } (\Omega); \\ Z_{L_1} &= j8 \text{ } (\Omega); \\ Z_{L_2} &= j6 \text{ } (\Omega); \\ Z_M &= j6 \text{ } (\Omega); \\ Z_2 &= 5 - j2 \text{ } (\Omega)\end{aligned}$$



Loop-current (branch-current)  
equation system

$$\begin{aligned}(Z_1 + Z_{L_1}) \dot{I}_1 - Z_M \dot{I}_2 &= \dot{E}_1 \\ -Z_M \dot{I}_1 + (Z_2 + Z_{L_2}) \dot{I}_2 &= 0\end{aligned}$$

Substitute values


$$\begin{aligned}(5 + j11) \dot{I}_1 - j6 \dot{I}_2 &= 12/\underline{0^\circ} \\ -j6 \dot{I}_1 + (5 + j4) \dot{I}_2 &= 0\end{aligned}$$



# Methods for Solving Magnetically Coupled Circuits
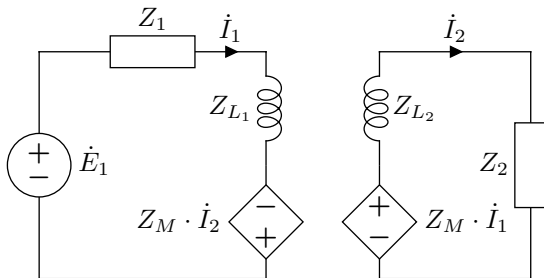
## Example 7.1

$$\begin{aligned}\dot{E}_1 &= 12/\underline{0^\circ} \text{ V}; \\ Z_1 &= 5 + j3 \text{ } (\Omega); \\ Z_{L_1} &= j8 \text{ } (\Omega); \\ Z_{L_2} &= j6 \text{ } (\Omega); \\ Z_M &= j6 \text{ } (\Omega); \\ Z_2 &= 5 - j2 \text{ } (\Omega)\end{aligned}$$



### Currents

$$\begin{aligned}\dot{I}_1 &= 0,9992/\underline{-38,57^\circ} \text{ (A)} \\ \dot{I}_2 &= 0,9363/\underline{12,77^\circ} \text{ (A)}\end{aligned}$$

### Voltages on the coils


$$\begin{aligned}\dot{U}_{L_1} &= Z_{L_1} \dot{I}_1 - Z_M \dot{I}_2 = 6,2728/\underline{7,06^\circ} \text{ (V)} \\ \dot{U}_{L_2} &= Z_{L_2} \dot{I}_2 - Z_M \dot{I}_1 = 5,0419/\underline{170,97^\circ} \text{ (V)}\end{aligned}$$



# Methods for Solving Magnetically Coupled Circuits
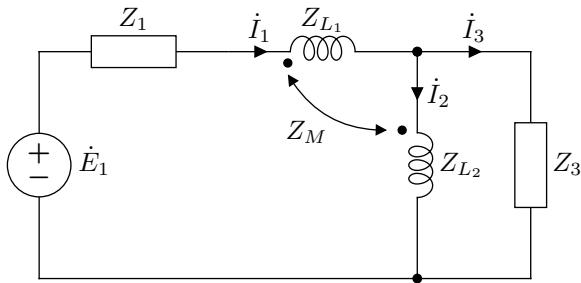
## Example 7.2

$$\begin{aligned}\dot{E}_1 &= 12/\underline{0^\circ} \text{ V}; \\ Z_1 &= 5 + j3 \text{ } (\Omega); \\ Z_{L_1} &= j8 \text{ } (\Omega); \\ Z_{L_2} &= j6 \text{ } (\Omega); \\ Z_M &= j6 \text{ } (\Omega); \\ Z_3 &= 5 - j2 \text{ } (\Omega)\end{aligned}$$



- Determine the sign of the mutual inductance: the mutual-inductance EMF (the  $M$  component) has the same sign as the self-inductance EMF (the  $L$  component)




# Methods for Solving Magnetically Coupled Circuits
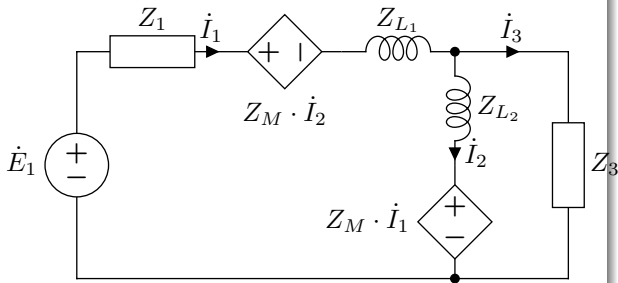
## Example 7.2

Convert to an equivalent CCVS model

$$\begin{aligned}\dot{E}_1 &= 12/\underline{0^\circ} \text{ V}; \\ Z_1 &= 5 + j3 \text{ } (\Omega); \\ Z_{L1} &= j8 \text{ } (\Omega); \\ Z_{L2} &= j6 \text{ } (\Omega); \\ Z_M &= j6 \text{ } (\Omega); \\ Z_3 &= 5 - j2 \text{ } (\Omega)\end{aligned}$$



## Loop-current equation system

$$\begin{aligned}(Z_1 + Z_{L1} + Z_{L2} + 2Z_M)\dot{I}_{V1} - (Z_{L2} + Z_M)\dot{I}_{V2} &= \dot{E}_1 \\ -(Z_{L2} + Z_M)\dot{I}_{V1} + (Z_3 + Z_{L2})\dot{I}_{V2} &= 0\end{aligned}$$




# Methods for Solving Magnetically Coupled Circuits
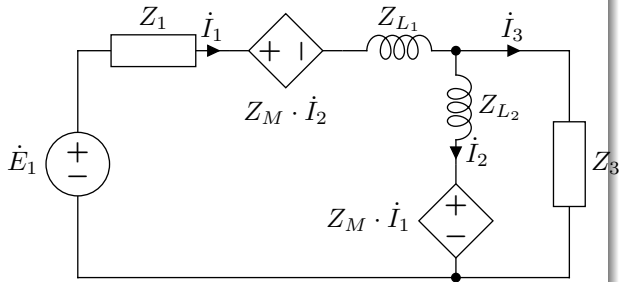
## Example 7.2

Convert to an equivalent CCVS model

$$\begin{aligned}\dot{E}_1 &= 12\angle 0^\circ \text{ V}; \\ Z_1 &= 5 + j3 \text{ } (\Omega); \\ Z_{L_1} &= j8 \text{ } (\Omega); \\ Z_{L_2} &= j6 \text{ } (\Omega); \\ Z_M &= j6 \text{ } (\Omega); \\ Z_3 &= 5 - j2 \text{ } (\Omega)\end{aligned}$$



Substitute values

$$\begin{aligned}(5 + j29) \dot{I}_{V1} - j12 \dot{I}_{V2} &= 12\angle 0^\circ \\ -j12 \dot{I}_{V1} + (5 + j4) \dot{I}_{V2} &= 0\end{aligned}$$

$\Rightarrow$  Loop currents

$$\begin{aligned}\dot{I}_{V1} &= 0,4434\angle -33,53^\circ \text{ (A)} \\ \dot{I}_{V2} &= 0,8309\angle 17,81^\circ \text{ (A)}\end{aligned}$$



# Chapter Outline

- 7 Mutual Inductance and Solving Magnetically Coupled Circuits
  - Mutual-Inductance Phenomenon
  - Methods for Solving Magnetically Coupled Circuits
  - **Mutual-Inductance Power**
  - One-Port Networks Containing Mutual Inductance



# Mutual-Inductance Power


## Return to Example 7.1

$$\dot{I}_1 = 0,9992 / -38,57^\circ \text{ (A)}$$

$$\dot{I}_2 = 0,9363 / 12,77^\circ \text{ (A)}$$

$$\dot{U}_{L_1} = 6,2728 / 7,06^\circ \text{ (V)}$$
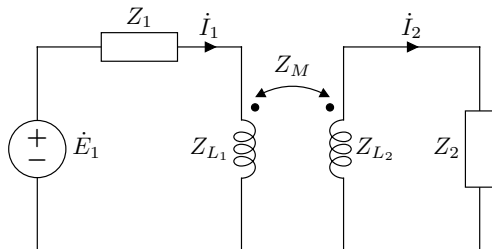
$$\dot{U}_{L_2} = 5,0419 / 170,97^\circ \text{ (V)}$$



Observation: The current and voltage on the coils are not in quadrature

⇒ There is “absorbed” power on magnetically coupled coils

$$P_{L_1} = |\dot{U}_1| \cdot |\dot{I}_1| \cdot \cos \left( \angle \dot{U}_1 - \angle \dot{I}_1 \right) = 4,3828 \text{ (W)}$$

$$P_{L_2} = |\dot{U}_2| \cdot |\dot{I}_2| \cdot \cos \left( \angle \dot{U}_2 - \angle \dot{I}_2 \right) = -4,3828 \text{ (W)}$$




# Mutual-Inductance Power

## Return to Example 7.1

$$P_{L_1} = 4,3828 \text{ (W)}$$

$$P_{L_2} = -4,3828 \text{ (W)}$$

$$P_{Z_2} = -P_{L_2}$$

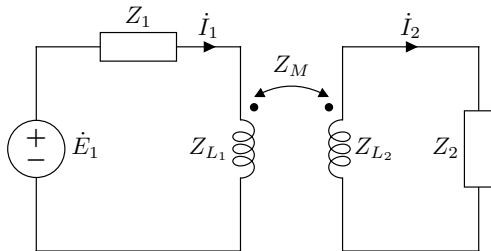

### ⇒ Observation

- The total absorbed power on the two coils is  $P_{L_1} + P_{L_2} = 0$
- Mutual-inductance power is essentially the transfer of energy as a magnetic field between coils at different positions in the circuit
- The coil with  $P > 0$  is **primary**; the coil with  $P < 0$  is **secondary**

# Chapter Outline



- 7 Mutual Inductance and Solving Magnetically Coupled Circuits
  - Mutual-Inductance Phenomenon
  - Methods for Solving Magnetically Coupled Circuits
  - Mutual-Inductance Power
  - One-Port Networks Containing Mutual Inductance



# One-Port Networks Containing Mutual Inductance

- A linear circuit with mutual inductance is still a linear circuit  
 $\Rightarrow$  the Thévenin–Norton theorems still hold
  - Branches with mutual inductance are converted into equivalent diagrams containing dependent sources
- $\Rightarrow$  When computing equivalent impedance, use one of two “indirect” methods (which give the same result):

1. 
$$Z_{\text{eq}} = \frac{\dot{U}_{\text{oc}}}{\dot{I}_{\text{sc}}} = \frac{\dot{E}_{\text{Th}}}{\dot{J}_{\text{N}}}$$


2. Add a source at the port (or determine the transfer function of voltage and current at the port): 
$$Z_{\text{eq}} = \frac{\dot{U}_{\text{port}}}{\dot{I}_{\text{port}}}$$



# One-Port Networks Containing Mutual Inductance
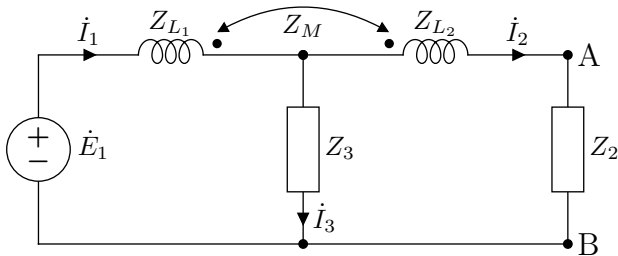
## Example 7.3


Find  $Z_2$  for impedance matching at port AB




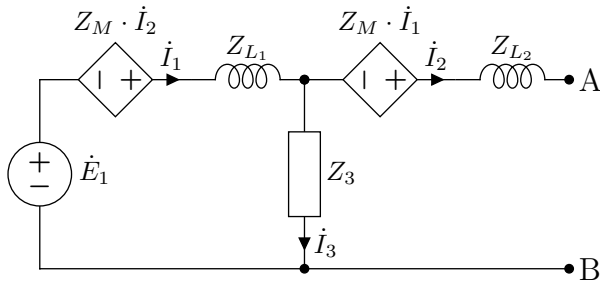
# One-Port Networks Containing Mutual Inductance

⇒ Equivalent model using dependent sources



- Determine  $\dot{U}_{oc}$
- Determine  $\dot{I}_{sc}$
- Determine  $Z_{eq} = \frac{\dot{U}_{oc}}{\dot{I}_{sc}} \Rightarrow$  impedance matching when  $Z_2 = Z_{eq}^*$



# Course Outline

- 1 Concepts of Kirchhoff Circuit Model
- 2 Linear Circuits in Steady State with DC Sources
- 3 Methods for Solving Linear Steady-State DC Circuits
- 4 Linear Circuits in Steady State with Sinusoidal Sources
- 5 Methods for Solving Linear Steady-State AC circuits
- 6 Thévenin–Norton Theorem and One-Port Networks
- 7 Mutual Inductance and Solving Magnetically Coupled Circuits
- 8 Two-Port Networks**
- 9 Circuits with Multiple Frequencies and Non-Sinusoidal Sources
- 10 Three-Phase Circuits



# Chapter Outline

- 8 Two-Port Networks
  - Two-Port Network Models
  - Methods for Determining Two-Port Network Parameters
  - Methods for Solving Circuits with Two-Port Networks
  - Thévenin–Norton for Circuits Containing Two-Port Networks
  - Transfer Function Concept in Electric Circuits
  - Interconnection of Two-Port Networks



# Chapter Outline

8

## Two-Port Networks

- Two-Port Network Models
- Methods for Determining Two-Port Network Parameters
- Methods for Solving Circuits with Two-Port Networks
- Thévenin–Norton for Circuits Containing Two-Port Networks
- Transfer Function Concept in Electric Circuits
- Interconnection of Two-Port Networks




# Two-Port Network Concept

- In many cases, a circuit needs to be divided into connected *subcircuits*.
- These subcircuits are called **networks**, connected through **pairs of nodes**
- Each such *node* is called a **terminal**; a *pair of nodes* forms a **port**
- Networks (subcircuits) interact through *state-variable pairs* of **current** and **voltage** at the ports
- *One-port networks* were studied in Chapter 6
- This chapter considers **two-port networks**
- The concept of a two-port network can be extended to multi-port networks




# Two-Port Network Concept

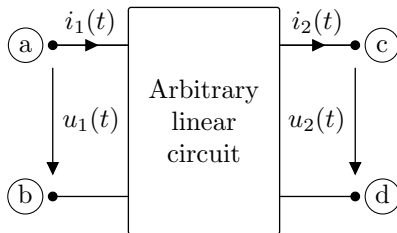

- A two-port network has 2 state-variable pairs:  $u_1, i_1$  and  $u_2, i_2$
- At each port, the current entering one terminal equals the current leaving the other terminal
- Pay attention to the reference directions of current and voltage
- Within the scope of Circuit Theory, we consider only two-port networks without independent sources (but dependent sources)
- The equations for DC and AC two-port networks have similar forms  $\rightarrow$  the lecture gives equations for only one type


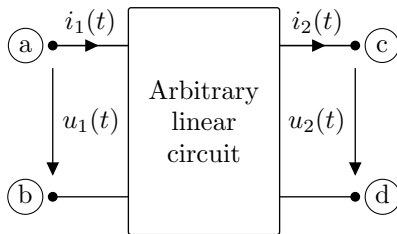
# Characteristic Relations of a Two-Port Network



- Relation of  $u_1, i_1$  in terms of  $u_2, i_2 \rightarrow$  **matrix  $\mathbf{A}$**  (forward transmission)
- Relation of  $u_2, i_2$  in terms of  $u_1, i_1 \rightarrow$  **matrix  $\mathbf{B}$**  (reverse transmission)
- Relation of  $u_1, u_2$  in terms of  $i_1, i_2 \rightarrow$  **matrix  $\mathbf{Z}$**  (impedance)
- Relation of  $i_1, i_2$  in terms of  $u_1, u_2 \rightarrow$  **matrix  $\mathbf{Y}$**  (admittance)
- Relation of  $u_1, i_2$  in terms of  $i_1, u_2 \rightarrow$  **matrix  $\mathbf{H}$**  (forward hybrid)
- Relation of  $i_1, u_2$  in terms of  $u_1, i_2 \rightarrow$  **matrix  $\mathbf{G}$**  (reverse hybrid)



# Parameter Matrices of a Two-Port Network

- They are square matrices of size  $2 \times 2 \rightarrow$  each matrix has 4 parameters to determine
- Circuit Theory often focuses on matrices **A**, **Z**, and **Y** and they match commonly used circuit-solving methods:
  - Matrix **A** is convenient for computing equivalent impedance
  - Matrix **Z** is convenient for the loop analysis
  - Matrix **Y** is convenient for the nodal analysis
  - Note: convenient, but not mandatory
- Example: matrix **A**

$$\begin{cases} \dot{U}_1 = a_{11} \cdot \dot{U}_2 + a_{12} \cdot \dot{I}_2 \\ \dot{I}_1 = a_{21} \cdot \dot{U}_2 + a_{22} \cdot \dot{I}_2 \end{cases}$$

$$\Leftrightarrow \begin{bmatrix} \dot{U}_1 \\ \dot{I}_1 \end{bmatrix} = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \cdot \begin{bmatrix} \dot{U}_2 \\ \dot{I}_2 \end{bmatrix} \Leftrightarrow \begin{bmatrix} \dot{U}_1 \\ \dot{I}_1 \end{bmatrix} = \mathbf{A} \cdot \begin{bmatrix} \dot{U}_2 \\ \dot{I}_2 \end{bmatrix}$$

# Chapter Outline



## 8 Two-Port Networks

- Two-Port Network Models
- **Methods for Determining Two-Port Network Parameters**
- Methods for Solving Circuits with Two-Port Networks
- Thévenin–Norton for Circuits Containing Two-Port Networks
- Transfer Function Concept in Electric Circuits
- Interconnection of Two-Port Networks

# Methods for Determining Two-Port Network Parameters



- The parameter matrices of a two-port network depend only on the network's own circuit structure, not on external quantities

Two common methods for determining two-port network parameters

1. Measure the open-circuit or short-circuit state of one port of the network
2. Given one matrix of the network, determine the remaining matrices



# Open/Short-Circuit Measurement Method

## Matrix **A**

$$\begin{cases} \dot{U}_1 = a_{11} \cdot \dot{U}_2 + a_{12} \cdot \dot{I}_2 \\ \dot{I}_1 = a_{21} \cdot \dot{U}_2 + a_{22} \cdot \dot{I}_2 \end{cases}$$

- Open-circuit port 2

$$\Rightarrow \dot{I}_2 = 0$$

$$a_{11} = \left. \frac{\dot{U}_1}{\dot{U}_2} \right|_{\dot{I}_2=0}$$

$$a_{21} = \left. \frac{\dot{I}_1}{\dot{U}_2} \right|_{\dot{I}_2=0}$$

- Short-circuit port 2

$$\Rightarrow \dot{U}_2 = 0$$

$$a_{12} = \left. \frac{\dot{U}_1}{\dot{I}_2} \right|_{\dot{U}_2=0}$$

$$a_{22} = \left. \frac{\dot{I}_1}{\dot{I}_2} \right|_{\dot{U}_2=0}$$

- $a_{11}$  and  $a_{22}$  are dimensionless
- $a_{12}$  has unit  $\Omega$ ;  $a_{21}$  has unit S



# Open/Short-Circuit Measurement Method

## Matrix $\mathbf{Z}$

$$\begin{cases} \dot{U}_1 = z_{11} \cdot \dot{I}_1 + z_{12} \cdot \dot{I}_2 \\ \dot{U}_2 = z_{21} \cdot \dot{I}_1 + z_{22} \cdot \dot{I}_2 \end{cases}$$

- Open-circuit port 2

$$\Rightarrow \dot{I}_2 = 0$$

$$z_{11} = \left. \frac{\dot{U}_1}{\dot{I}_1} \right|_{\dot{I}_2=0}$$

$$z_{21} = \left. \frac{\dot{U}_2}{\dot{I}_1} \right|_{\dot{I}_2=0}$$

- Open-circuit port 1

$$\Rightarrow \dot{I}_1 = 0$$

$$z_{12} = \left. \frac{\dot{U}_1}{\dot{I}_2} \right|_{\dot{I}_1=0}$$

$$z_{22} = \left. \frac{\dot{U}_2}{\dot{I}_2} \right|_{\dot{I}_1=0}$$

- All parameters of matrix  $\mathbf{Z}$  have unit  $\Omega$



# Open/Short-Circuit Measurement Method

## Matrix $\mathbf{Y}$

$$\begin{cases} \dot{I}_1 = y_{11} \cdot \dot{U}_1 + y_{12} \cdot \dot{U}_2 \\ \dot{I}_2 = y_{21} \cdot \dot{U}_1 + y_{22} \cdot \dot{U}_2 \end{cases}$$

- Short-circuit port 2  
 $\Rightarrow \dot{U}_2 = 0$

$$y_{11} = \left. \frac{\dot{I}_1}{\dot{U}_1} \right|_{\dot{U}_2=0}$$

$$y_{21} = \left. \frac{\dot{I}_2}{\dot{U}_1} \right|_{\dot{U}_2=0}$$

- Short-circuit port 1  
 $\Rightarrow \dot{U}_1 = 0$

$$y_{12} = \left. \frac{\dot{I}_1}{\dot{U}_2} \right|_{\dot{U}_1=0}$$

$$y_{22} = \left. \frac{\dot{I}_2}{\dot{U}_2} \right|_{\dot{U}_1=0}$$

- All parameters of matrix  $\mathbf{Y}$  have unit S



# Matrix Conversion Method

- The structure of a two-port network is uniquely determined
- ⇒ The parameter matrices can be equivalently converted into one another
- It is easy to see:
  - $\mathbf{Y} = \mathbf{Z}^{-1}$
  - $\mathbf{H} = \mathbf{G}^{-1}$
- For other matrices, conversion formulas can be derived
- Example: from  $\mathbf{A}$  to  $\mathbf{Z}$

$$\mathbf{Z} = \begin{bmatrix} \frac{a_{11}}{a_{21}} & -\frac{\det(\mathbf{A})}{a_{21}} \\ \frac{1}{a_{21}} & -\frac{a_{22}}{a_{21}} \end{bmatrix}$$

- For other conversions: consult tables in the references
- ⚠ Note that the reference direction convention for current  $i_2$  in different materials affects the signs of the parameters



# Chapter Outline

8


## Two-Port Networks

- Two-Port Network Models
- Methods for Determining Two-Port Network Parameters
- **Methods for Solving Circuits with Two-Port Networks**
- Thévenin–Norton for Circuits Containing Two-Port Networks
- Transfer Function Concept in Electric Circuits
- Interconnection of Two-Port Networks


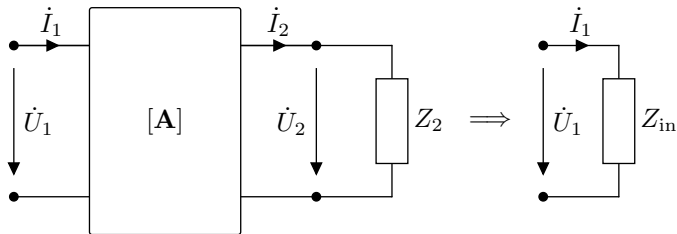
# Equivalent-Impedance Method with Matrix $\mathbf{A}$

- Suitable for circuits with a source at the input port and a load at the output port
  - Procedure:
    - Find the equivalent impedance looking into the input port
    - Use the relation based on  $\mathbf{A} \rightarrow$  convenient for equivalent impedance
- $\Rightarrow$  determine the current-voltage pair at the input port
- $\Rightarrow$  determine the current-voltage pair at the output port




$$Z_{\text{in}} = \frac{\dot{U}_1}{\dot{I}_1} = \frac{a_{11} \cdot \dot{U}_2 + a_{12} \cdot \dot{I}_2}{a_{21} \cdot \dot{U}_2 + a_{22} \cdot \dot{I}_2} \text{ with } \dot{U}_2 = Z_2 \cdot \dot{I}_2 \Rightarrow Z_{\text{in}} = \frac{a_{11} \cdot Z_2 + a_{12}}{a_{21} \cdot Z_2 + a_{22}}$$



# Equivalent-Impedance Method with Matrix $\mathbf{A}$

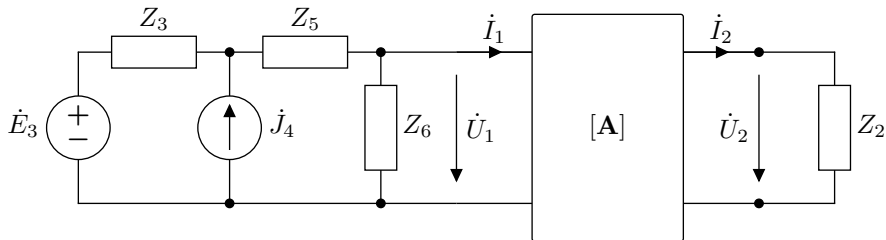
Example 8.1: Determine the current-voltage pairs at the 2 ports





# Loop Analysis with Matrix $\mathbf{Z}$

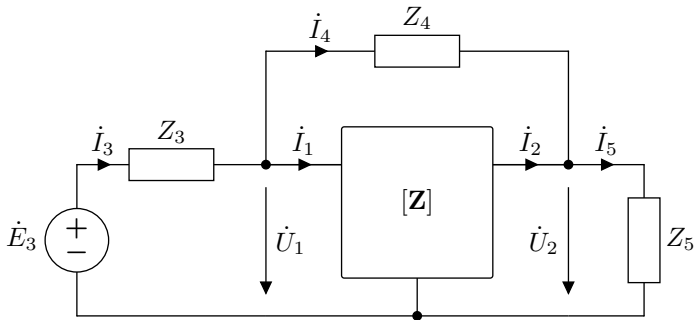
Example 8.2: Determine the current-voltage pairs at the 2 ports





# Nodal Analysis with Matrix $\mathbf{Y}$

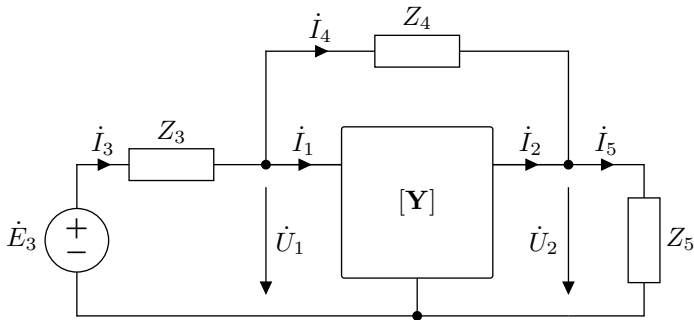
Example 8.3: Determine the current-voltage pairs at the 2 ports





# T and $\Pi$ Equivalent Two-Port Networks
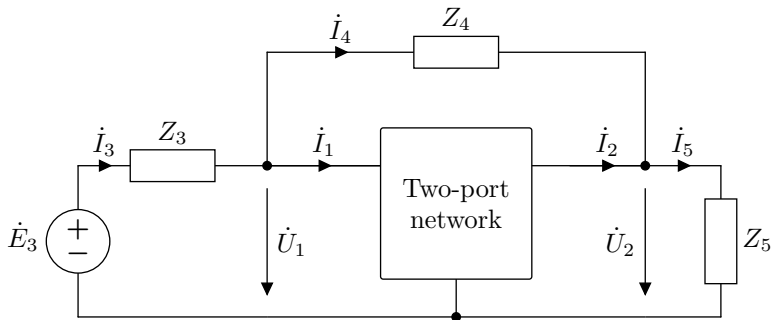
## Equivalent model of a two-port network




- Two-port networks with the same parameter set are equivalent
- ⇒ Equivalent circuit models of two-port networks can be constructed
- Two common models are the T network and the  $\Pi$  network



# T and $\Pi$ Equivalent Two-Port Networks

## T-model of a two-port network

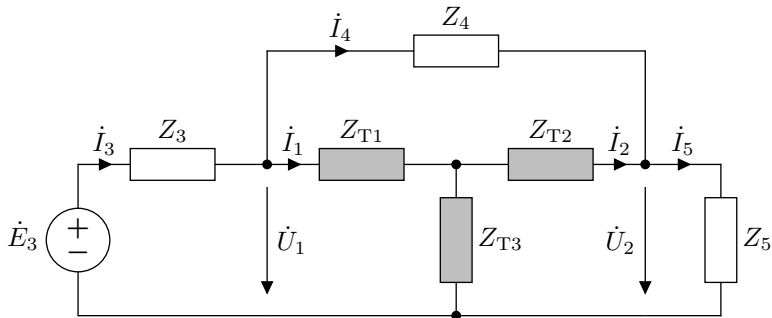


- Determine characteristic matrices from the equivalent impedance set: based on the short-circuit and open-circuit of each port
- ⇒ From there, formulas for equivalent impedances can be derived from the characteristic matrices.



# T and $\Pi$ Equivalent Two-Port Networks

## $\Pi$ -model of a two-port network

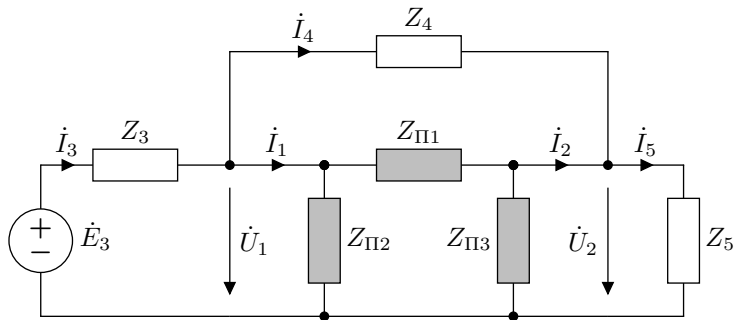

- Similar to the T network
- Other equivalent diagrams also exist

# Chapter Outline



8

## Two-Port Networks


- Two-Port Network Models
- Methods for Determining Two-Port Network Parameters
- Methods for Solving Circuits with Two-Port Networks
- Thévenin–Norton for Circuits Containing Two-Port Networks
- Transfer Function Concept in Electric Circuits
- Interconnection of Two-Port Networks



# One-Port Network Containing a Two-Port Network

- A linear circuit containing a two-port network is also linear  
 $\Rightarrow$  The Thévenin–Norton theorems still hold

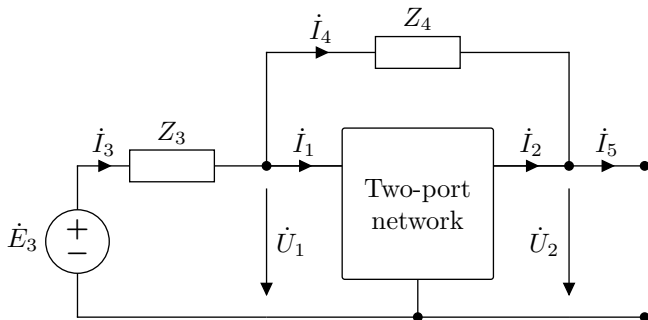Example 8.4: Find the Thévenin–Norton equivalent diagram for network [Y]




⚠ Note: current  $\dot{I}_2$  under this open-circuit condition  $\neq 0$
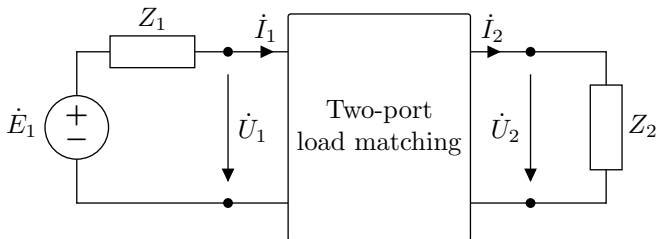
# Using a Two-Port Network for Impedance Matching



- A two-port network can be connected between a source and a load to achieve maximum power transfer
- Procedure: Determine the equivalent impedance, then match the source and load impedances





# Chapter Outline


## 8 Two-Port Networks

- Two-Port Network Models
- Methods for Determining Two-Port Network Parameters
- Methods for Solving Circuits with Two-Port Networks
- Thévenin–Norton for Circuits Containing Two-Port Networks
- **Transfer Function Concept in Electric Circuits**
- Interconnection of Two-Port Networks


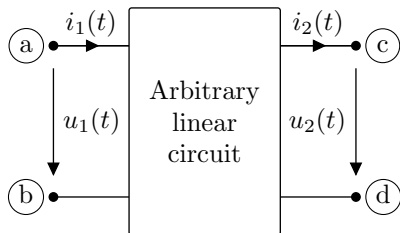
# Transfer Function Concept in Electric Circuits

- So far, characteristic equations have been constructed as relations between current and voltage on elements
  - These relations can be extended to current and voltage state variables at arbitrary positions in the circuit
  - For a linear circuit, these relations are definite and unique
- ⇒ They are called **linear relations** between state variables
- ⇒ The ratio between state variables is called a **transfer function**



- Voltage transfer function  $k_u = \frac{u_2}{u_1}$
- Current transfer function:  $k_i = \frac{i_2}{i_1}$
- Impedance transfer function  $k_Z = \frac{u_2}{i_1}$  and admittance transfer function  $k_Y = \frac{i_2}{u_1}$



# Chapter Outline

8


## Two-Port Networks

- Two-Port Network Models
- Methods for Determining Two-Port Network Parameters
- Methods for Solving Circuits with Two-Port Networks
- Thévenin–Norton for Circuits Containing Two-Port Networks
- Transfer Function Concept in Electric Circuits
- Interconnection of Two-Port Networks



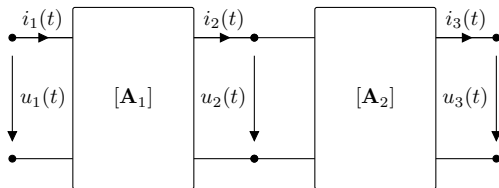
# Cascaded Two-Port Networks

For cascade connection, matrix  $\mathbf{A}$  is the most convenient


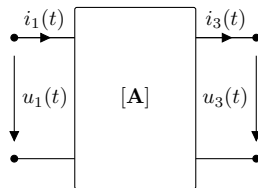
$$\Rightarrow \mathbf{A} = \mathbf{A}_1 \cdot \mathbf{A}_2$$




- They share the current and voltage at the connected port



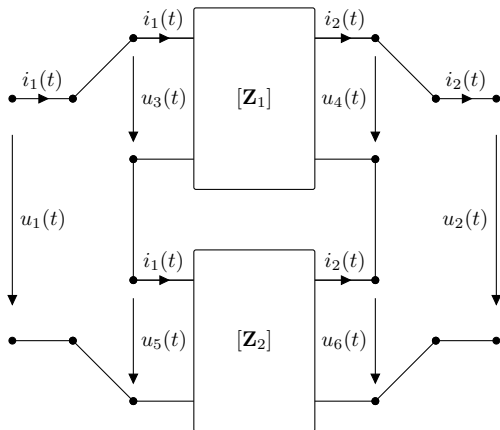
# Series-Connected Two-Port Networks

For series connection, matrix  $\mathbf{Z}$  is the most convenient


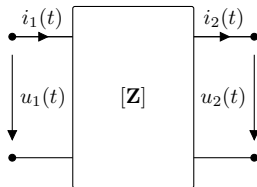
$$\Rightarrow \mathbf{Z} = \mathbf{Z}_1 + \mathbf{Z}_2$$



At each port:


- Common current
- Voltage equals the algebraic sum of voltages

$\Rightarrow$  This is called series connection



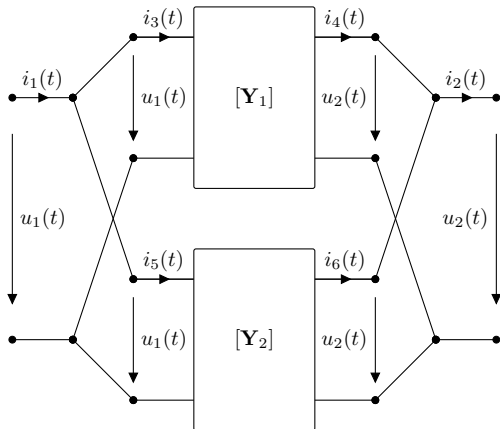
# Parallel-Connected Two-Port Networks

For parallel connection, matrix  $\mathbf{Y}$  is the most convenient


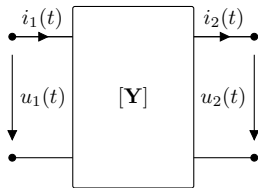
$$\Rightarrow \mathbf{Y} = \mathbf{Y}_1 + \mathbf{Y}_2$$



At each port:

- Common voltage
- Current equals the algebraic sum of currents

$\Rightarrow$  This is called parallel connection



# Course Outline

- 1 Concepts of Kirchhoff Circuit Model
- 2 Linear Circuits in Steady State with DC Sources
- 3 Methods for Solving Linear Steady-State DC Circuits
- 4 Linear Circuits in Steady State with Sinusoidal Sources
- 5 Methods for Solving Linear Steady-State AC circuits
- 6 Thévenin–Norton Theorem and One-Port Networks
- 7 Mutual Inductance and Solving Magnetically Coupled Circuits
- 8 Two-Port Networks
- 9 Circuits with Multiple Frequencies and Non-Sinusoidal Sources**
- 10 Three-Phase Circuits



# Chapter Outline

- 9 Circuits with Multiple Frequencies and Non-Sinusoidal Sources
  - Applying the Superposition Principle in Multi-Frequency Circuits
  - Power in Multi-Frequency Circuits
  - Circuits with Non-Sinusoidal Sources – Fourier Method
  - Frequency Response of Transfer Functions – Electric Filters

# Chapter Outline



- 9 Circuits with Multiple Frequencies and Non-Sinusoidal Sources
  - Applying the Superposition Principle in Multi-Frequency Circuits
  - Power in Multi-Frequency Circuits
  - Circuits with Non-Sinusoidal Sources – Fourier Method
  - Frequency Response of Transfer Functions – Electric Filters



# Circuits with Multiple Frequencies

## Circuits with multiple frequencies

- So far, we have considered DC circuits (which can be regarded as  $f = 0$ ) and AC circuits whose sources have the same frequency
- In many cases, sources in a circuit may have different frequencies

## Problem

- The phasor method can only be used for AC circuits whose sources have the same frequency


## Solution

- Solve the circuit for each frequency in turn by suppressing sources with other frequencies (short-circuit voltage sources, open-circuit current sources)
- Superpose the solutions *in the time domain*



# Circuits with Multiple Frequencies

Example 9.1: Determine current  $i_3(t)$

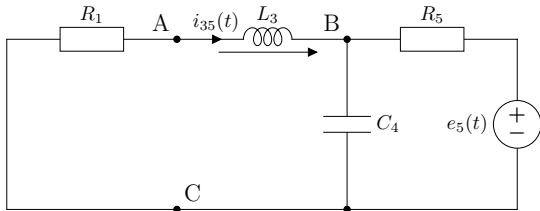

$$\begin{aligned}
 E_1 &= 15 \text{ V}; R_1 = 10 \Omega; \\
 j_2(t) &= \sqrt{2} \sin(5t + 15^\circ) \text{ A}; \\
 L_3 &= 1 \text{ H}; C_4 = 0,02 \text{ F}; \\
 R_5 &= 5 \Omega; \\
 e_5(t) &= 12\sqrt{2} \sin(10t + 30^\circ) \text{ V}
 \end{aligned}$$


Solution

- $i_3(t) = i_{31}(t) + i_{32}(t) + i_{35}(t)$
- $i_{31}(t)$  is the current through  $L_3$  when only  $E_1$  on,  $j_2(t)$  and  $e_5(t)$  off
- $i_{32}(t)$  is the current through  $L_3$  when only  $j_2(t)$  on,  $E_1$  and  $e_5(t)$  off
- $i_{35}(t)$  is the current through  $L_3$  when only  $e_5(t)$  on,  $j_2(t)$  and  $E_1$  off




# Circuits with Multiple Frequencies

Example 9.1: Determine current  $i_3(t)$

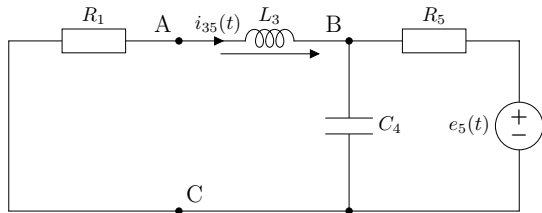
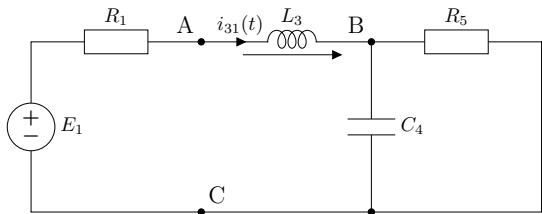
$$\begin{aligned} E_1 &= 15 \text{ V}; R_1 = 10 \Omega; \\ j_2(t) &= \sqrt{2} \sin(5t + 15^\circ) \text{ A}; \\ L_3 &= 1 \text{ H}; C_4 = 0,02 \text{ F}; \\ R_5 &= 5 \Omega; \\ e_5(t) &= 12\sqrt{2} \sin(10t + 30^\circ) \text{ V} \end{aligned}$$




Component  $i_{31}(t) = I_{31}$

$$I_{31} = \frac{E_1}{R_1 + R_5} = 1 \text{ A}$$




# Circuits with Multiple Frequencies

Example 9.1: Determine current  $i_3(t)$

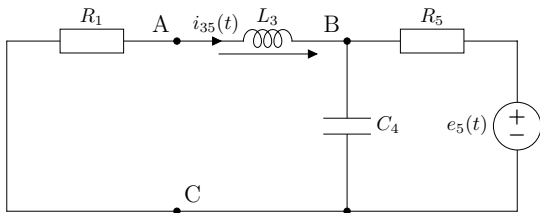
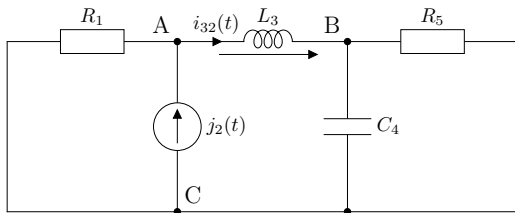
$$\begin{aligned} E_1 &= 15 \text{ V}; R_1 = 10 \Omega; \\ j_2(t) &= \sqrt{2} \sin(5t + 15^\circ) \text{ A}; \\ L_3 &= 1 \text{ H}; C_4 = 0,02 \text{ F}; \\ R_5 &= 5 \Omega; \\ e_5(t) &= 12\sqrt{2} \sin(10t + 30^\circ) \text{ V} \end{aligned}$$



Component  $i_{32}(t)$

Convert the circuit to the complex domain

$$Z_{L_3} = j\omega_2 L_3 = j5 \Omega$$


$$Z_{C_4} = \frac{1}{j\omega_2 C_4} = -j10 \Omega$$

determine  $i_{32}(t) = \dots$




# Circuits with Multiple Frequencies

Example 9.1: Determine current  $i_3(t)$

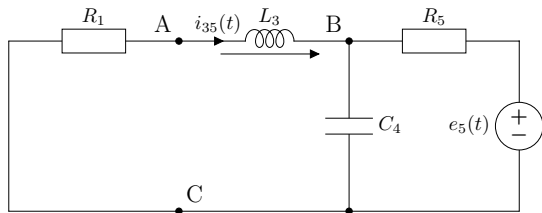
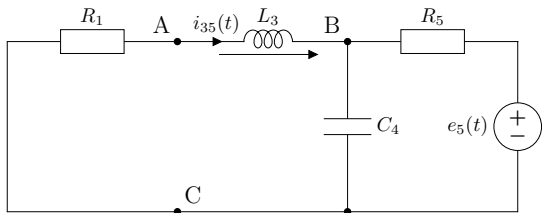
$$\begin{aligned} E_1 &= 15 \text{ V}; R_1 = 10 \Omega; \\ j_2(t) &= \sqrt{2} \sin(5t + 15^\circ) \text{ A}; \\ L_3 &= 1 \text{ H}; C_4 = 0,02 \text{ F}; \\ R_5 &= 5 \Omega; \\ e_5(t) &= 12\sqrt{2} \sin(10t + 30^\circ) \text{ V} \end{aligned}$$



Component  $i_{35}(t)$

Convert the circuit to the complex domain

$$Z_{L_3} = j\omega_5 L_3 = j10 \Omega$$

$$Z_{C_4} = \frac{1}{j\omega_5 C_4} = -j5 \Omega$$

determine  $i_{35}(t) = \dots$




# Chapter Outline

- 9 Circuits with Multiple Frequencies and Non-Sinusoidal Sources
  - Applying the Superposition Principle in Multi-Frequency Circuits
  - **Power in Multi-Frequency Circuits**
  - Circuits with Non-Sinusoidal Sources – Fourier Method
  - Frequency Response of Transfer Functions – Electric Filters


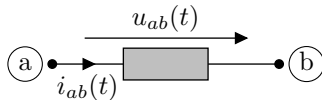
# Review: Instantaneous Power and Average Power



- Instantaneous absorbed power:

$$p(t) = u_{ab}(t) \cdot i_{ab}(t)$$

- Instantaneous supplied power:

$$p_{\text{sup}}(t) = -p(t) = u_{ba}(t) \cdot i_{ab}(t) = u_{ab}(t) \cdot i_{ba}(t)$$

- Average power is the average value of instantaneous power

$$P = \frac{1}{T} \int_0^T p(t) \cdot dt$$



# Power in Multi-Frequency Circuits

- When current and voltage quantities have multiple frequency components

$$u(t) = U_0 + U_1 \sin(\omega_1 t + \varphi_1) + U_2 \sin(\omega_2 t + \varphi_2) + \dots$$

$$i(t) = I_0 + I_1 \sin(\omega_1 t + \theta_1) + I_2 \sin(\omega_2 t + \theta_2) + \dots$$

- Instantaneous power:

$$\begin{aligned} p(t) = u(t) \cdot i(t) &= U_0 I_0 + \sum_i U_i I_i \sin(\omega_i t + \varphi_i) \sin(\omega_i t + \theta_i) \\ &+ \sum_{i \neq j} U_i I_j \sin(\omega_i t + \varphi_i) \sin(\omega_j t + \theta_j) \end{aligned}$$



# Power in Multi-Frequency Circuits

- Instantaneous power:

$$p(t) = u(t) \cdot i(t) = U_0 I_0 + \sum_i U_i I_i \sin(\omega_i t + \varphi_i) \sin(\omega_i t + \theta_i) \\ + \sum_{i \neq j} U_i I_j \sin(\omega_i t + \varphi_i) \sin(\omega_j t + \theta_j)$$

- Average power:

$$P = \frac{1}{T} \int_0^T p(t) dt = U_0 I_0 + \sum_i \frac{1}{T} \int_0^T (U_i I_i \sin(\omega_i t + \varphi_i) \sin(\omega_i t + \theta_i)) dt \\ + \sum_{i \neq j} \frac{1}{T} \int_0^T (U_i I_j \sin(\omega_i t + \varphi_i) \sin(\omega_j t + \theta_j)) dt \\ = U_0 I_0 + \sum_i \frac{U_i I_i}{2} \cos(\varphi_i - \theta_i) + 0 = P_{DC} + \sum_i P_{\omega_i}$$



# RMS Value in Multi-Frequency Circuits

- $u(t) = U_0 \rightarrow U_{\text{rms}} = U_0$
- $u(t) = U_1 \sin(\omega_1 t + \varphi_1) \rightarrow U_{\text{rms}} = \frac{U_1}{\sqrt{2}}$
- $u(t) = U_0 + U_1 \sin(\omega_1 t + \varphi_1) + U_2 \sin(\omega_2 t + \varphi_2) + \dots$   
 $\rightarrow U_{\text{rms}} = \sqrt{\left( U_0^2 + \frac{U_1^2}{2} + \frac{U_2^2}{2} + \dots \right)}$

⚠ Note: in multi-frequency circuits, average power must not be determined from RMS current and voltage values

$$P_{\text{avg}} \neq U_{\text{rms}} \cdot I_{\text{rms}}$$



# Chapter Outline

- 9 Circuits with Multiple Frequencies and Non-Sinusoidal Sources
  - Applying the Superposition Principle in Multi-Frequency Circuits
  - Power in Multi-Frequency Circuits
  - Circuits with Non-Sinusoidal Sources – Fourier Method
  - Frequency Response of Transfer Functions – Electric Filters




# Circuits with Non-Sinusoidal Sources
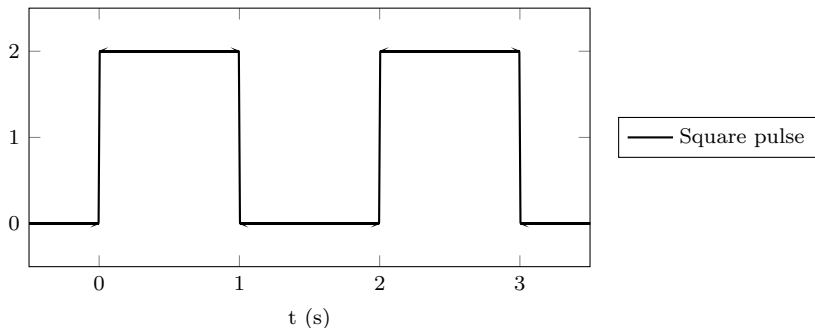
## Example 9.2: Fourier expansion of a square pulse

- Given a square voltage pulse with amplitude 1 V, period 1 s, and offset 1 V

$$u(t) = 1 + \frac{1}{4\pi} \sum_{n=1}^{\infty} \frac{\sin(n\pi t)}{n} \text{ for odd } n$$






# Circuits with Non-Sinusoidal Sources

## Example 9.2: Fourier expansion of a square pulse

- DC component (order 0)

$$u(t) = 1$$

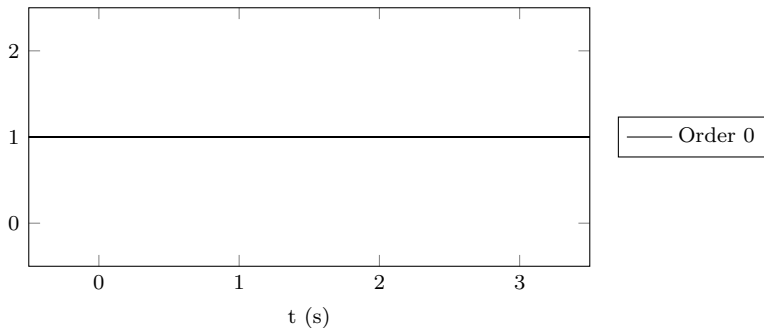




# Circuits with Non-Sinusoidal Sources
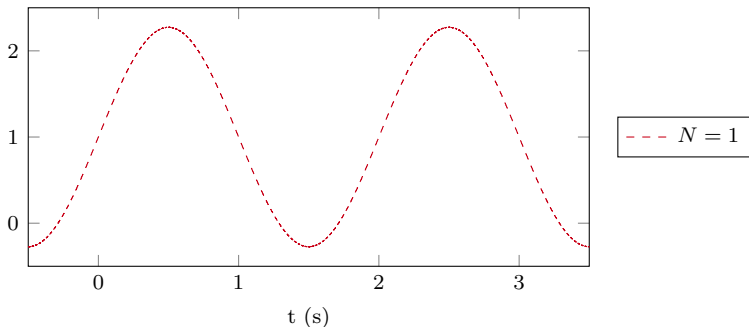
## Example 9.2: Fourier expansion of a square pulse

- Expansion up to the 1st harmonic component

$$u(t) = 1 + \frac{1}{4\pi} \sin(\pi t)$$






# Circuits with Non-Sinusoidal Sources
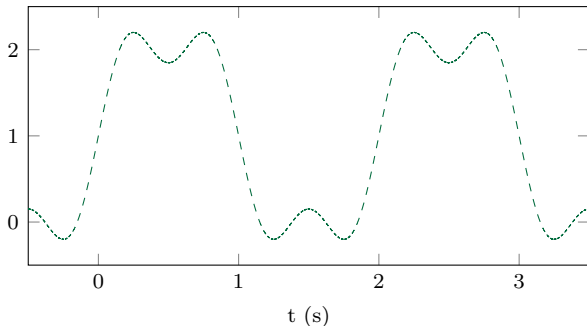
## Example 9.2: Fourier expansion of a square pulse

- Expansion up to the 3rd harmonic component

$$u(t) = 1 + \frac{1}{4\pi} \sin(\pi t) + \frac{1}{4\pi} \frac{\sin(3\pi t)}{3}$$






# Circuits with Non-Sinusoidal Sources
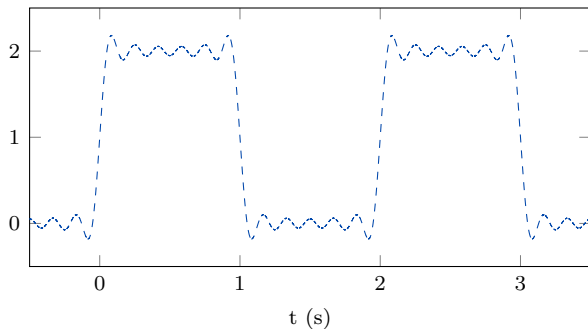
## Example 9.2: Fourier expansion of a square pulse

- Expansion up to the 11th harmonic component

$$u(t) = 1 + \frac{1}{4\pi} \sum_{n=1}^{11} \frac{\sin(n\pi t)}{n} \text{ for odd } n$$






# Circuits with Non-Sinusoidal Sources
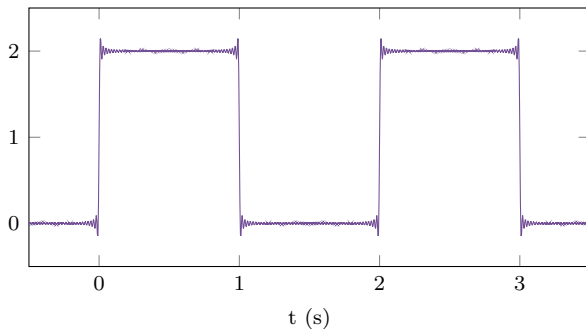
## Example 9.2: Fourier expansion of a square pulse

- Expansion up to the 101st harmonic component

$$u(t) = 1 + \frac{1}{4\pi} \sum_{n=1}^{101} \frac{\sin(n\pi t)}{n} \text{ for odd } n$$






# Circuits with Non-Sinusoidal Sources
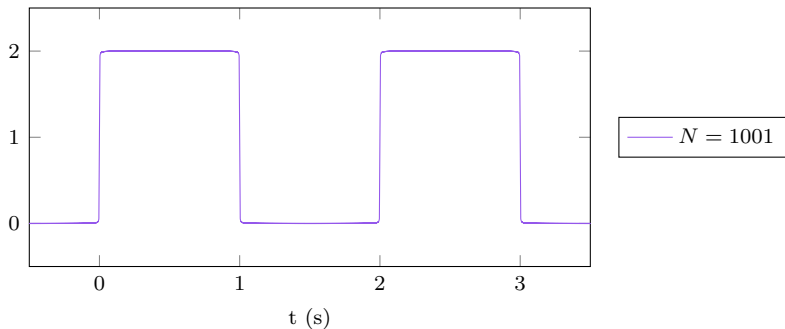
## Example 9.2: Fourier expansion of a square pulse

- Expansion up to the 1001st harmonic component


$$u(t) = 1 + \frac{1}{4\pi} \sum_{n=1}^{1001} \frac{\sin(n\pi t)}{n} \text{ for odd } n$$





# Circuits with Non-Sinusoidal Sources
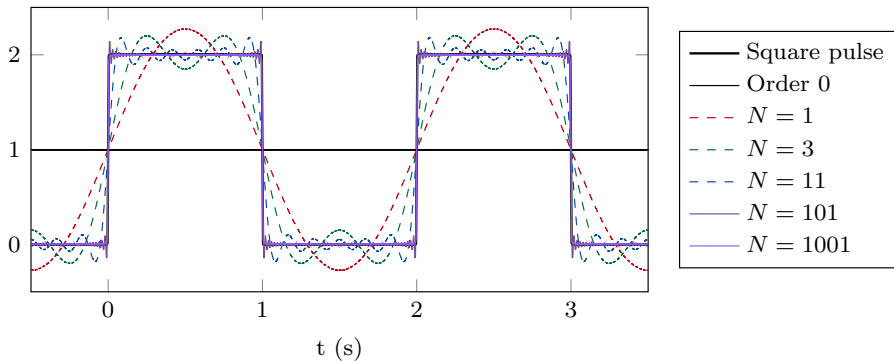
## Example 9.2: Fourier expansion of a square pulse



- Exercise: Determine the expansions of other periodic signals such as triangular waves, sawtooth waves, etc.

# Chapter Outline



- 9 Circuits with Multiple Frequencies and Non-Sinusoidal Sources
  - Applying the Superposition Principle in Multi-Frequency Circuits
  - Power in Multi-Frequency Circuits
  - Circuits with Non-Sinusoidal Sources – Fourier Method
  - Frequency Response of Transfer Functions – Electric Filters




# Frequency Response of Transfer Functions

- A transfer function is a proportional relation between current-voltage state variables in a circuit
- ⇒ The transfer function is formed from the circuit impedances
- Capacitors and inductors have different complex impedances at different frequencies in the circuit
- ⇒ The transfer function is a complex function whose magnitude and phase characteristics depend on frequency
- ⇒ The concept of **frequency–magnitude–phase response** of a transfer function

# Frequency Response of Transfer Functions

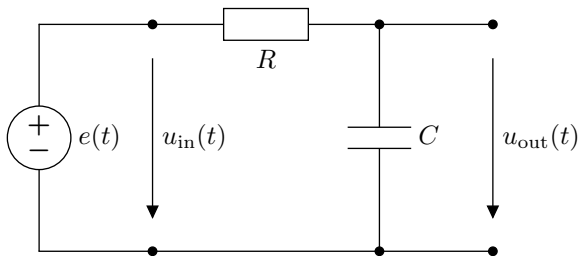
Example 9.3: Consider the voltage transfer function of an  $RC$  circuit



$$\begin{aligned} H(j\omega) &= \frac{\dot{U}_{\text{out}}}{\dot{U}_{\text{in}}} = \frac{Z_C}{R + Z_C} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \\ &= \frac{1}{j\omega RC + 1} \end{aligned}$$

# Frequency Response of Transfer Functions

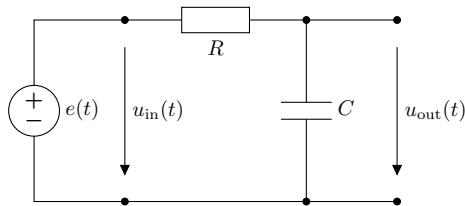Example 9.3: Consider the voltage transfer function of an  $RC$  circuit



- Set  $RC = \frac{1}{\omega_c}$
- $\omega_c$  is called the *cutoff frequency*

$$\Rightarrow H(j\omega) = \frac{1}{j\frac{\omega}{\omega_c} + 1}$$


- Magnitude response  $|H(j\omega)| = \frac{1}{\sqrt{\left(\frac{\omega}{\omega_c}\right)^2 + 1}}$

- Phase response  $\angle H(j\omega) = \angle 1 - \angle j\frac{\omega}{\omega_c} + 1 = -\arctan\left(\frac{\omega}{\omega_c}\right)$


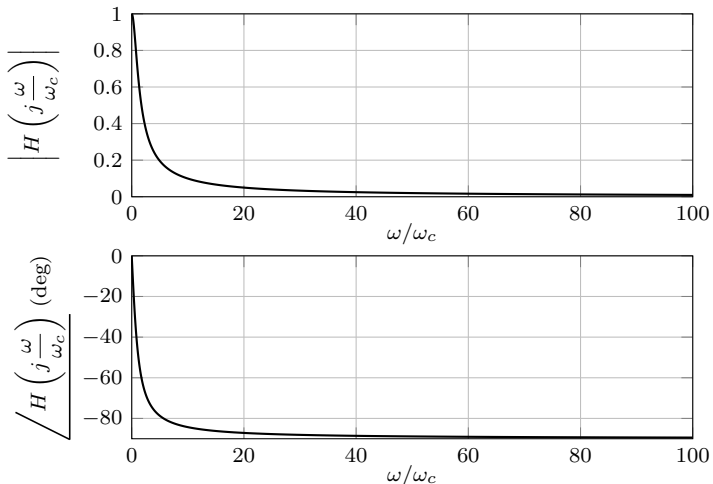
# Frequency Response of Transfer Functions

Both the plot and the formulas are inconvenient





# Frequency Response of Transfer Functions

## Decibel magnitude (dB) and logarithmic frequency scale


- The log function is convenient because it converts multiplication and division into addition and subtraction → operations can be performed directly on the plot
  - A logarithmic scale makes frequency plots easier to read than a linear scale
- ⇒ The dB magnitude of the magnitude response is defined as
- $$20 \log_{10}(|H(j\omega)|)^*$$
- ⇒ A plot in dB and on a log scale is called a **Bode plot**

---

The choice of unit and formula is historical. Initially, the bel was named to recognize telephone inventor Alexander Graham Bell. This unit is the base-10 logarithm of the ratio between two powers:  $\log_{10}(P_2/P_1)$  bels =  $10 \log_{10}(P_2/P_1)$  decibels. Meanwhile, signal power is proportional to the square of signal amplitude →  $10 \log_{10}(P_2/P_1) = 10 \log_{10}(|H(j\omega)|^2) = 20 \log_{10}(|H(j\omega)|)$  dB. (Lathi, Linear Systems and Signals)

# Frequency Response of Transfer Functions
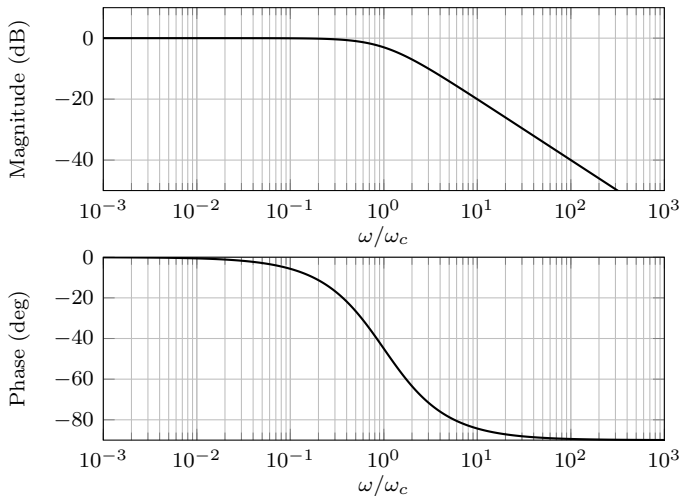
## Bode plot of a first-order $RC$ low-pass filter





# Course Outline

- 1 Concepts of Kirchhoff Circuit Model
- 2 Linear Circuits in Steady State with DC Sources
- 3 Methods for Solving Linear Steady-State DC Circuits
- 4 Linear Circuits in Steady State with Sinusoidal Sources
- 5 Methods for Solving Linear Steady-State AC circuits
- 6 Thévenin–Norton Theorem and One-Port Networks
- 7 Mutual Inductance and Solving Magnetically Coupled Circuits
- 8 Two-Port Networks
- 9 Circuits with Multiple Frequencies and Non-Sinusoidal Sources
- 10 Three-Phase Circuits**



# Chapter Outline

- 10 Three-Phase Circuits
  - Three-Phase Circuit Concept
  - Balanced Three-Phase Circuits
  - Unbalanced Three-Phase Circuits





# Chapter Outline

- 10 Three-Phase Circuits
  - Three-Phase Circuit Concept
  - Balanced Three-Phase Circuits
  - Unbalanced Three-Phase Circuits


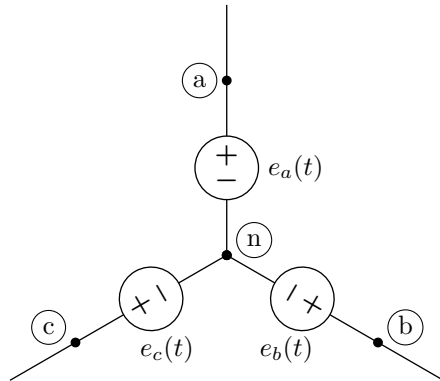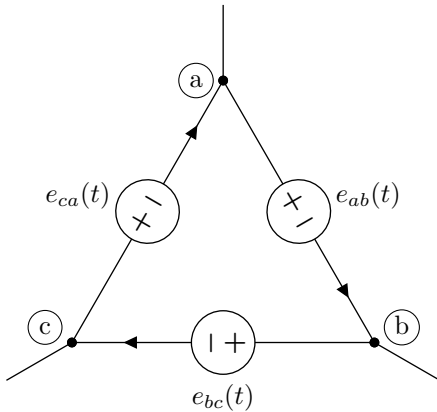
# Three-Phase Circuit Concept



- A three-phase source system is a set of 3 AC voltage sources with phase shifts
- A three-phase source set can be connected in wye (Y) or delta ( $\Delta$ )




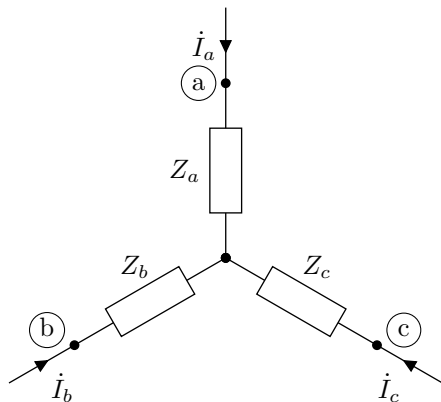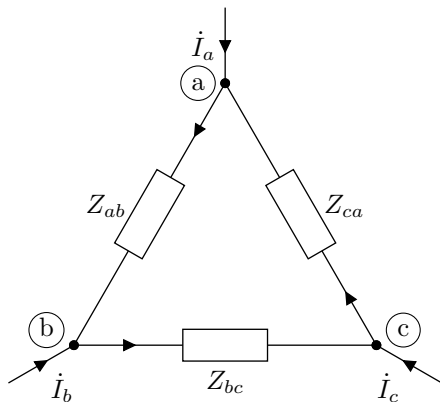
# Three-Phase Circuit Concept


- A three-phase load can also be connected in wye (Y) or delta ( $\Delta$ )




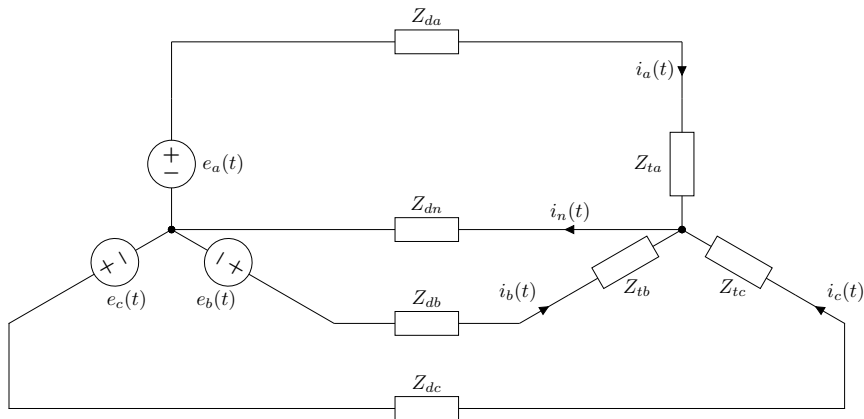
# Three-Phase Circuit Concept


- When connecting source and load, line impedance can be considered
- A neutral wire can be connected





# Three-Phase Circuit Concept

- Or the neutral wire can be omitted

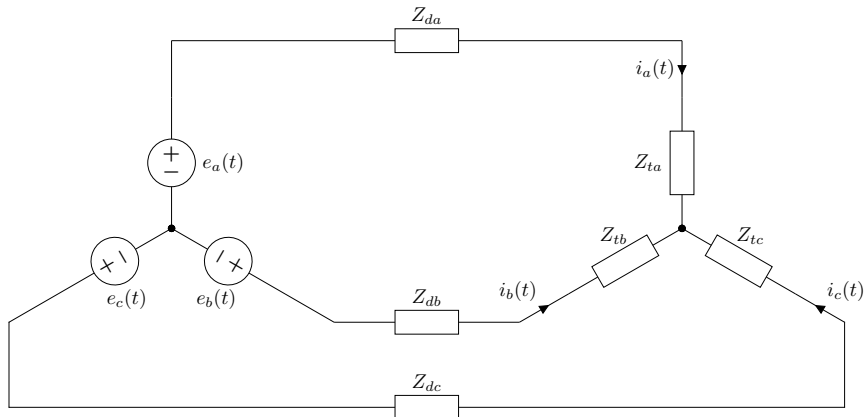

- And other three-phase circuit connections



# Chapter Outline

- 10 Three-Phase Circuits
  - Three-Phase Circuit Concept
  - **Balanced Three-Phase Circuits**
  - Unbalanced Three-Phase Circuits





# Balanced Three-Phase Circuits

- Balanced load:  $Z_{ta} = Z_{tb} = Z_{tc}$
- Balanced line:  $Z_{da} = Z_{db} = Z_{dc}$
- Balanced source: equal amplitudes and phase shifts of  $120^\circ$
- Let  $a = 1/\underline{-120^\circ}$  be the  $-120^\circ$  rotation operator


$$\Rightarrow \dot{U}_{bn} = a \cdot \dot{U}_{an}; \dot{U}_{cn} = a \cdot \dot{U}_{bn} = a^2 \cdot \dot{U}_{an}; \dot{U}_{an} = a \cdot \dot{U}_{cn}$$
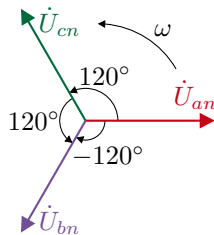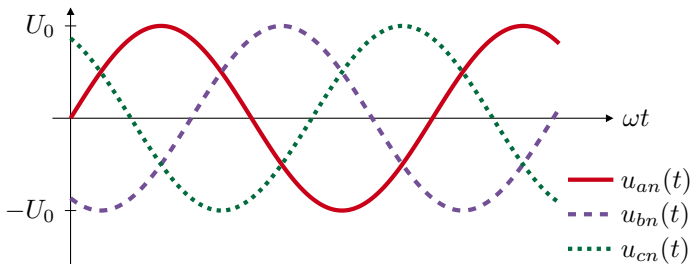
$$\Rightarrow \dot{U}_{an} + \dot{U}_{bn} + \dot{U}_{cn} = (1 + a + a^2) \cdot \dot{U}_{an} = 0$$





# Solving Three-Phase Circuits

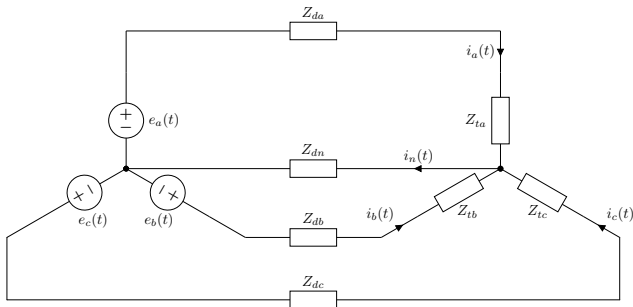

- Case with a neutral wire  $\rightarrow$  Nodal Analysis

$$\begin{aligned} \dot{V} \left( \frac{1}{Z_{ta} + Z_{da}} + \frac{1}{Z_{tb} + Z_{db}} + \frac{1}{Z_{tc} + Z_{dc}} + \frac{1}{Z_{dn}} \right) \\ = \frac{\dot{E}_a}{Z_{ta} + Z_{da}} + \frac{\dot{E}_b}{Z_{tb} + Z_{db}} + \frac{\dot{E}_c}{Z_{tc} + Z_{dc}} \end{aligned}$$




# Solving Three-Phase Circuits

Define phase impedances

$$Z_a = Z_{ta} + Z_{da}$$

$$Z_b = Z_{tb} + Z_{db}$$

$$Z_c = Z_{tc} + Z_{dc}$$

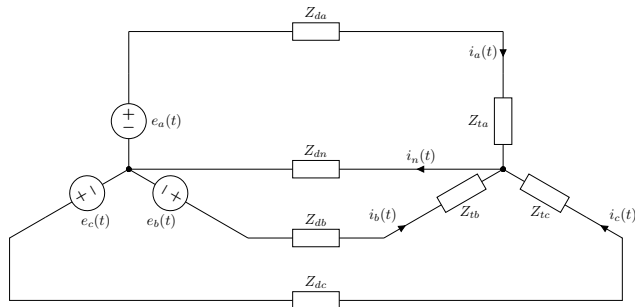

⇒ Node potential

$$\dot{V} = \frac{\frac{\dot{E}_a}{Z_a} + \frac{\dot{E}_b}{Z_b} + \frac{\dot{E}_c}{Z_c}}{\frac{1}{Z_a} + \frac{1}{Z_b} + \frac{1}{Z_c} + \frac{1}{Z_n}}$$



# Solving Balanced Three-Phase Circuits

- Balanced three-phase circuit

$$Z_a = Z_b = Z_c$$

$$\dot{E}_a + \dot{E}_b + \dot{E}_c = 0$$

$$\Rightarrow \dot{V} = \frac{\frac{\dot{E}_a}{Z_a} + \frac{\dot{E}_b}{Z_b} + \frac{\dot{E}_c}{Z_c}}{\frac{1}{Z_a} + \frac{1}{Z_b} + \frac{1}{Z_c} + \frac{1}{Z_n}} = 0$$

$$\Rightarrow \dot{I}_a = \frac{\dot{E}_a}{Z_a}; \dot{I}_b = \frac{\dot{E}_b}{Z_b}; \dot{I}_c = \frac{\dot{E}_c}{Z_c}; \dot{I}_n = 0$$

- Balanced three-phase currents

$$\dot{I}_b = a \cdot \dot{I}_a; \dot{I}_c = a \cdot \dot{I}_b = a^2 \cdot \dot{I}_a; \dot{I}_a = a \cdot \dot{I}_c$$

- Balanced three-phase load voltages

$$\dot{U}_{tb} = a \cdot \dot{U}_{ta}; \dot{U}_{tc} = a \cdot \dot{U}_{tb} = a^2 \cdot \dot{U}_{ta}; \dot{U}_{ta} = a \cdot \dot{U}_{tc}$$

$$\text{with } a = 1/\underline{-120^\circ}$$



# Power in Balanced Three-Phase Circuits

- Load power

$$\begin{aligned}
 P_{ta} &= |\dot{U}_{ta}| \cdot |\dot{I}_{ta}| \cdot \cos \left( \angle \dot{U}_{ta} - \angle \dot{I}_{ta} \right) \\
 &= |\dot{U}_{tb}| \cdot |\dot{I}_{tb}| \cdot \cos \left( \left( \angle \dot{U}_{tb} + 120^\circ \right) - \left( \angle \dot{I}_{tb} + 120^\circ \right) \right) \\
 &= |\dot{U}_{tb}| \cdot |\dot{I}_{tb}| \cdot \cos \left( \angle \dot{U}_{tb} - \angle \dot{I}_{tb} \right) \\
 &= P_{tb} = P_{tc}
 \end{aligned}$$

⇒ The absorbed power of the load on each phase is equal

⇒ Similarly, the supplied power of the source on each phase is equal

- The total instantaneous power at every instant is constant

$$P = 3 \cdot U_{\text{rms}} \cdot I_{\text{rms}} \cdot \cos(\varphi - \theta) = \frac{3}{2} \cdot U_0 \cdot I_0 \cdot \cos(\varphi - \theta)$$

where  $\varphi$  and  $\theta$  are the angles of voltage and current on each phase



# Chapter Outline

- 10 Three-Phase Circuits
  - Three-Phase Circuit Concept
  - Balanced Three-Phase Circuits
  - Unbalanced Three-Phase Circuits



# Unbalanced Three-Phase Circuits

- A three-phase circuit whose source or load is unbalanced in amplitude or phase angle
- Solution methods
  - Direct solution
  - Symmetrical-component method
- Extend the concept of a balanced three-phase system: complex coefficient  $k$  satisfies

$$\dot{E}_b = k \cdot \dot{E}_a; \dot{E}_c = k \cdot \dot{E}_b; \dot{E}_a = k \cdot \dot{E}_c$$

⇒ there are 3 solutions:  $k_0 = 1$ ;  $k_1 = a$ ;  $k_2 = a^2$


- Corresponding to 3 symmetrical three-phase systems
  1. Positive sequence  $k_1 = a = 1/\underline{-120^\circ}$   
(clockwise → opposite to the conventional positive direction)
  2. Negative sequence  $k_2 = a^2 = 1/\underline{120^\circ}$   
(counterclockwise → same as the conventional positive direction)
  3. Zero sequence  $k_0 = 1$  (no rotation)




# Unbalanced Three-Phase Circuits

## Symmetrical-component method


### • Positive sequence

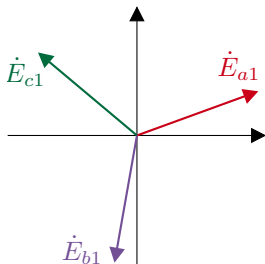

### • Negative sequence

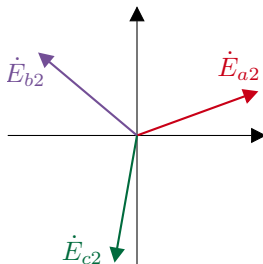

### • Zero sequence

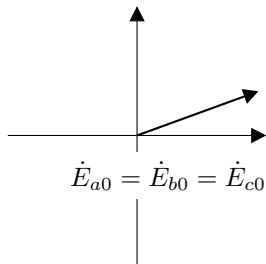

- An unbalanced three-phase source system is the superposition of 3 symmetrical source components

⇒ Solve 3 equations in 3 unknowns to find the 3 symmetrical components



# Symmetrical-Component Method

- For any unbalanced source set  $\dot{E}_a; \dot{E}_b; \dot{E}_c$ , there exists a source set of symmetrical components  $\dot{E}_{a0}; \dot{E}_{a1}; \dot{E}_{a2}$  such that:

$$\dot{E}_a = \dot{E}_{a0} + \dot{E}_{a1} + \dot{E}_{a2} \quad = \dot{E}_{a0} + \dot{E}_{a1} + \dot{E}_{a2}$$

$$\dot{E}_b = \dot{E}_{a0} + k_1 \cdot \dot{E}_{a1} + k_2 \cdot \dot{E}_{a2} \quad = \dot{E}_{b0} + \dot{E}_{b1} + \dot{E}_{b2}$$

$$\dot{E}_c = \dot{E}_{a0} + k_1^2 \cdot \dot{E}_{a1} + k_2^2 \cdot \dot{E}_{a2} \quad = \dot{E}_{c0} + \dot{E}_{c1} + \dot{E}_{c2}$$

$$\Rightarrow \begin{bmatrix} \dot{E}_a \\ \dot{E}_b \\ \dot{E}_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \cdot \begin{bmatrix} \dot{E}_{a0} \\ \dot{E}_{a1} \\ \dot{E}_{a2} \end{bmatrix} \Rightarrow \begin{bmatrix} \dot{E}_{a0} \\ \dot{E}_{a1} \\ \dot{E}_{a2} \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix}^{-1} \cdot \begin{bmatrix} \dot{E}_a \\ \dot{E}_b \\ \dot{E}_c \end{bmatrix}$$

$$\dot{E}_{a0} = \frac{1}{3} (\dot{E}_a + \dot{E}_b + \dot{E}_c)$$

$$\Rightarrow \dot{E}_{a1} = \frac{1}{3} (\dot{E}_a + a^2 \cdot \dot{E}_b + a \cdot \dot{E}_c)$$


$$\dot{E}_{a2} = \frac{1}{3} (\dot{E}_a + a \cdot \dot{E}_b + a^2 \cdot \dot{E}_c)$$



# Exercises
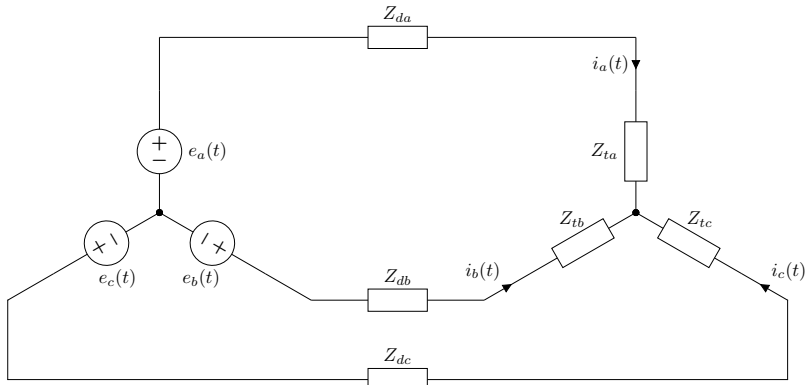
## BT 10.1

- Given a balanced three-phase circuit  $\dot{E}_a = 200\angle 0^\circ \text{ V}$ ;  
 $Z_{da} + Z_{ta} = 100\angle 60^\circ \Omega$
- Determine the total power absorbed by the load





# Exercises

## Exercise 10.1: Determine average power

- Because the circuit is balanced, the current in each phase is:

$$\dot{I}_a = \frac{\dot{E}_a}{Z_{da} + Z_{ta}} = 2 \angle -60^\circ \text{ A}$$

⇒ Average power on one phase

$$P_a = \dot{E}_a \cdot \dot{I}_a \cdot \cos \varphi = 200 \cdot 2 \cdot \cos 60^\circ = 200 \text{ W}$$

⇒ The total average power on the load is 600 W



# Exercises

## Exercise 10.1: Determine instantaneous power

- Consider a three-phase power system with frequency 50 Hz

$$\Rightarrow e_a(t) = 200\sqrt{2} \sin(100\pi t) \text{ V}$$

$$i_a(t) = 2\sqrt{2} \sin(100\pi t - 60^\circ) \text{ A}$$

- Instantaneous power on phase A

$$\begin{aligned} p_a(t) &= [200\sqrt{2} \sin(100\pi t) 2\sqrt{2} \sin(100\pi t - 60^\circ)] \\ &= 400[\cos(60^\circ) - \cos(200\pi t - 60^\circ)] \\ &= 200 - 400 \cos(200\pi t - 60^\circ) \text{ W} \end{aligned}$$

- Similarly, instantaneous power on phases B and C

$$p_b(t) = 200 - 400 \cos(200\pi t - 300^\circ) \text{ W}$$

$$p_c(t) = 200 - 400 \cos(200\pi t - 180^\circ) \text{ W}$$


- Total instantaneous power  $p(t) = p_a(t) + p_b(t) + p_c(t) = 600 \text{ W}$



# Exercises
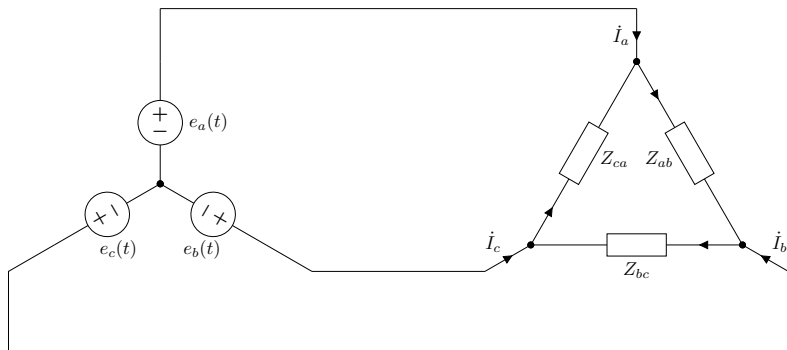
## BT 10.2

- Given a balanced three-phase circuit  $\dot{E}_a = 100/\underline{10^\circ}$  V;  
 $Z_{ab} = 8 + j4 \Omega$
- Determine the load phase currents and line currents





# Exercises

## BT 10.2

- Line voltage:  $\dot{U}_{\text{line}} = \dot{U}_{\text{phase}}\sqrt{3}/30^\circ = 100\sqrt{3}/40^\circ \text{ V}$
- Load phase current:  $\dot{I}_{pL} = \frac{\dot{U}_{\text{line}}}{Z_{ab}} = \frac{100\sqrt{3}/40^\circ}{8 + j4} = 19,3655/13,43^\circ \text{ A}$
- Load line current:  $\dot{I}_{lL} = \dot{I}_{pL}\sqrt{3}/-30^\circ = 19,3655\sqrt{3}/13,43^\circ - 30^\circ = 33,542/-16,57^\circ \text{ A}$
- Use symmetry to infer the other currents



# Exercises

## BT 10.3

- Given a Y-Y connected three-phase circuit with source set  $\dot{E}_a = 220/\underline{10^\circ} \text{ V}$ ;  $\dot{E}_b = 210/\underline{-100^\circ} \text{ V}$ ;  $\dot{E}_c = 215/\underline{110^\circ} \text{ V}$
- and load  $Z_a = Z_b = Z_c = 10 + j5 \Omega$
- Determine the current in each phase

## BT 10.4

- Given a Y-Y connected three-phase circuit with source set  $\dot{E}_a = 220/\underline{10^\circ} \text{ V}$ ;  $\dot{E}_b = 210/\underline{-100^\circ} \text{ V}$ ;  $\dot{E}_c = 215/\underline{110^\circ} \text{ V}$
- and load  $Z_a = 10 + j5 \Omega$ ;  $Z_b = 12 + j4 \Omega$ ;  $Z_c = 15 + j6 \Omega$
- Determine the current in each phase

# Appendix: Circuit Simulation with LTspice







# Introduction to SPICE and LTspice

- SPICE is a popular electrical and electronic circuit simulation tool in academia and industry
- SPICE stands for **S**imulation **P**rogram with **I**ntegrated **C**ircuit **E**mphasis, created at the University of California, Berkeley, USA, in the 1970s
- SPICE was originally a tool for describing and solving circuits using command-code descriptions (netlists)
- Later, software tools were developed to help create netlists by drawing circuits through graphical interfaces
- Commercial SPICE-based circuit simulation software: OrCAD PSpice, PrimeSim HSPICE, etc.
- Free SPICE-based circuit simulation software: LTspice, TINA, etc.
- LTspice is a free tool from Linear Technology (now part of Analog Devices) powerful enough for most study and research tasks related to circuits

# LTspice Startup Interface

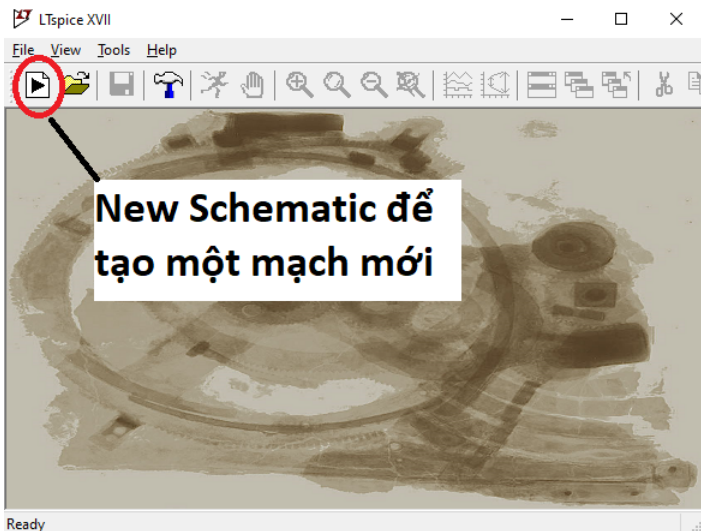


# Main Toolbar

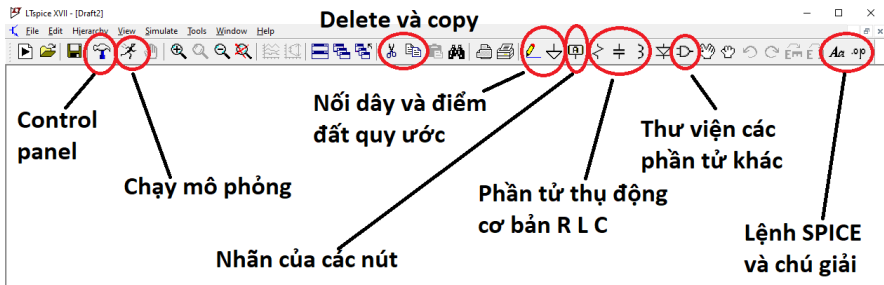

## Some LTspice operations


- End an operation: right-click
- Start an operation: choose a tool icon (e.g., scissors mean delete, the hand means move, etc.) and then select the element to act on. (LTspice does not operate in the usual way of selecting an element first and then choosing an operation; but in the opposite order.)
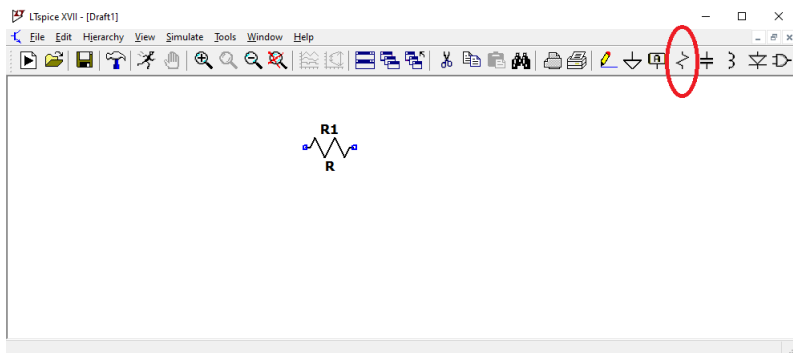
# Example 1: Getting Started with LTspice




1. Click the button to place a resistor element
2. Before placing the element, press **Ctrl+R** to rotate it horizontally
3. Left-click to place the element
4. Right-click to exit resistor-placement mode
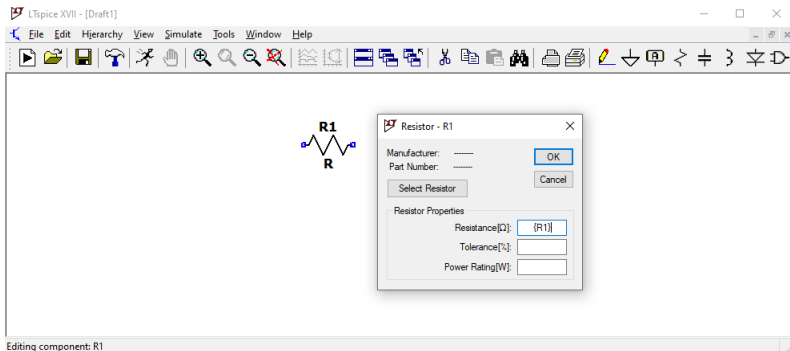
# Example 1: Getting Started with LTspice




1. Point the mouse to the resistor element
2. Right-click to open the value-entry dialog
3. Enter the resistor parameter value as **{R1}** (note the braces)  
(Recommendation: enter a parameter and then declare the value, rather than entering the value directly on the element)
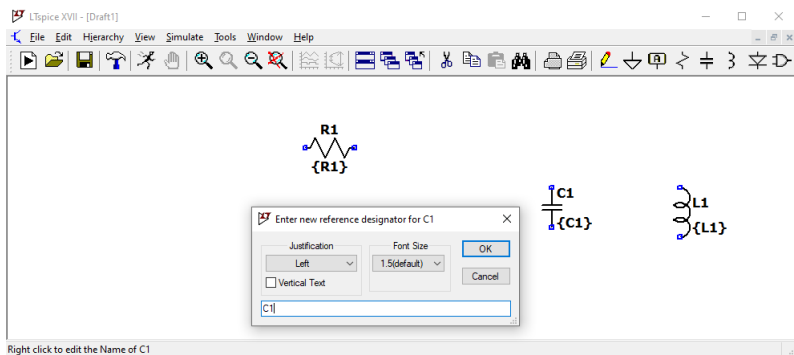
# Example 1: Getting Started with LTspice




1. Continue placing and entering parameter values for L and C elements
2. To change element names and parameter values: move the mouse to the text position of the element name or value and right-click
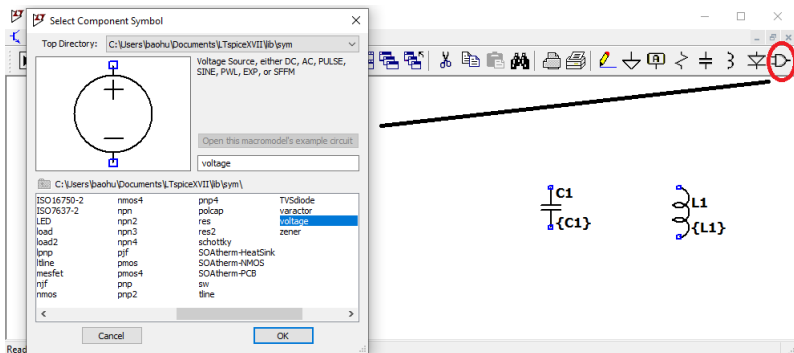
# Example 1: Getting Started with LTspice




1. Click the component-library button to open LTspice's rich component library
2. Choose **voltage** to place a voltage-source element
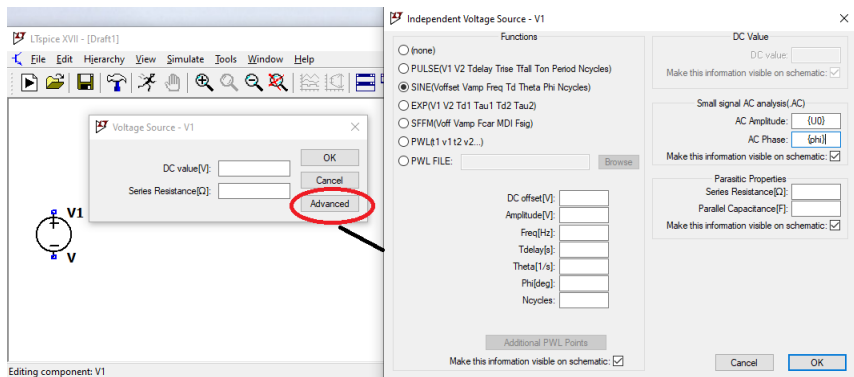
# Example 1: Getting Started with LTspice




1. Right-click the voltage source → open the default DC-source dialog
2. Click **Advanced** to open the advanced dialog
3. Enter amplitude **{U0}** and phase angle **{phi}** under **AC analysis**
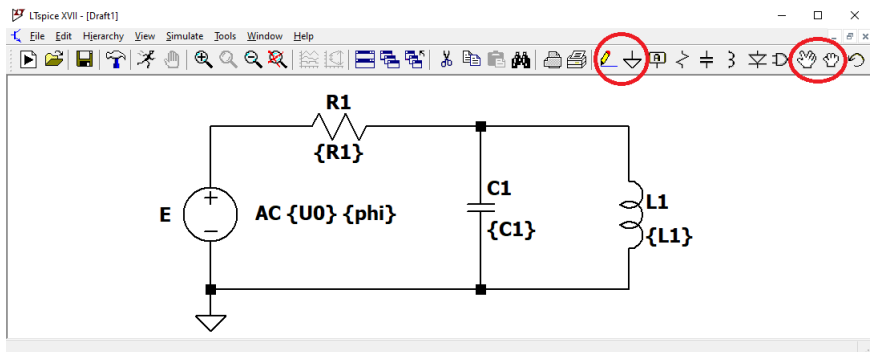
# Example 1: Getting Started with LTspice




1. Use **Move** or **Drag** to arrange elements and text  
(Note the difference between **Move** and **Drag** after wiring)
2. Place the reference ground and connect wires
3. The source element name can be changed from **V1** to **E**
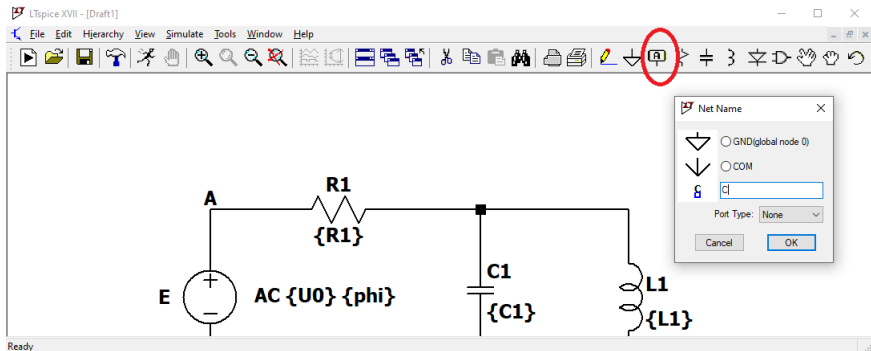
# Example 1: Getting Started with LTspice




- Labels can be attached to nodes whose potentials relative to ground need to be determined
- Here, node potential  $A$  equals the source voltage  $E$ , and node potential  $C$  equals the voltage on capacitor  $C1$  and inductor  $L1$
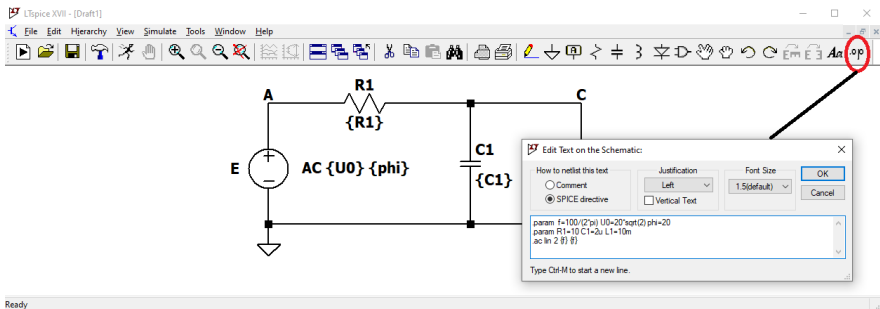
# Example 1: Getting Started with LTspice




- Write parameter-value declarations **.param** and the AC simulation command **.ac** by clicking the **.op** button to open the command-entry dialog.
- Use **SPICE directive** for commands and **Comment** for comments
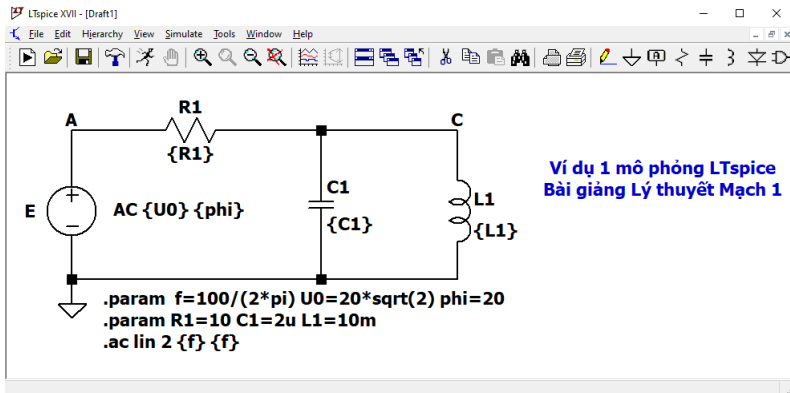
# Example 1: Getting Started with LTspice




- The command `.ac lin 2 {f} {f}` solves the AC circuit with a linear frequency sweep and 2 calculation points
- In this example, the circuit is solved at one frequency, so both frequencies are set to **f**
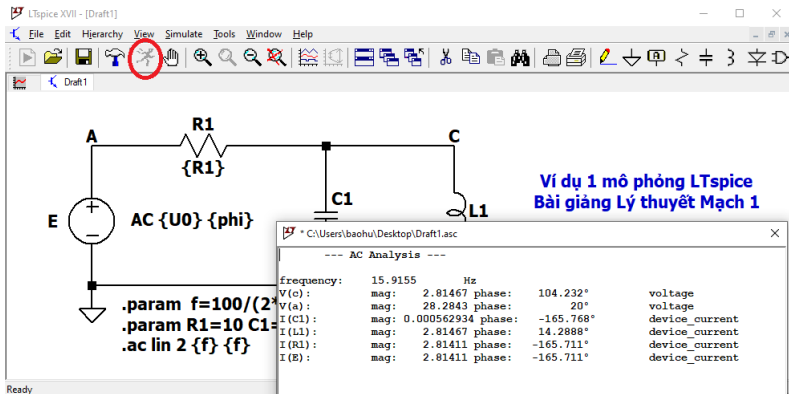
# Example 1: Getting Started with LTspice




- Click **Run** to run the simulation and obtain magnitude and phase results
- Pay attention to current directions. Especially important in circuits with current-controlled sources
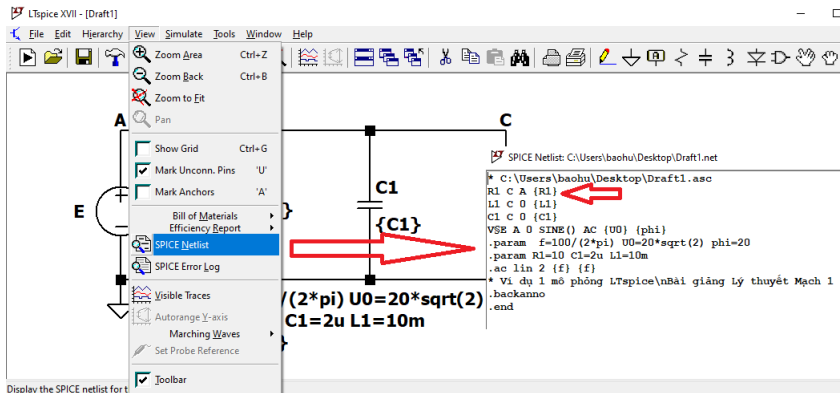
# Example 1: Getting Started with LTspice




- Use **View** → **SPICE Netlist** to view the SPICE netlist
- The netlist shows that resistor R1 is connected from C to A → the direction of current  $I_{CA}$  is the positive reference direction
- The simulated current  $I_{R1}$  is opposite in phase to the positive reference current  $I_{CA}$
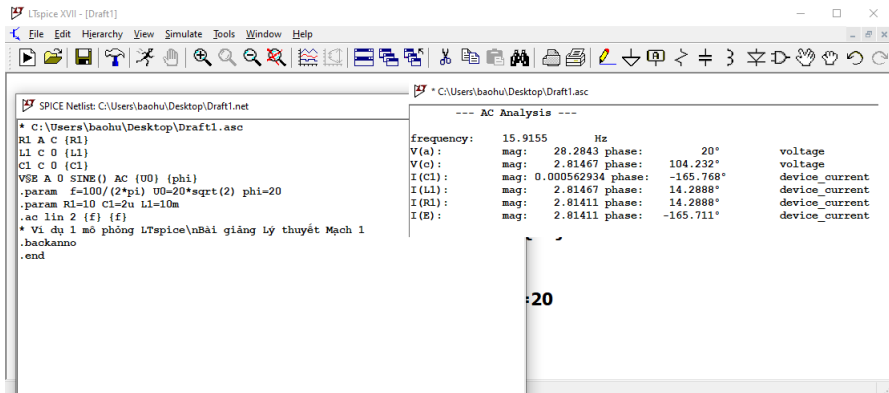
# Example 1: Getting Started with LTspice




- If the positive reference direction of  $\dot{I}_{R1}$  needs to be  $A \rightarrow C$ , use **Move** to pull R1 off the wire, then press **Ctrl+R** to reverse R1
- Check the netlist and results again

## Example 2: Voltage-Controlled Source

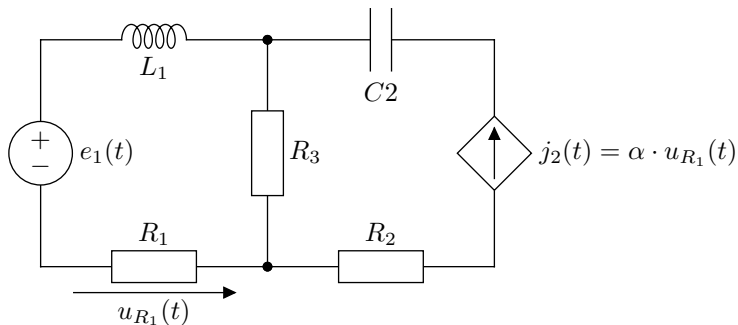


- $e_1(t) = 5\sqrt{2} \sin(100t + 20^\circ) \text{ V}$ ;  $L_1 = 0,5 \text{ mH}$ ;  $C_2 = 2000 \mu\text{F}$ ;
- $R_1 = 2 \Omega$ ;  $R_2 = 1 \Omega$ ;  $R_3 = 5 \Omega$ ;  $\alpha = 1,5$ .

## Example 2: Voltage-Controlled Source

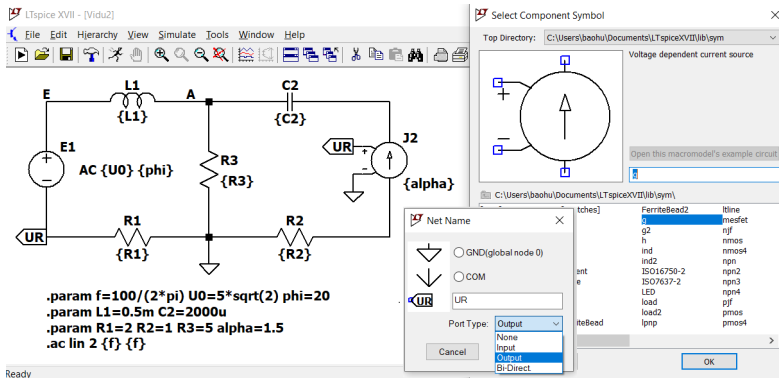


- A VCCS is element **g** (VCVS is **e**)
- Node-potential label **UR** with corresponding **output** and **input** types
- Compare with hand-determined results (note: LTspice determines amplitude, while Circuit Theory uses RMS values)

## Example 3: Current-Controlled Source

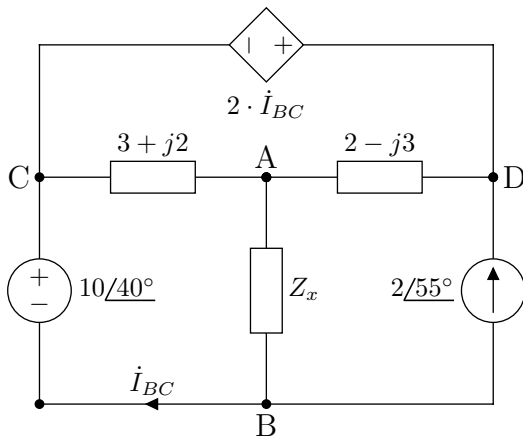


- Find  $Z_x$  such that the power delivered to this impedance is maximized

## Example 3: Current-Controlled Source

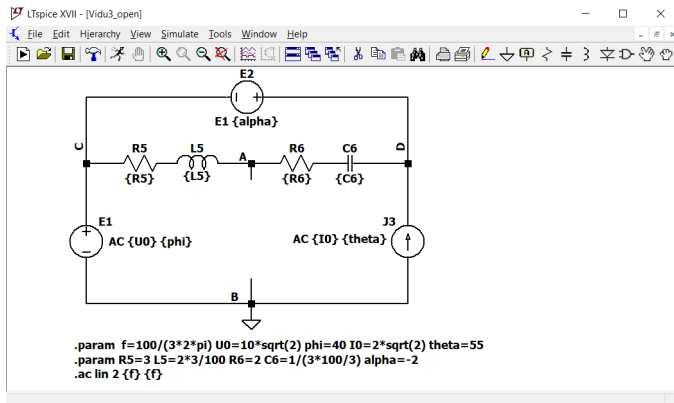


- Determine open-circuit voltage  $\dot{U}_{oc} = \dot{U}_{AB}$ . Assume arbitrary  $\omega$ .
- A CCVS is element **h** (CCCS is **f**)
- A CC source must declare which element current it depends on (here, E1). Pay attention to sign of  $\alpha$  w.r.s to direction of  $\dot{I}_{BC}$ .

## Example 3: Current-Controlled Source

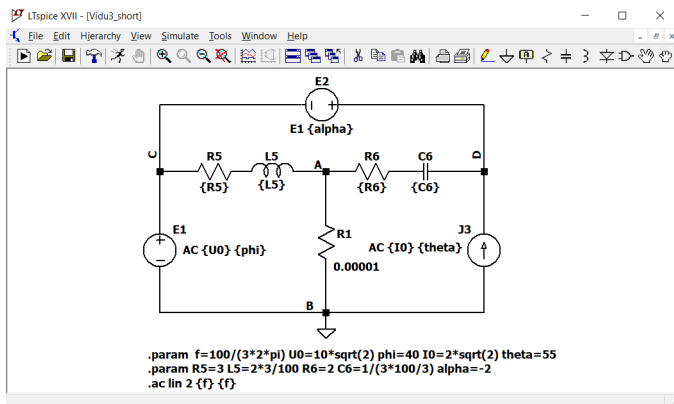

- Determine the short-circuit current  $\dot{I}_{sc} = \dot{I}_{AB}$
- LTspice determines currents through elements  $\rightarrow$  use a very small resistor to approximate a wire.

# Example 3: Current-Controlled Source

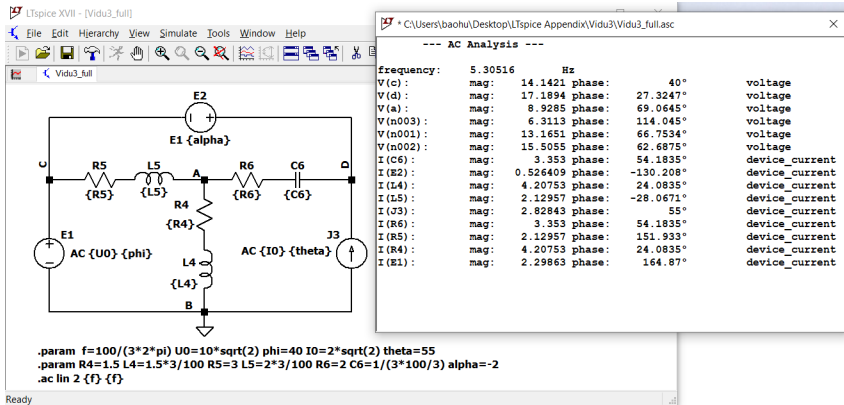


- Determine  $Z_{Th}$  and the corresponding matched load impedance
- Recheck the result with the load value just found
- Drawback: LTspice current-controlled sources are visually easy to confuse with independent sources

## Example 4: Circuit with Mutual Inductance


Simulate the circuit in Example 7.1

Given a transformer circuit. Determine the currents and voltages on the coils.
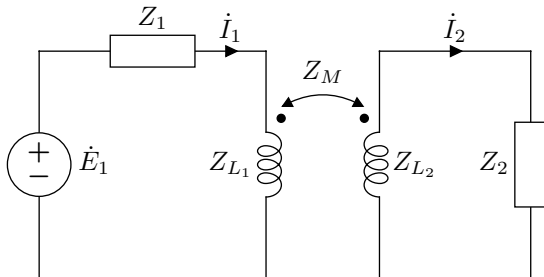
$$\begin{aligned}\dot{E}_1 &= 12/\underline{0^\circ} \text{ V}; \\ Z_1 &= 5 + j3 \text{ } (\Omega); \\ Z_{L_1} &= j8 \text{ } (\Omega); \\ Z_{L_2} &= j6 \text{ } (\Omega); \\ Z_M &= j6 \text{ } (\Omega); \\ Z_2 &= 5 - j2 \text{ } (\Omega)\end{aligned}$$


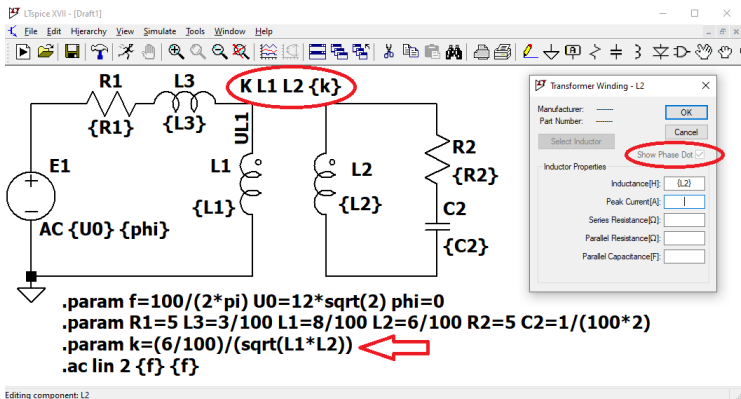
# Example 4: Circuit with Mutual Inductance



- Enable display of coil polarity dots
- Mutual inductance is defined between coils using the command **K L1 L2 {k}**
- Coupling coefficient  $k = M/\sqrt{L_1 L_2}$